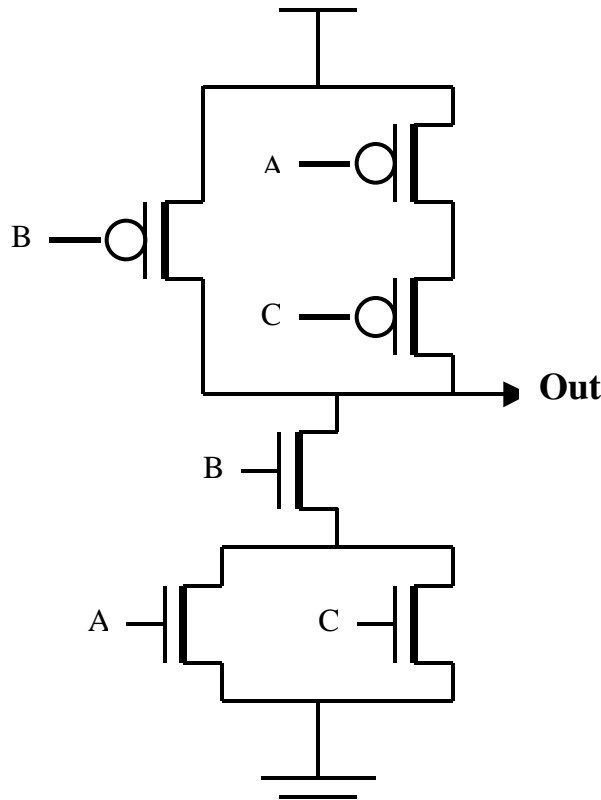


Transistor-Level Circuit Understanding

For the following switch level circuit, complete the truth table computed. If a floating or shorted output is detected, indicate that in the truth table. If no floats or shorts are detected, write the Boolean expression computed by the circuit.

A	B	C	Out
0	0	0	<b>1</b>
0	0	1	<b>1</b>
0	1	0	<b>0</b>
0	1	1	<b>0</b>
1	0	0	<b>1</b>
1	0	1	<b>1</b>
1	1	0	<b>0</b>
1	1	1	<b>1</b>

“Out” is “1” if B is “0” or A’ and C’ are both “0”.



Write the Boolean expression for this function,  $Out = \underline{B' + A'C'}$


Given the Boolean expression:  $Out = A'C + ABC \equiv C(A'+AB) \equiv C(A'+B)$

**(if logic expression is not simplified, there should be 10 FET's below)**

Complete the truth table.

A	B	C	Out	Note
0	0	0	0	
0	0	1	1	$A'C=1$
0	1	0	0	
0	1	1	1	$A'C=1$
1	0	0	0	
1	0	1	0	
1	1	0	0	
1	1	1	1	$ABC = 1$

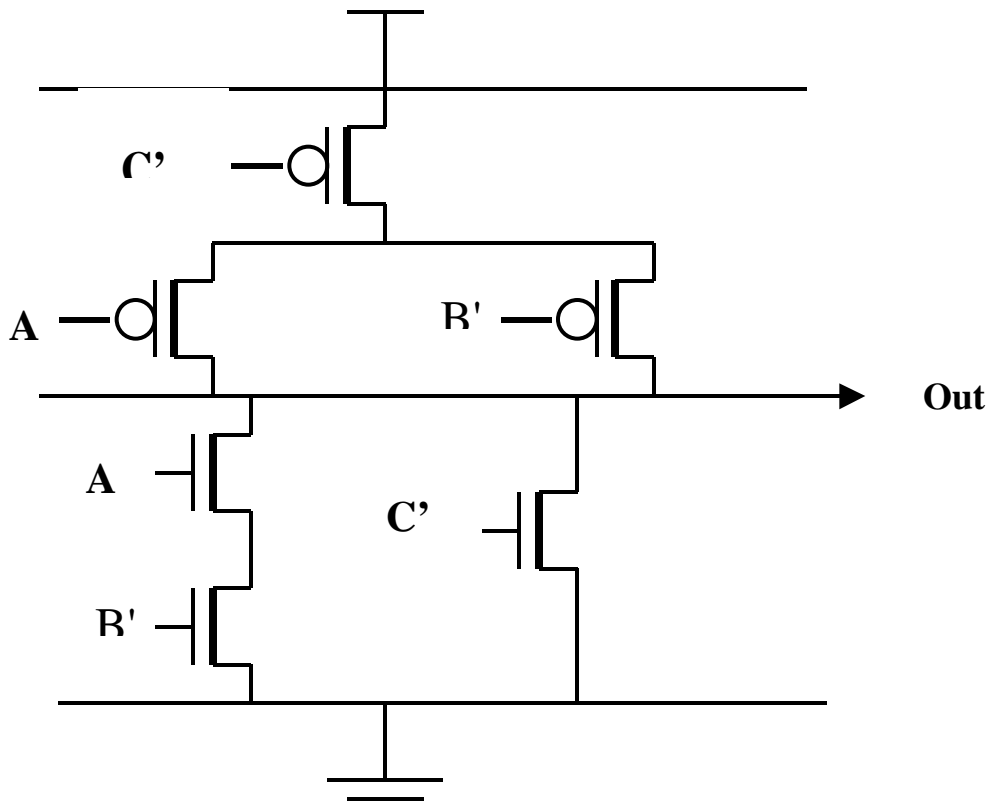Draw the CMOS transistor diagram. Assume A, A', B, B', C, C' signals are available.



Given the truth table.

A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Write the Boolean expression as 3 terms: **Out = AB + BC + AC** from observation that Out is “1” whenever any two inputs are one).

**By the minterm approach:**  $Out = A'BC + AB'C + ABC' + ABC$

**Using Boolean Equalities:**  $A'BC + ABC = BC$  and  $ABC = ABC + ABC + ABC$

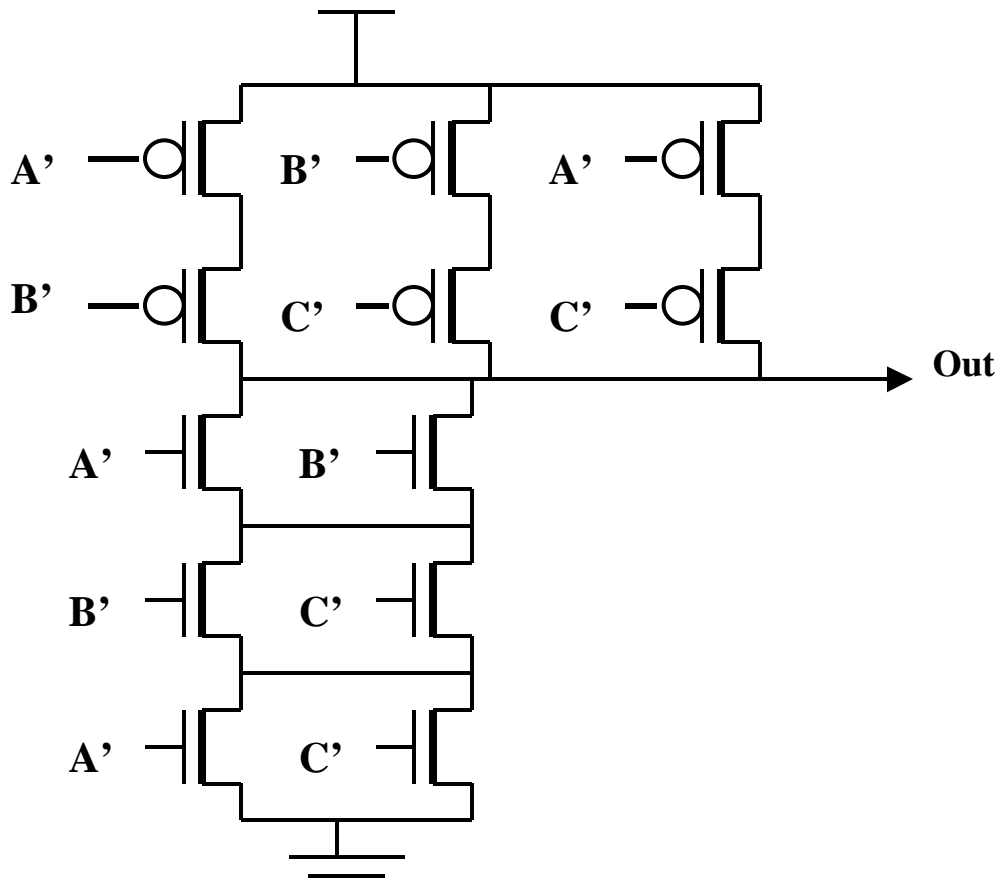**OUT = AB + BC + AC**

Draw the CMOS transistor diagram. Assume A, A', B, B', C, C' signals are available.



Bonus – use a Karnaugh map to find the simplest logic expression for Problem 3. There are three Essential Prime Implements, AC (blue), BC (green), and AB (red).

A \ BC	00	01	11	10
0	0	0	1	0
1	0	1	1	1