

ECE2030b HW-2 Due Wed. Sept.18, 2002 --- ANSWERS


**Question 1 – Truth Table.**Given the Boolean expression:  $Out = AB + ABC + A'B'$ Hint – simplify first AB + A'B'

Complete the truth table.

A	B	C	Out
0	0	0	<u>1</u>
0	0	1	<u>1</u>
0	1	0	<u>0</u>
0	1	1	<u>0</u>
1	0	0	<u>0</u>
1	0	1	<u>0</u>
1	1	0	<u>1</u>
1	1	1	<u>1</u>

**Question 2 – CMOS Logic**

Draw the CMOS transistor diagram for  $AB + CD$ . Assume  $A, A', B, B', C, C', D'$  and  $D'$  signals are available.

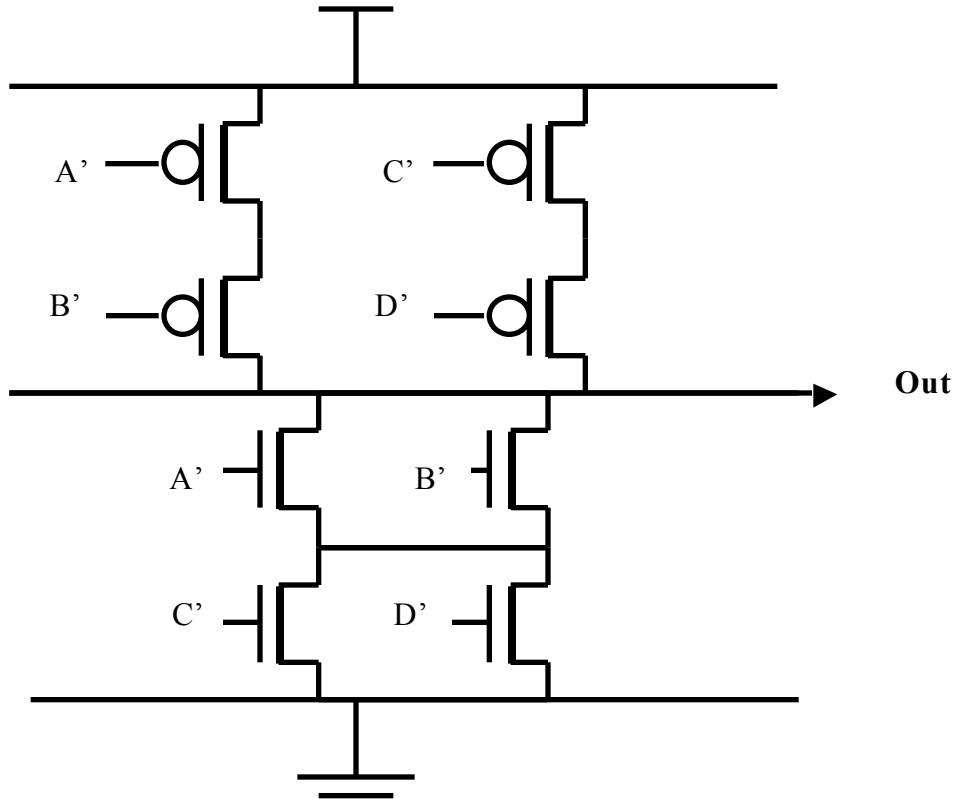

**Question 3 – Logic Identities**

Simplify the follow Boolean expressions:

A.  $X(X+Y)$  X

B.  $X + Y + XZ$   $X + Y$

C.  $(X' + Y)'$   $XY$

D.  $X + XY$  X

E.  $XY + YZ + X'Z$   $XY + X'Z$  (if  $YZ = 1$  then  $Y=1$  and  $Z=1$  &  $XY$  or  $X'Z = 1$ )

**Question 4 – Minterm and Maxterm Indices**

For the truth tables below, express the minterm sum of products, and the maxterm product of sums:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

sum of products    $A'BC' + AB'C + ABC$   

product of sums    $(A'+B'+C')(A'+B'+C)(A'+B+C)(A+B'+C')(A+B+C')$   

Draw a Karnaugh Map for the truth table in Question 4. Circle the Prime Implicants with a solid line. Label the Essential prime Implicants with a dashed line.  **$F = AC + A'BC'$**

A \ BC	00	01	11	10
0	0	0	0	1
1	0	1	1	0

.....AC.....

**Question 5 – Karnaugh Map** For the Karnaugh map below, circle the Prime Implicants and label the Essential Prime Implicants with “EPI” [all are “Essential” Prime Implicants except  $A'BC$  and  $A'CD$ ].

AB \ CD	00	01	11	10
00	0	1	1	0
01	1	0	1	1
11	0	0	0	1
10	0	1	1	0

Write the reduced logic expression:    $A'D + A'BD' + BCD' + (A'BC \text{ or } A'CD)$   

maxterm indices (decimal)   0, 2, 5, 7, 8, 10, 12, 13, 15