

# **CHAPTER VI**



## **COMBINATIONAL LOGIC BUILDING BLOCKS**

- Combinational logic
  - Output at any time is determined completely by the current input.
    - We will later consider circuits where the output is determined by the input and the current state (memory) of the system.
  - In this chapter we will consider some useful building blocks that can be pieced together and used in larger designs. This will include:
    - Multiplexers (selectors) and demultiplexers (distributors)
    - Encoders, priority encoders, decoders
    - Adders (full and half)
    - Parity generators and parity checkers
    - Shifters and rotators
    - Comparators

# DECODERS
  
## BASIC DECODER

- Standard decoder is an  $n$ -to- $m$ -line decoder, where  $m \leq 2^n$ .
- Example: 3-to-8-line decoder




- All outputs  $D_m$  are low except for the one corresponding to the binary value of the input  $A_n \dots A_1 A_0$ .

# DECODERS

## DECODERS WITH ENABLE

- Often, combinational logic building blocks will also have an enable line that turns on outputs or leaves them off.

3-to-8 Decoder  
with Enable

 

# **DECODERS**

## **TRUTH TABLES**



- Truth table for a **3-to-8-line decoder**:

<b>Inputs</b>				<b>Outputs</b>							
$A_2$	$A_1$	$A_0$	$E$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
<b>X</b>	<b>X</b>	<b>X</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>

# DECODERS
  
## IMPLEMENTATION

- How can a decoder be implemented? Fill in the circuit!




# DECODERS

## DESIGNING WITH DECODERS

- Any Boolean function can be implemented using a **decoder** and **OR** gates by ORing together the function's **minterms**.

Inputs			Outputs	
$A_2$	$A_1$	$A_0$	$F_1$	$F_2$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

 


# DECODERS
 
## DECODER NETWORKS

- We can also use multiple decoders to form a larger decoder.

3-to-8 Decoder Implemented  
with two 2-to-4 Decoders



**A<sub>2</sub>** used with enable input to control which decoder will output the **1**.


**A<sub>1</sub>** and **A<sub>0</sub>** used to select which output on specific decoder will output **1**.




# ENCODERS
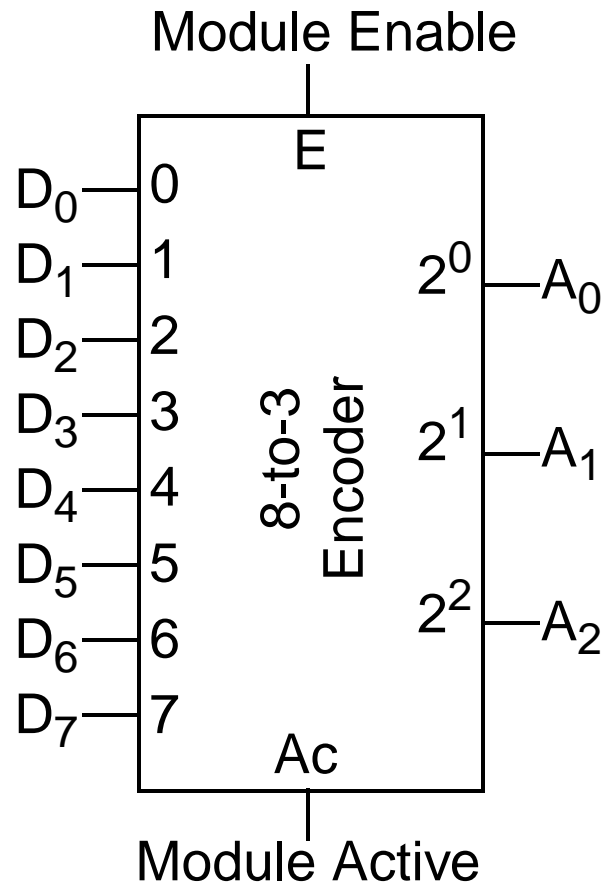
## BASIC ENCODER

- Standard binary encoder is an  $m$ -to- $n$ -line encoder, where  $m \leq 2^n$ .
- Example: 8-to-3-line encoder



Example:  
Input of 00010000

 

# ENCODERS

## ENCODER TRUTH TABLE

- Truth table for an **8-to-3-line encoder**:

Inputs								Outputs		
D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

- Assumed that only one input is **1**. What happens if more than one is **1**?


# ENCODERS

## DESIGNING WITH ENCODERS

- DECODERS
- ENCODERS
  - BASIC ENCODER
  - TRUTH TABLE

- Encoders are useful when the occurrence of one of several disjoint events needs to be represented by an integer identifying the event.

Example: Wind direction encoder

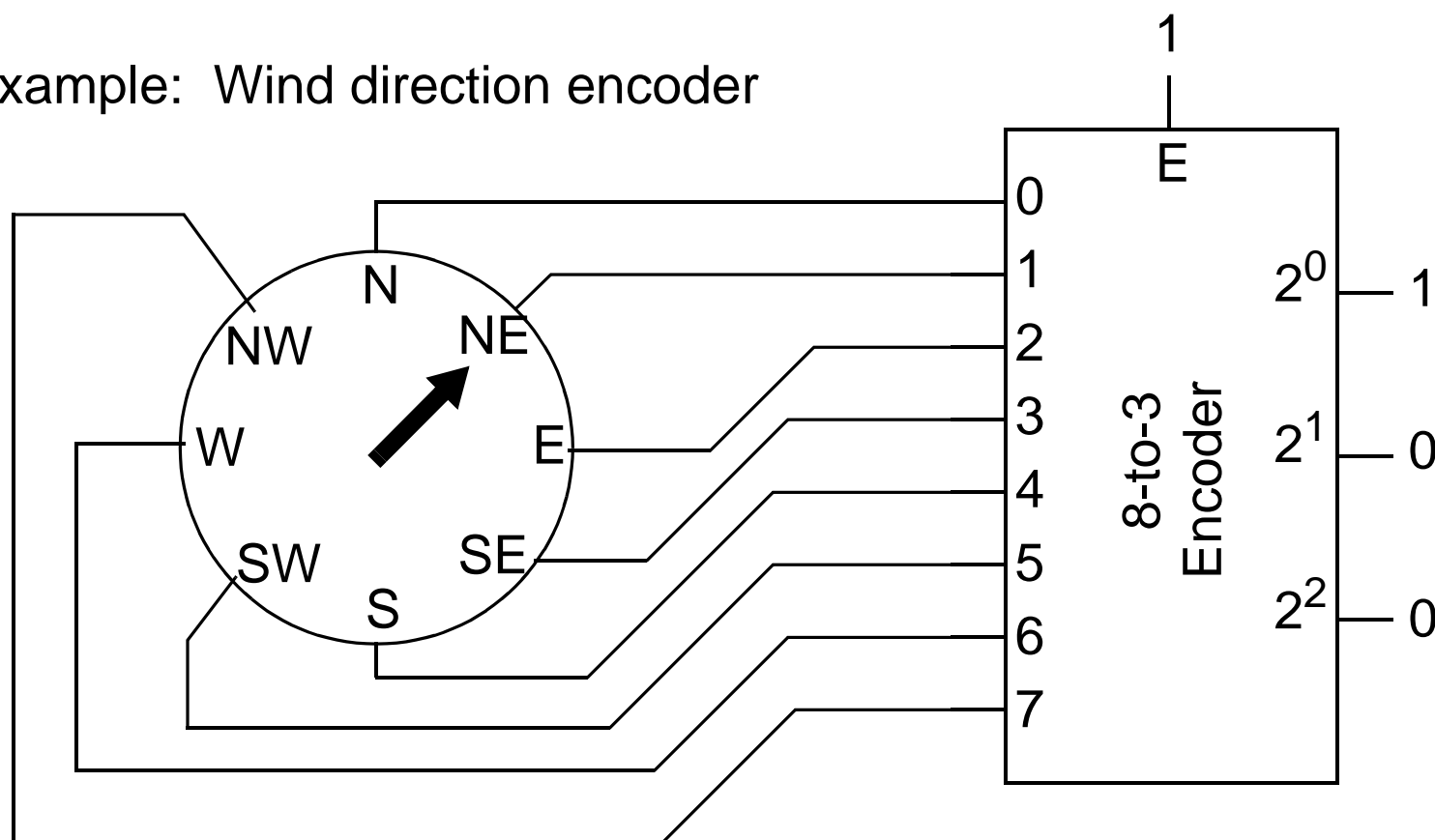

# ENCODERS

## PRIORITY ENCODERS

- A priority encoder takes the input of 1 with the highest index and translates that index to the output.


Inputs								Outputs		
D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

# ENCODERS

## DESIGN WITH P-ENCODER

- Priority encoders are useful when inputs have a predefined priority and we wish to select the input with the highest priority.

Example: Resolving interrupt requests

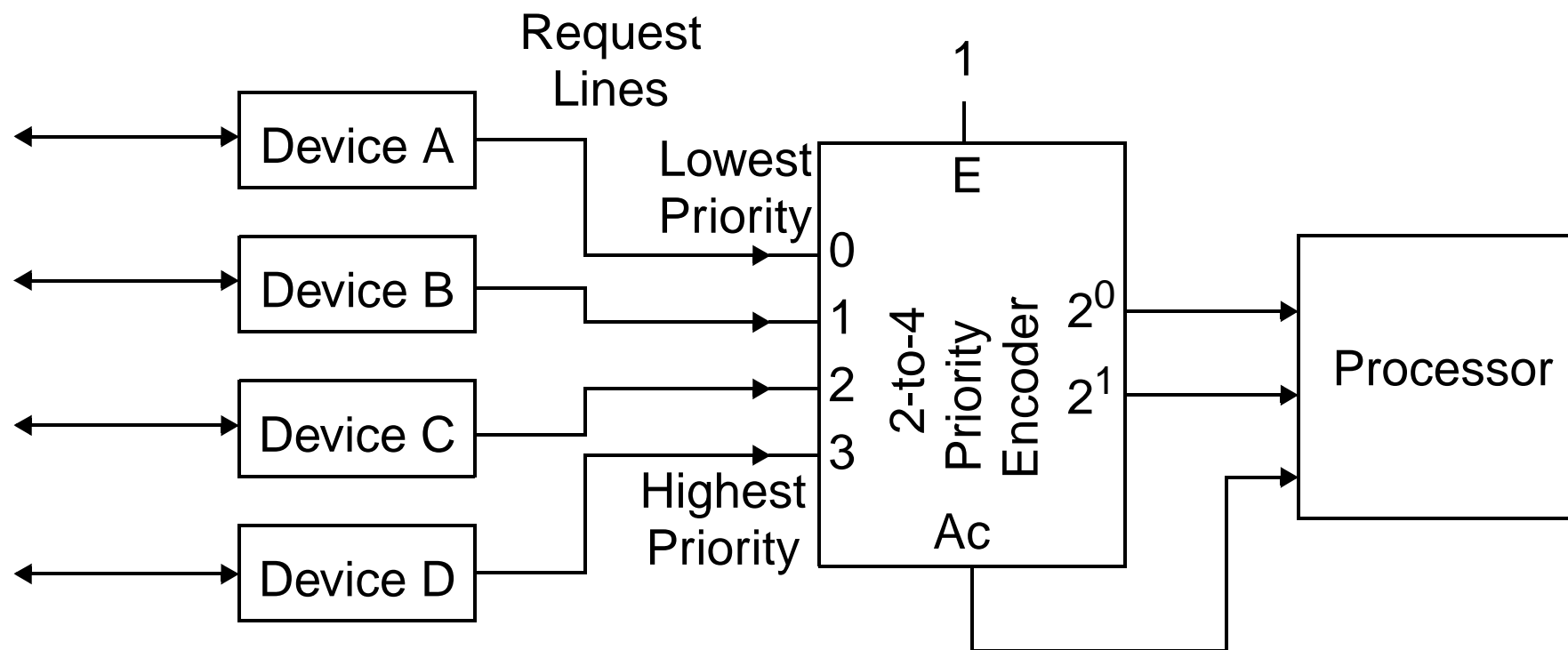


pp. 253-256 of Ercegovic, Lang and Moreno, "Introduction to Digital Systems", 1999.

# MULTIPLEXERS
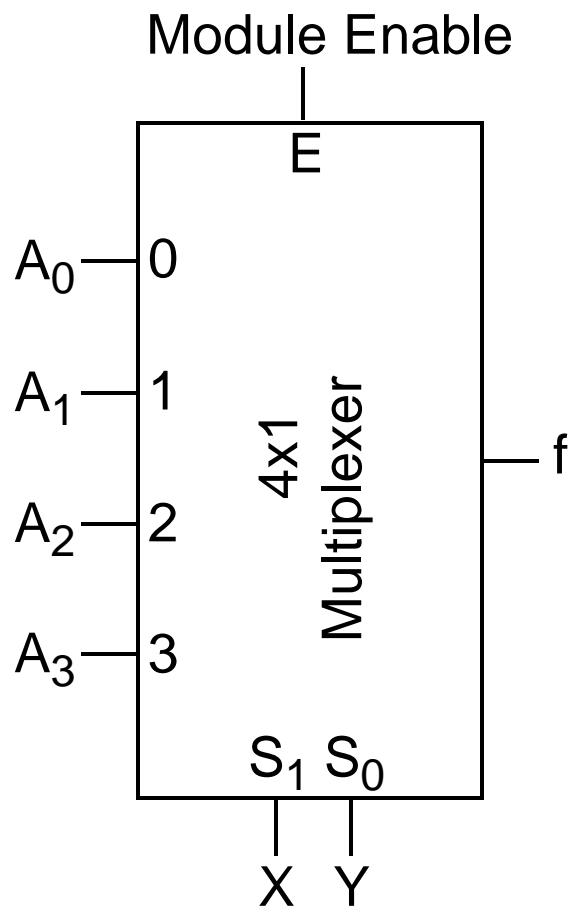
## BASIC MULTIPLEXER (MUX)

- Selects one of many inputs to be directed to an output.




		Inputs				Output
X	Y	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	F
0	0	X	X	X	0	A <sub>0</sub> =0
0	1	X	X	0	X	A <sub>1</sub> =0
1	0	X	0	X	X	A <sub>2</sub> =0
1	1	0	X	X	X	A <sub>3</sub> =0
0	0	X	X	X	1	A <sub>0</sub> =1
0	1	X	X	1	X	A <sub>1</sub> =1
1	0	X	1	X	X	A <sub>2</sub> =1
1	1	1	X	X	X	A <sub>3</sub> =1

# MULTIPLEXERS
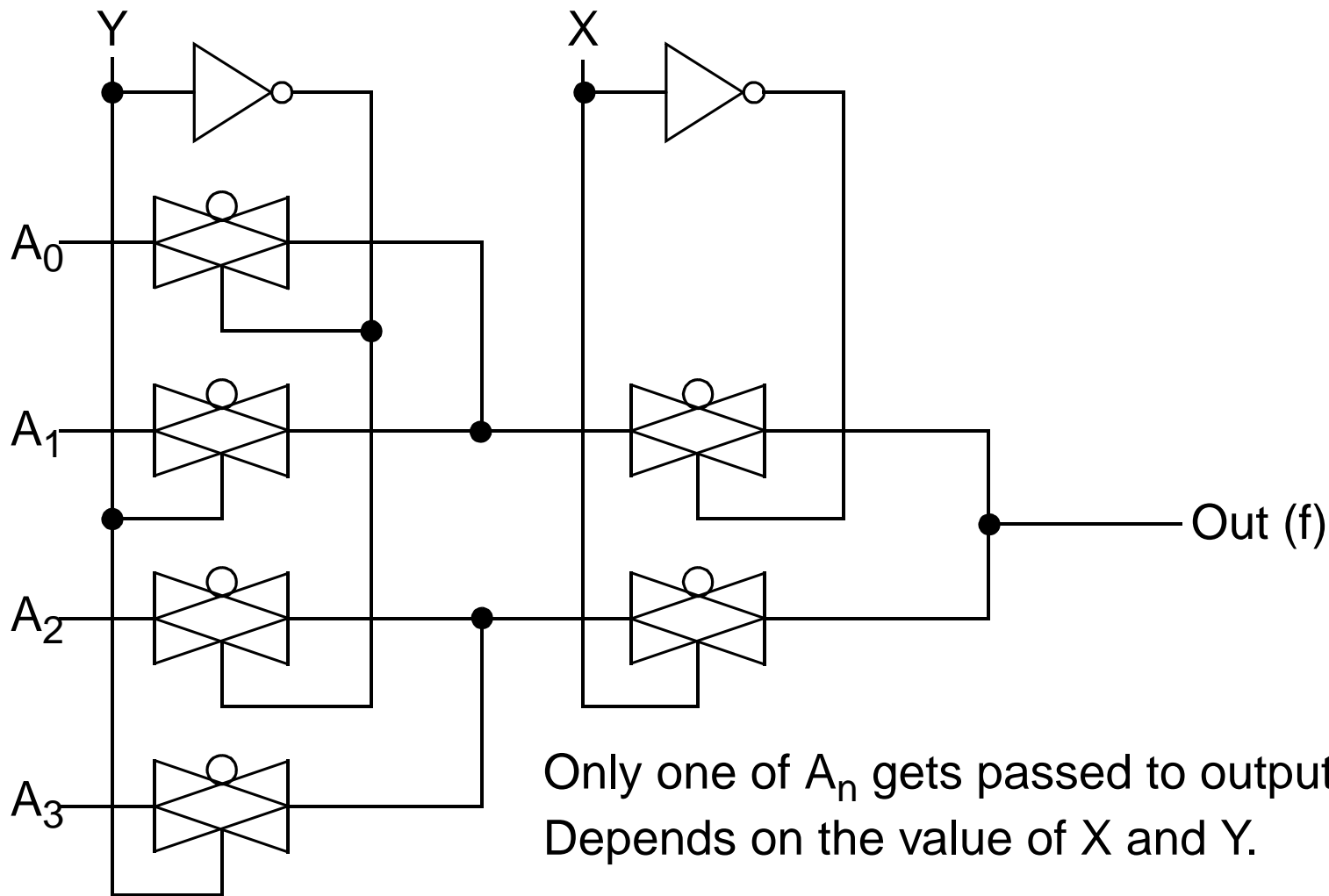
## USING PASS GATES

- The **4x1 mux** can be implemented with **pass gates** as follows.




# MULTIPLEXERS

## DESIGN WITH MULTIPLEXERS

- ENCODERS
- MULTIPLEXERS
  - BASIC MULTIPLEXER
  - USING PASS GATES

- Any Boolean function can be implemented by setting the inputs corresponding to the function and the selectors as the variables.

Example:

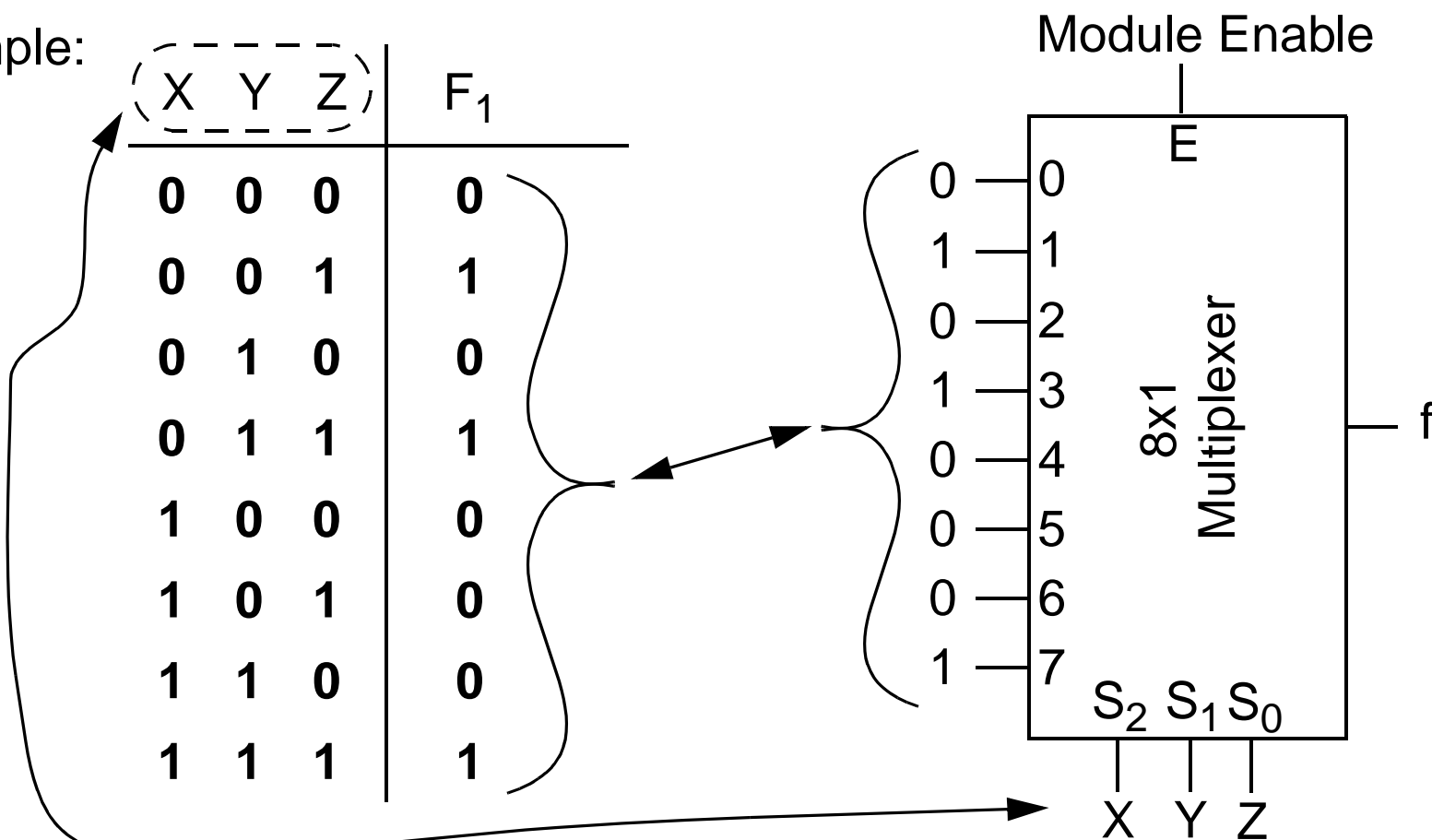




# DEMULTIPLEXERS
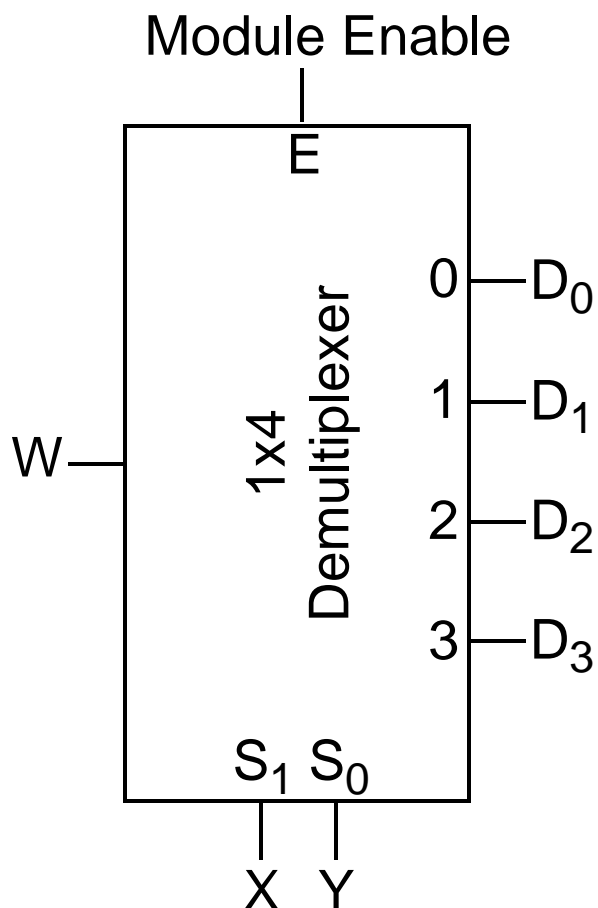
## BASIC DEMULTIPLEXER


- Takes one input and selects one of many outputs to direct the input.



Inputs			Outputs			
X	Y	W	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	0	0	W=0
0	1	0	0	0	W=0	0
1	0	0	0	W=0	0	0
1	1	0	W=0	0	0	0
0	0	1	0	0	0	W=1
0	1	1	0	0	W=1	0
1	0	1	0	W=1	0	0
1	1	1	W=1	0	0	0

- A demultiplexer is useful for routing an input to a desired location.


Example:

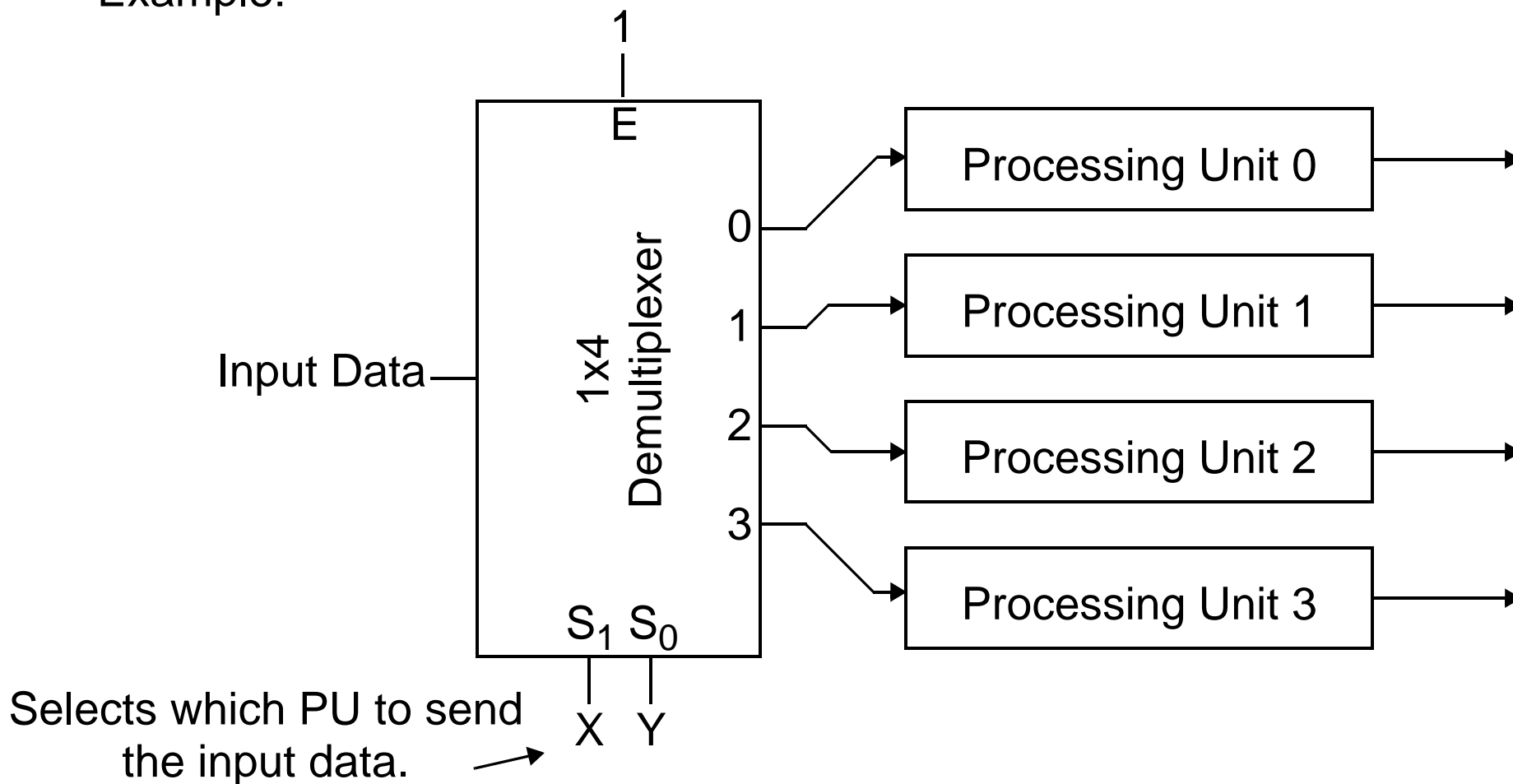

# SHIFTERS
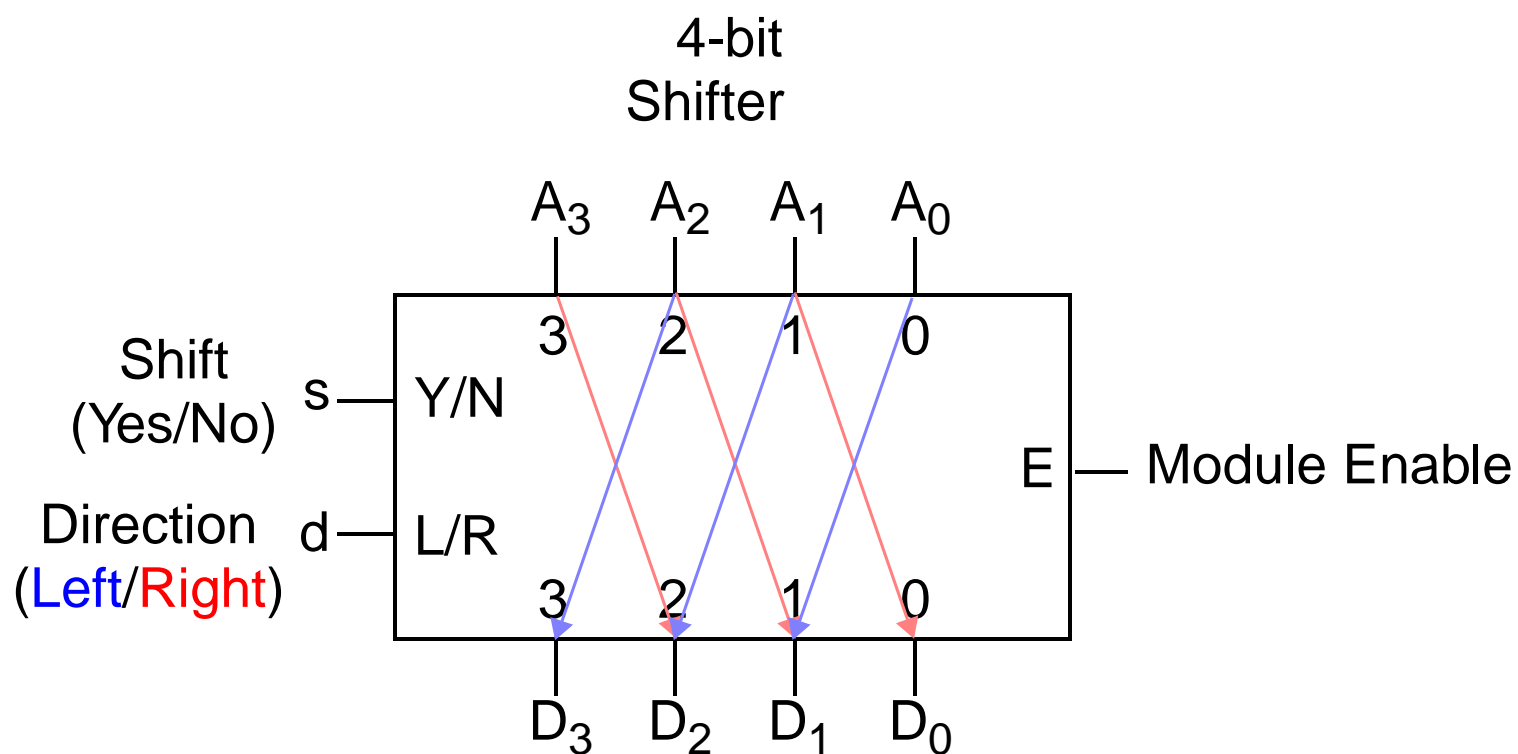
## BASIC SHIFTER


- A shifter takes a set of inputs and shifts it to the right or left.



# SHIFTERS
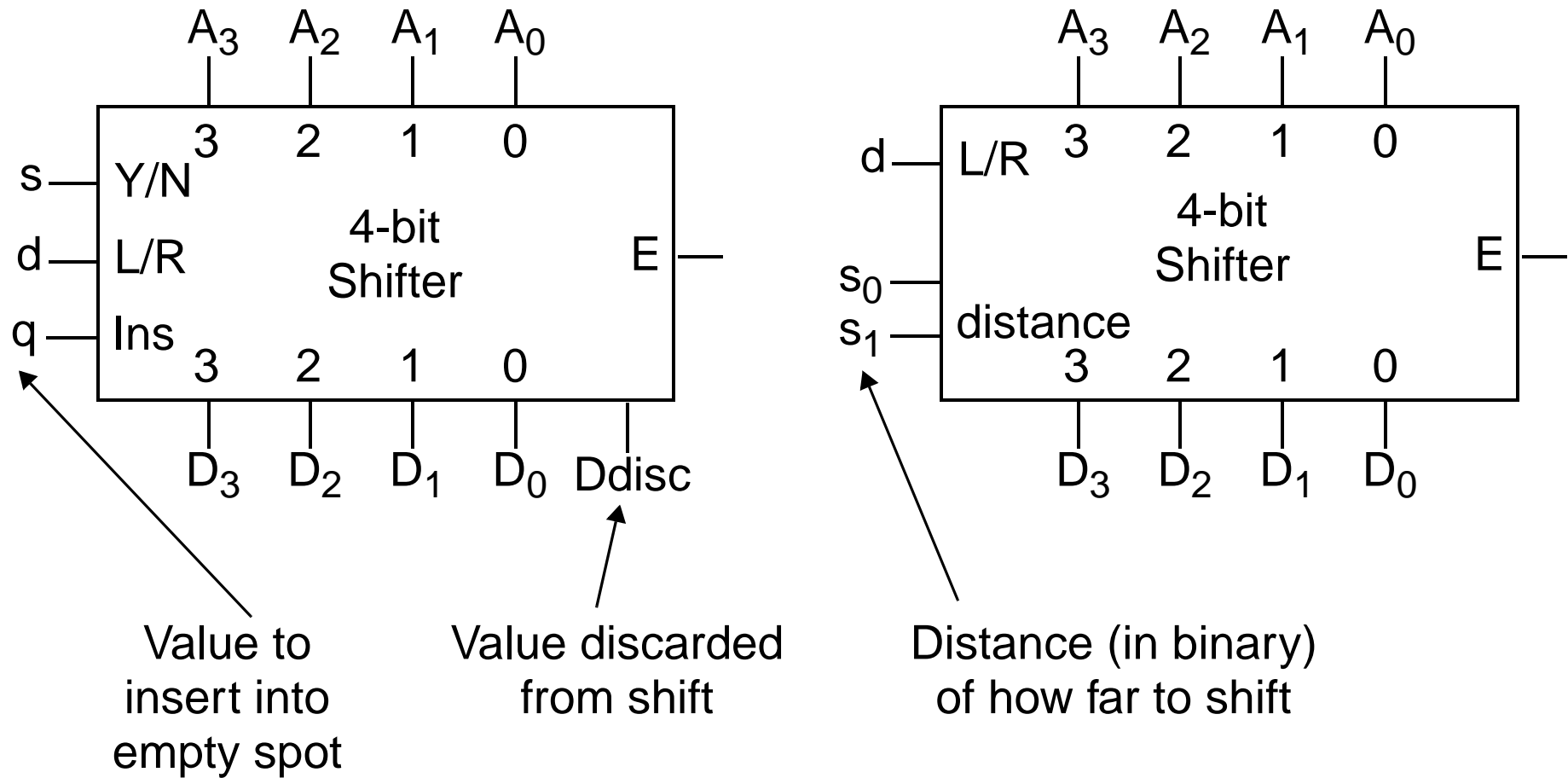
## COMMON SHIFTERS


- A whole variety of other shifters are possible such as



# ROTATORS
 
## BASIC ROTATOR


- A rotator takes a set of inputs and rotates it to the right or left.
- This is similar to a shifter except that instead of dropping the bit off of the end in the shifting, the normally discarded bit is taken and moved to fill the empty spot on the end.




# ADDERS
 
## HALF- AND FULL-ADDERS

- Two basic building blocks for arithmetic are half- and full-adders as depicted by the block diagrams below.



Half-adder

 

Full-adder

# ADDERS


## HALF-ADDER (HA)

- First of all, how do we add?
- 2's complement arithmetic allows us to add numbers normally.

Inputs		Sum	Carry-out
A	B	S	C <sub>OUT</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C_{OUT} = AB$$

 

# ADDERS

## FULL-ADDER (FA) (1)

- Half-adder missed a possible carry-in. A full-adder (FA) includes this additional carry-in.

Inputs		Carry-in	Sum	Carry-out
A	B	C <sub>IN</sub>	S	C <sub>OUT</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = AB + C_{IN}(A \oplus B)$$




# ADDERS

## FULL-ADDER (FA) (2)

- ADDERS
  - HALF- & FULL-ADDERS
  - HALF-ADDER (HA)
  - FULL-ADDER (FA)

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = AB + C_{IN}(A \oplus B)$$

 


# ADDERS
 
## BINARY ADDITION

- ADDERS
  - HALF- & FULL-ADDERS
  - HALF-ADDER (HA)
  - FULL-ADDER (FA)


- A 4-bit binary adder can be formed with four full-adders as follows.



# COMPARATORS
 
## MAGNITUDE COMPARATOR

- Given two  $n$ -bit magnitudes, A and B, a comparator indicates whether
  - $A = B$ ,  $A > B$ , or  $A < B$



# COMPARATORS

## MAGNITUDE COMPARATOR

- The approach is to use the XNOR function (equivalence) on each of the  $n$ -bits as follows

$$x_i = \mathbf{A}_i \mathbf{B}_i + \overline{\mathbf{A}_i} \overline{\mathbf{B}_i} = \overline{\mathbf{A}_i \oplus \mathbf{B}_i}$$

- The Boolean functions for a 4-bit magnitude comparator is as follows
  - $(\mathbf{A} = \mathbf{B}) = x_3 x_2 x_1 x_0$
  - $(\mathbf{A} > \mathbf{B}) = \mathbf{A}_3 \overline{\mathbf{B}_3} + x_3 \mathbf{A}_2 \overline{\mathbf{B}_2} + x_3 x_2 \mathbf{A}_1 \overline{\mathbf{B}_1} + x_3 x_2 x_1 \mathbf{A}_0 \overline{\mathbf{B}_0}$
  - $(\mathbf{A} < \mathbf{B}) = \overline{\mathbf{A}_3} \mathbf{B}_3 + x_3 \overline{\mathbf{A}_2} \mathbf{B}_2 + x_3 x_2 \overline{\mathbf{A}_1} \mathbf{B}_1 + x_3 x_2 x_1 \overline{\mathbf{A}_0} \mathbf{B}_0$

Note:  $\mathbf{A}_i \overline{\mathbf{B}_i}$  indicates whether  $\mathbf{A}_i > \mathbf{B}_i$ ,  $\overline{\mathbf{A}_i} \mathbf{B}_i$  indicates whether  $\mathbf{A}_i < \mathbf{B}_i$ , and  $x_i$  indicates whether  $\mathbf{A}_i = \mathbf{B}_i$ .


# BUILDING BLOCKS

## PARITY GENERATORS

- A parity generator/checker can detect a 1-bit error in a message.


To generate an even parity bit

$$P = X \oplus Y \oplus Z$$

 

To check a even parity bit

$$C = X \oplus Y \oplus Z \oplus P$$

 

Message			Even	
X	Y	Z	Parity Bit, P	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	0

If no errors detected, **C = 0**