 



# **CHAPTER VII**
 
## **SEQUENTIAL SYSTEMS - LATCHES & REGISTERS**


- So far...
  - So far we have dealt only with combinational logic where the output is formed from the current input.
- Sequential systems
  - Sequential systems extend the idea of combinational logic by including a **system state**, or in other words **memory**, to our system.
  - This allows our system to perform operations that build on past operations in a *sequential* manner (*i.e.* one after another).
  - Timing diagrams will be needed to analyze the operation of many sequential systems.



- Mealy machine
  - Sequential system where output depends on current input and state.



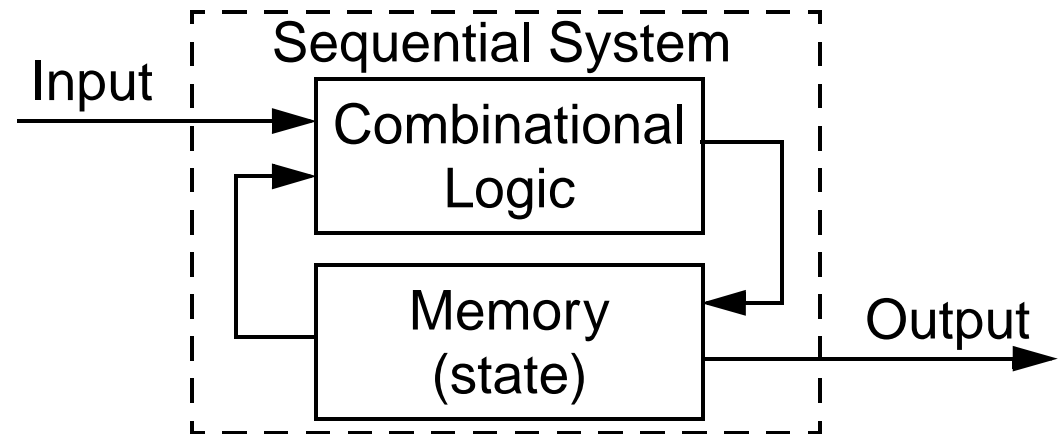
- Moore machine
  - Sequential system where output depends only on current state.




# STORING BITS
 
## STORING A BIT

- Since there are propagation delays in real components, this time delay can be used to store information.
- For instance, the following buffer has a propagation delay of  $t_{pd}$ .





Timing Diagram

 


# STORING BITS
  
## FEEDBACK LOOPS

- If we wish to store data for an indefinite period of time, then a feedback loop can be used to maintain the bit.



Can also use two inverters!

 


- How do we get the bit in there?

# STORING BITS
 
## LOADING A BIT

- To store a bit, we need a way of loading an input bit into the structure and making/breaking the connection in the feedback loop.
- One way of breaking connections is to use transmission gates.



Note: The latch is level-sensitive.

If  $A$  changes while  $S_1 = 1$ , then  $Q$  will change as well.


- $A$  gets temporarily stored in the inverters when  $S_1 = 1$  and  $S_2 = 0$ .  
Then setting  $S_1 = 0$  and  $S_2 = 1$ ,  $A$  gets held in the feedback loop.

# LATCHES
 
## D LATCH (WITH TG)

- STORING BITS
- STORING A BIT
- FEEDBACK LOOPS
- LOADING A BIT

- The previous example is a data latch (**D latch**) if both  $S_1$  and  $S_2$  are controlled by a single line **C** as follows.



Note: The latch is level-sensitive.

If **D** changes while **C** = 1, then **Q** will change as well.


- The control line **C** might be derived from the **clock signal**, or a signal from the **controller/sequencer** in the microprocessor.

# LATCHES
 
## $\bar{S}\bar{R}$ LATCH (NAND GATES)

- LATCHES
  - D LATCH (WITH TG)
  - NAND PRIMITIVES
  - CONSTRUCTING A LATCH

- NAND gates can also be used to create a latch, this time an  $\bar{S}\bar{R}$  latch.



S	R	Q	$\bar{Q}$	
1	0	0	1	
1	1	0	1	(after S = 1, R = 0)
0	1	1	0	
1	1	1	0	(after S = 0, R = 1)
0	0	1	1	

Recall:		
A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

- Notice that this latch is level-sensitive.




# LATCHES
 
## SR LATCH (NOR GATES)

- LATCHES
  - CONSTRUCTING A LATCH
  - S'R' LATCH - NAND GATES
  - MIXED LOGIC EQUIV.

- The SR latch also uses feedback to “store” a bit.



S	R	Q	$\bar{Q}$	
1	0	1	0	
0	0	1	0	(after S = 1, R = 0)
0	1	0	1	
0	0	0	1	(after S = 0, R = 1)
1	1	0	0	


Recall:		
A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- Notice that this latch is level-sensitive.

# LATCHES
 
## SR LATCH WITH CONTROL

- A control line can be added to the  $\bar{S}\bar{R}$  latch as follows forming an SR latch




- This control line makes it possible to decide when the inputs **S** and **R** are allowed to change the state of the latch.

# LATCHES
 
## D LATCH (WITH $\bar{S}\bar{R}$ LATCH)

- LATCHES
  - MIXED LOGIC EQUIV.
  - SR LATCH - NOR GATES
  - SR LATCH W/ CONTROL

- A D latch can be implemented using what is effectively the SR latch with a control line as follows.




- Note that as long as **C** = 1, that the latch will change according to the value of **D**.

# LATCHES
 
## TIMING DIAGRAMS

- LATCHES
  - SR LATCH -NOR GATES
  - SR LATCH W/ CONTROL
  - D LATCH

- Timing diagrams allow you to see how a sequential system changes with time using different inputs.
- For instance, a timing diagram for a **D latch** might look like the following.




# LATCHES
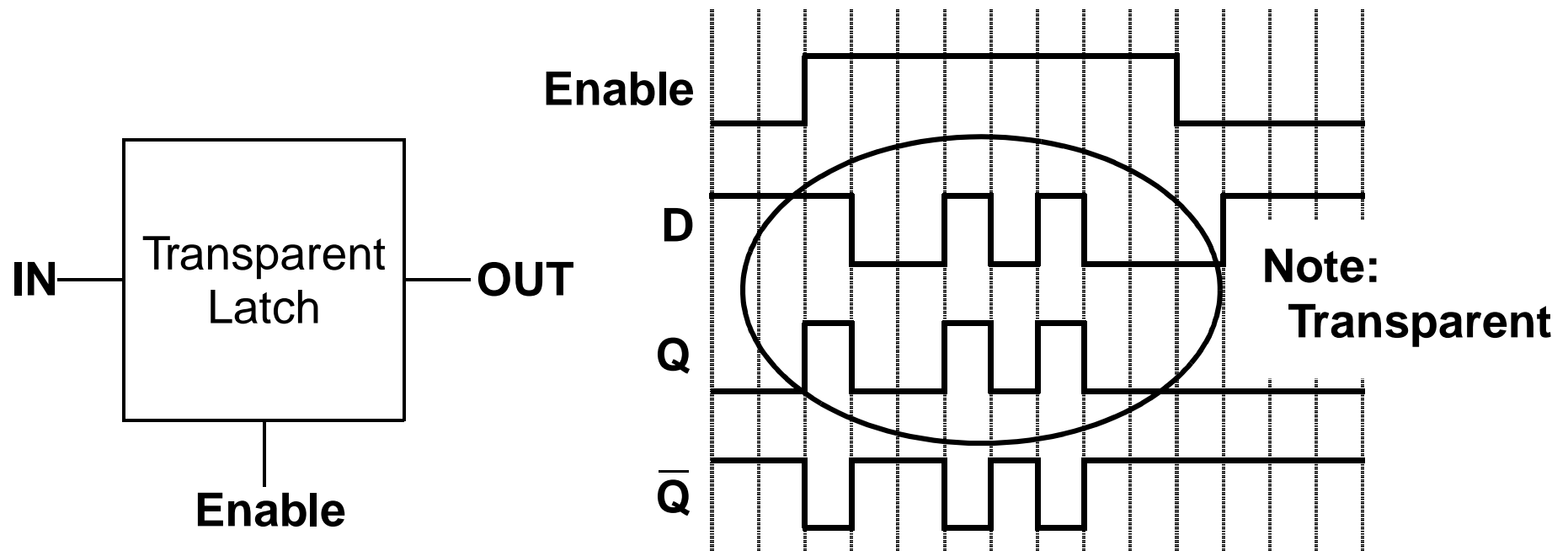
## TRANSPARENCY (1)

- LATCHES
  - SR LATCH W/ CONTROL
  - D LATCH
  - TIMING DIAGRAMS


- Latches like the D latch are termed “transparent” or **level-sensitive**.
  - This is because, when enabled, the **output follows the input**.



# LATCHES
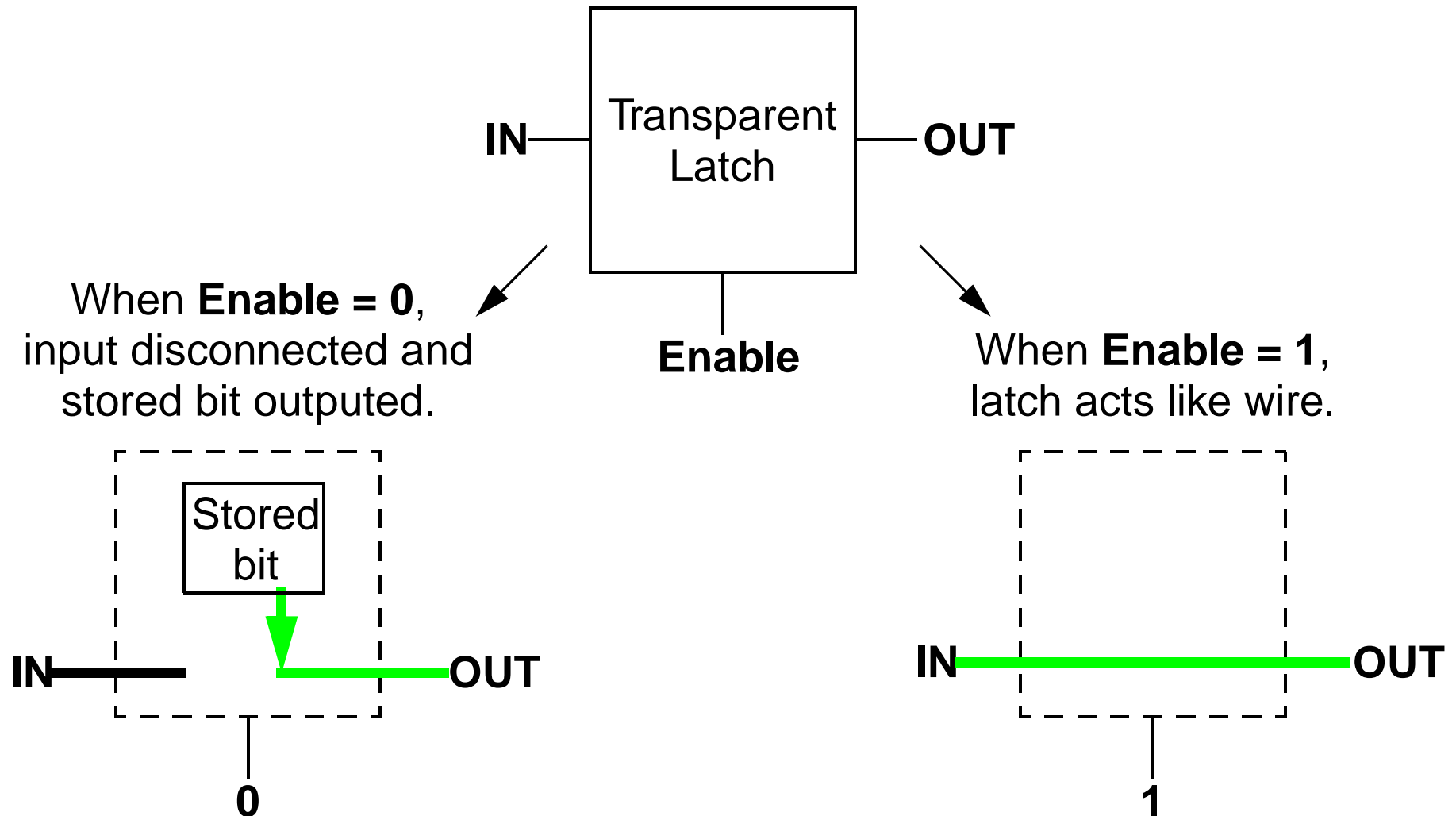
## TRANSPARENCY (2)

- The following behaviour is observed for Enable = 0 and Enable = 1.




# LATCH EXAMPLE
 
## PROBLEMS W/ TRANSPARENCY

- LATCHES
  - D LATCH
  - TIMING DIAGRAMS
  - TRANSPARENCY

- A problem with latches is that they are level-sensitive.
  - A momentary change of input changes the value passed out of the latch.
- This is a problem if the input of a latch depends on the output of the same latch.
  - Example: Design a system that flips a stored bit whenever **Enable** goes high. An inexperienced engineer might design the following.



How will this design behave?


Will the bit flip once when the **Enable** signal goes high?

Answer: The output will follow the input, which happens to keep changing.


# LATCH EXAMPLE

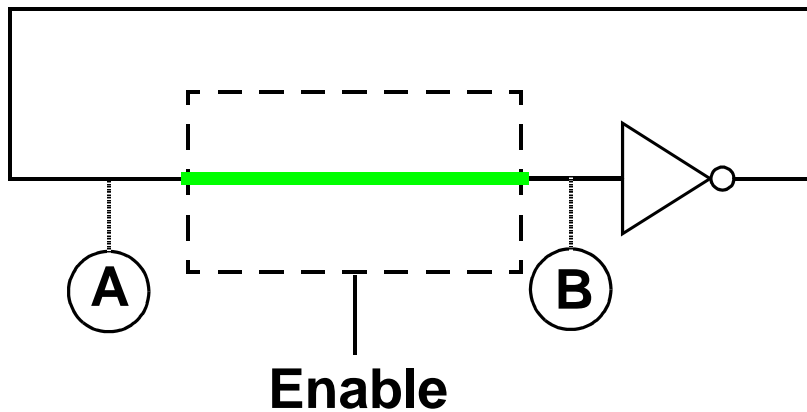PROBLEMS W/ TRANSPARENCY

- Let's analyze the timing behaviour of this "poor" design.



 - Notice that instead of the desired bit flip when **Enable=1**, that the input oscillates. This is because the output depends directly on the input since **A** and **B** appear to be connected by a wire.






# LATCH EXAMPLE
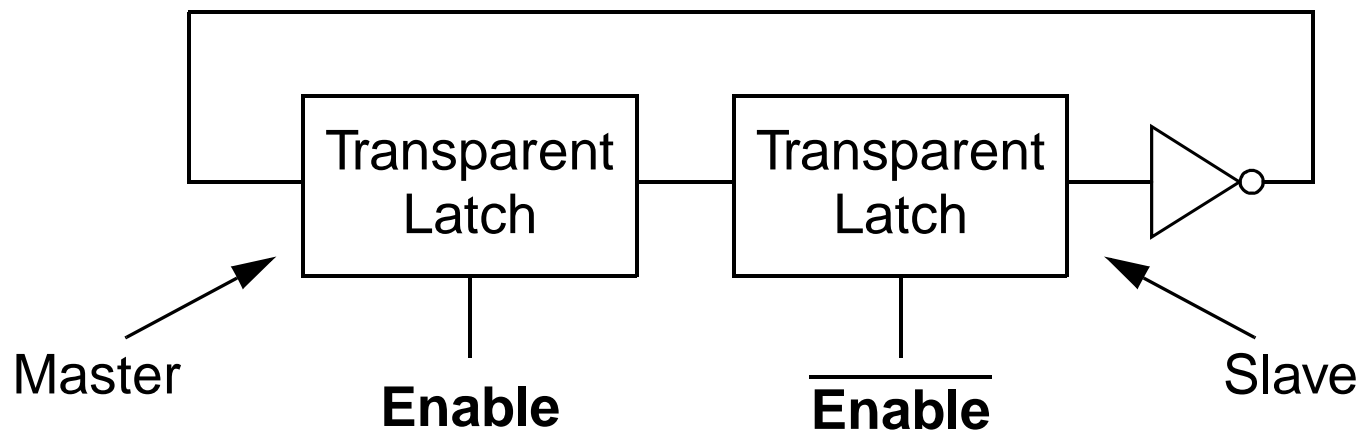
## ELIMINATING TRANSPARENCY

- The problem with transparent, level-sensitive latches can be fixed by splitting the input and output so that they are independent.
- New solution: Consider the following improved design that flips a stored bit whenever **Enable** goes high. This design now uses a master and a slave transparent latches to separate the input from the output.





# LATCH EXAMPLE
 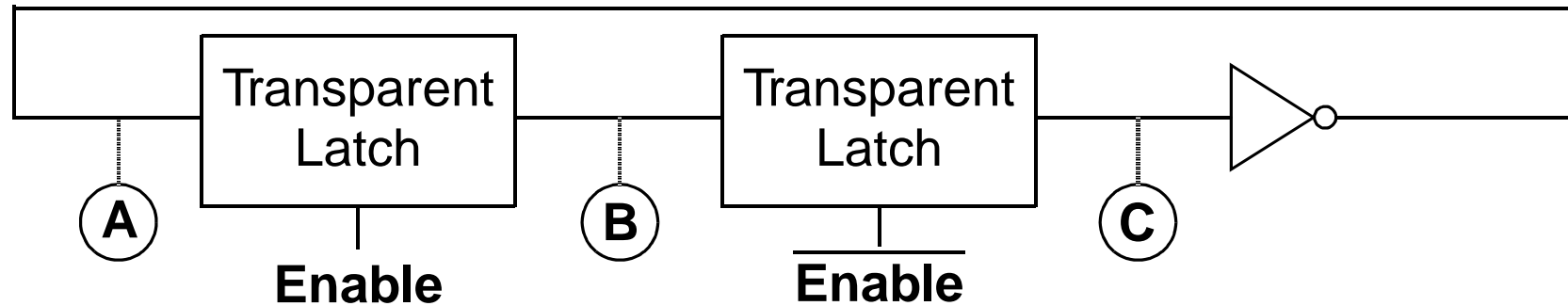
## TIMING DIAGRAM

- LATCHES
- LATCH EXAMPLE
  - PROB W/TRANSPARENCY
  - ELIMIN. TRANSPARENCY

- Let's analyze the timing behaviour of this improved design.




# LATCH EXAMPLE

## LATCH BEHAVIOUR


- LATCH EXAMPLE
- PROB W/TRANSPARENCY
- ELIMIN. TRANSPARENCY
- TIMING DIAGRAM

- The behaviour of the master and the slave transparent latches can be thought of as follows.

**Enable = 1**

 


**Enable = 0**

 

# FLIP-FLOPS
 
## SINGLE BIT STORAGE

- A flip-flop is a single bit storage unit with two stages (master/slave):
  - First stage, or master, to accept input (flip)
  - Second stage, or slave, to give output as received by the first stage (flop)




- A number of different types of flip-flops exist such as the SR,  $\bar{S}\bar{R}$ , D, and JK flip-flops. You may wish to review Chapter 4 regarding these types.


# FLIP-FLOPS
 
## EDGE TRIGGERED

- A common and useful type of flip-flop are edge triggered flip-flops.
  - Positive edge triggered flip-flops



- Negative edge triggered flip-flops

 


# FLIP-FLOPS
 
## NEGATIVE EDGE TRIGGERED

- LATCH EXAMPLE
- FLIP-FLOPS
  - SINGLE BIT STORAGE
  - EDGE TRIGGERED

- The output C, which is also the bit stored, appears to change on the negative edge of the Enable transitions.




# FLIP-FLOPS
 
## POSITIVE EDGE TRIGGERED

- FLIP-FLOPS
  - SINGLE BIT STORAGE
  - EDGE TRIGGERED
  - NEG. EDGE TRIGGERED

- The output C, which is also the bit stored, appears to change on the positive edge of the Enable transitions.




# FLIP-FLOPS
 
## NON-IDEAL W/ DUAL-PHASE

- FLIP-FLOPS
  - EDGE TRIGGERED
  - NEG. EDGE TRIGGERED
  - POS. EDGE TRIGGERED

- The previous timing diagrams are in an ideal case. In reality, an implementation with delays might have the following timing diagram.



Propagation delays shift the outputs and slew transitions


- Notice that **Enable/Enable** are replaced with  $\phi_1/\phi_2$ , which are **non-overlapping** phases (normally generated from a dual-phase clock).



# FLIP-FLOPS
 
## DUAL-PHASE ENABLE

- Why use non-overlapping, dual-phase signals for the latch enable?
  - What happens if the latch enable input flip simultaneously?
  - How about if propagation delays cause one latch to change enable state slightly before the other?
  - The goal is to ensure that the **master latch has latched** the input **before the slave** latch tries takes this bit from the master.




- If the master has not latched, the slave sees the input transparently!!!
- A non-overlapping, dual-phase enable solves this problem.

# REGISTERS
 
## REGISTERS FROM FLIP-FLOPS

- FLIP-FLOPS
  - POS. EDGE TRIGGERED
  - NON-IDEAL W/DUAL- $\phi$
  - DUAL-PHASE ENABLE


- In essence, a flip-flop is a 1-bit register.
- An n-bit register can be formed by groupign n flip-flops together.



# REGISTERS
 
## READ/WRITE CONTROL (1)

- When a clock is used, such as the non-overlapping, dual-phase clock  $\phi_1$  and  $\phi_2$ , we want control over when a new value is written into a register (instead of writing a new value every clock cycle).
- A read/write control is therefore required.
- One “poor” design might be as follows for a 1-bit register.




- What is the problem with this design?

# REGISTERS

## READ/WRITE CONTROL (2)

- A better design might be as follows

 


- When Read/Write = **0**, the output is feed back into the master latch.
- When Read/Write = **1**, the input is feed into the master latch.

# REGISTERS
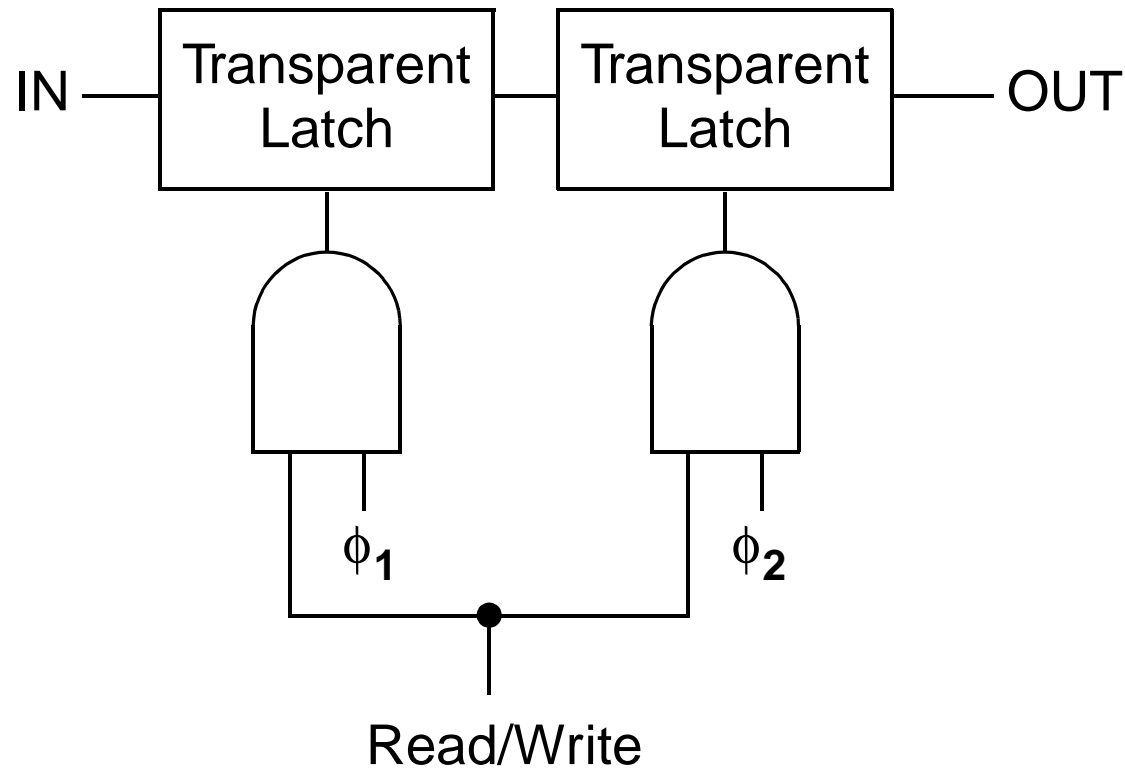
## READ/WRITE CONTROL (3)

- A different design approach might be as follows



- What problems might exist with this design?
  - One issue might be that both latch enables are **0** when  $R/W = 0$ .