

CHAPTER IX

REGISTER BLOCKS COUNTERS, SHIFT, AND ROTATE REGISTERS

READ PAGES 249-275 FROM MANO AND KIME


- Like combinational building blocks, we can also develop some simple building blocks using registers. These include:
 - Shift registers
 - Rotate registers
 - Counters
- Implementations of these components can use state machines, but, it is often easier to think of them without the complication of a state machine.

SHIFT REGISTERS


INTRODUCTION

- Logical shift registers take the bits stored and move them up a significant bit or down a significant bit.


LOGICAL SHIFT RIGHT (LSR)

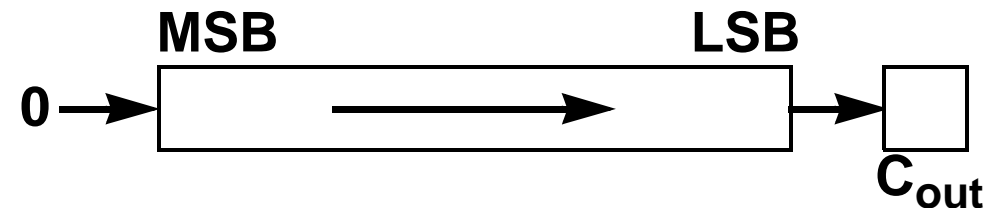


ARITHMETIC SHIFT RIGHT (ASR)

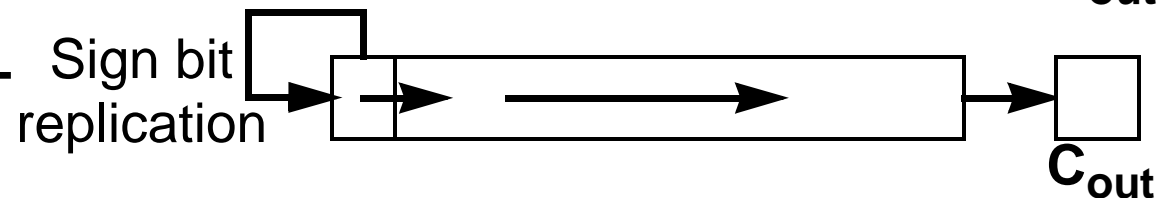

LOGICAL SHIFT LEFT (LSL)

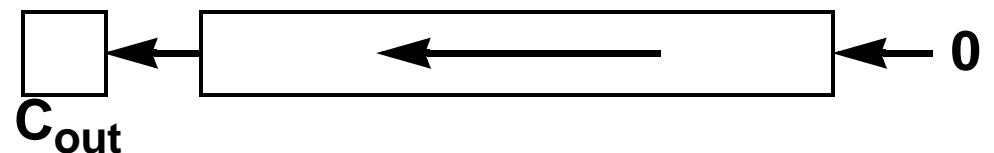

ARITHMETIC SHIFT LEFT (ASL)

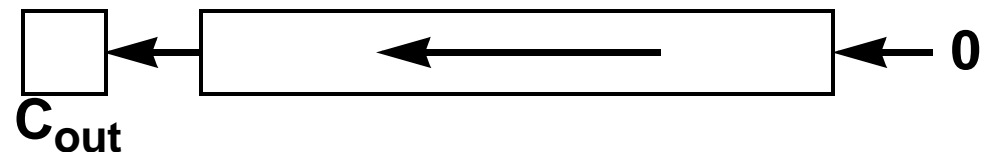


- Notice that logical and arithmetic shift lefts are the same.

SHIFT REGISTERS

LSR SAMPLE

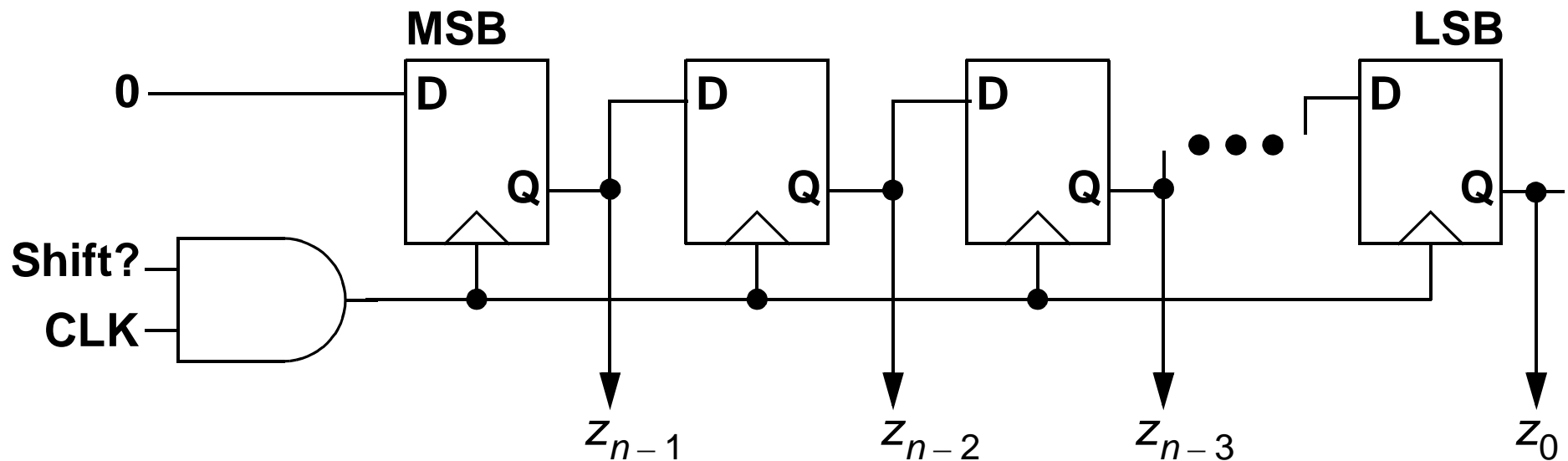
- A simple implementation of a logical right shift register might look like the following.



SHIFT REGISTERS

ASR SAMPLE

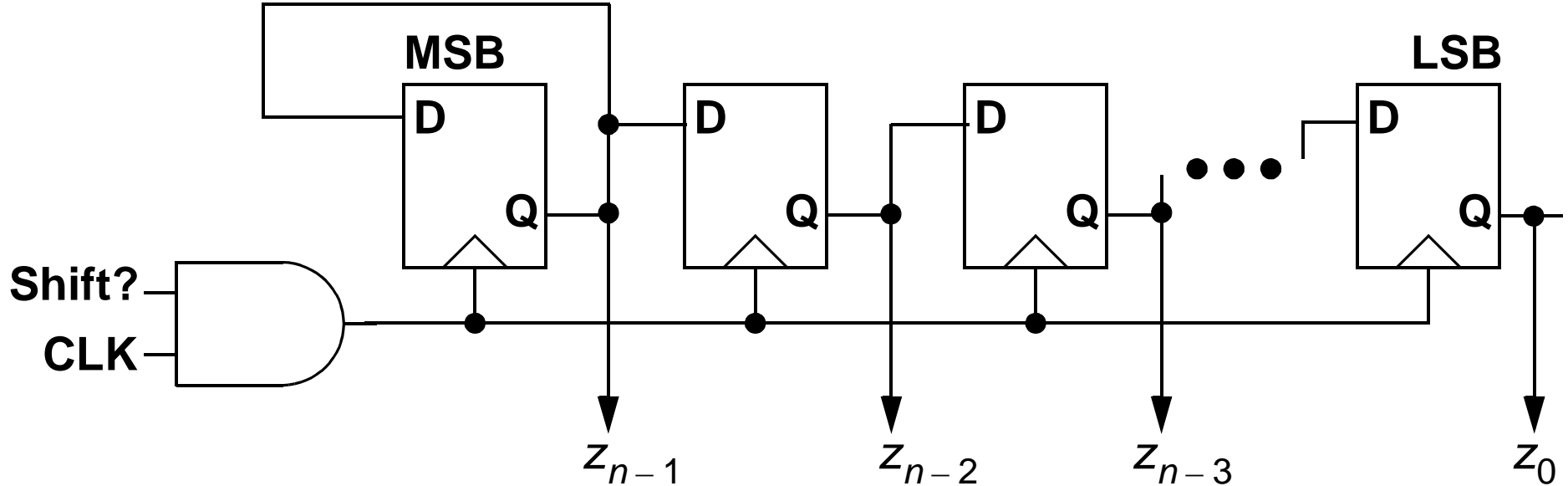
- An arithmetic right shift register might look like the following.



SHIFT REGISTERS

4-BIT BIDIRECTIONAL

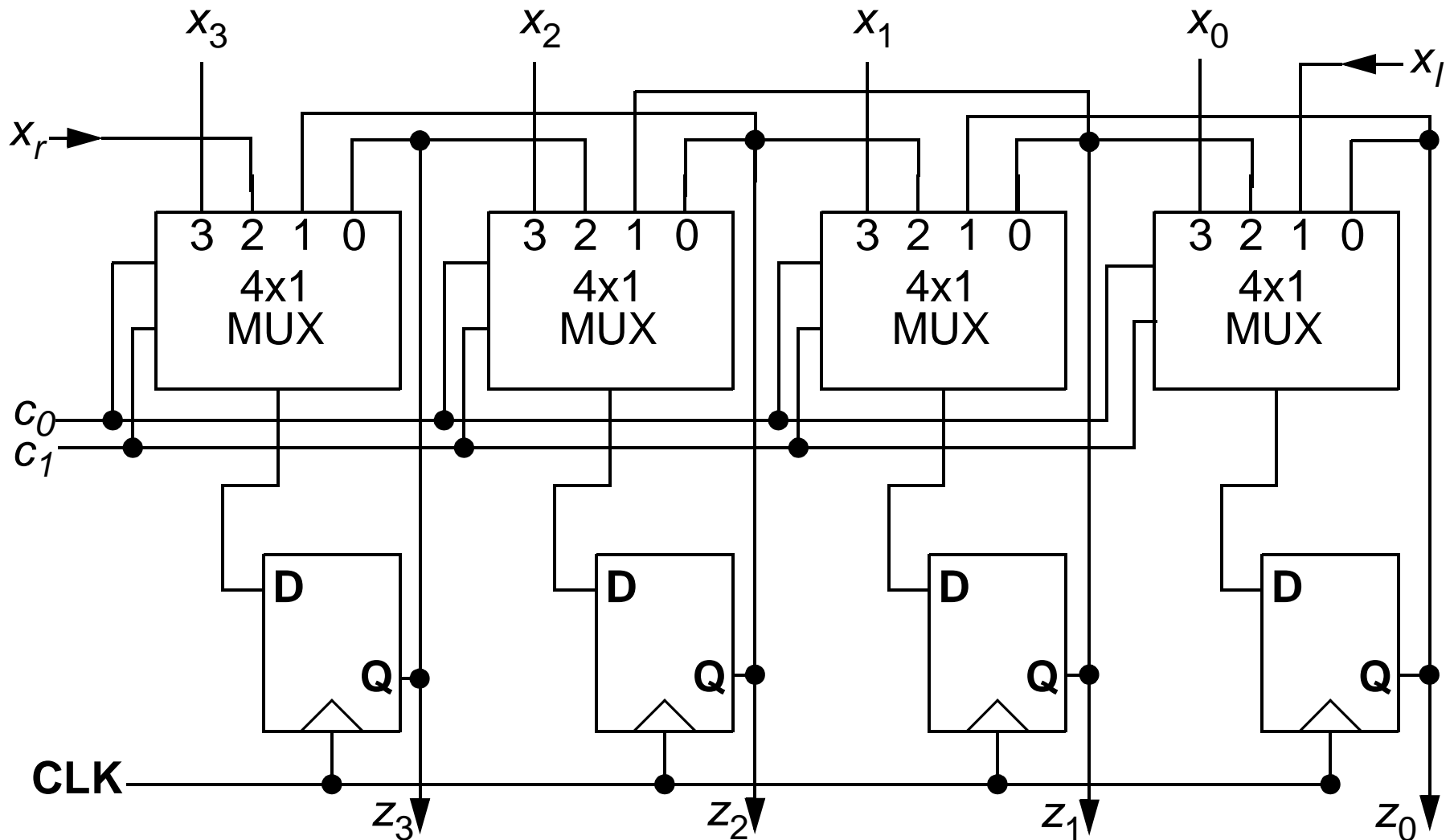
- The following is a 4-bit bidirectional shift register with parallel load.



SHIFT REGISTERS

CASCADING (1)

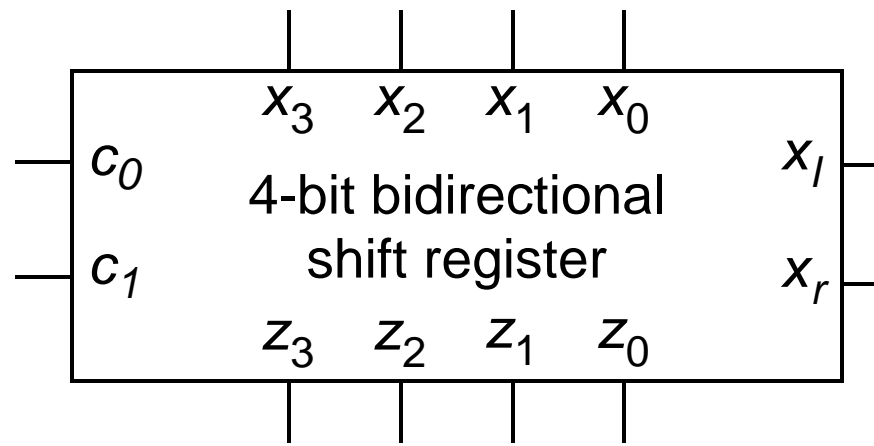
- Cascading of shift registers can also be done if the discarded bit is used to shift into another shift register module.
- For instance, the 4-bit bidirectional shift register previously presented can be easily cascaded using the
 - x_r (right shift data input) and
 - x_l (left shift data input)



SHIFT REGISTERS

CASCADING (2)

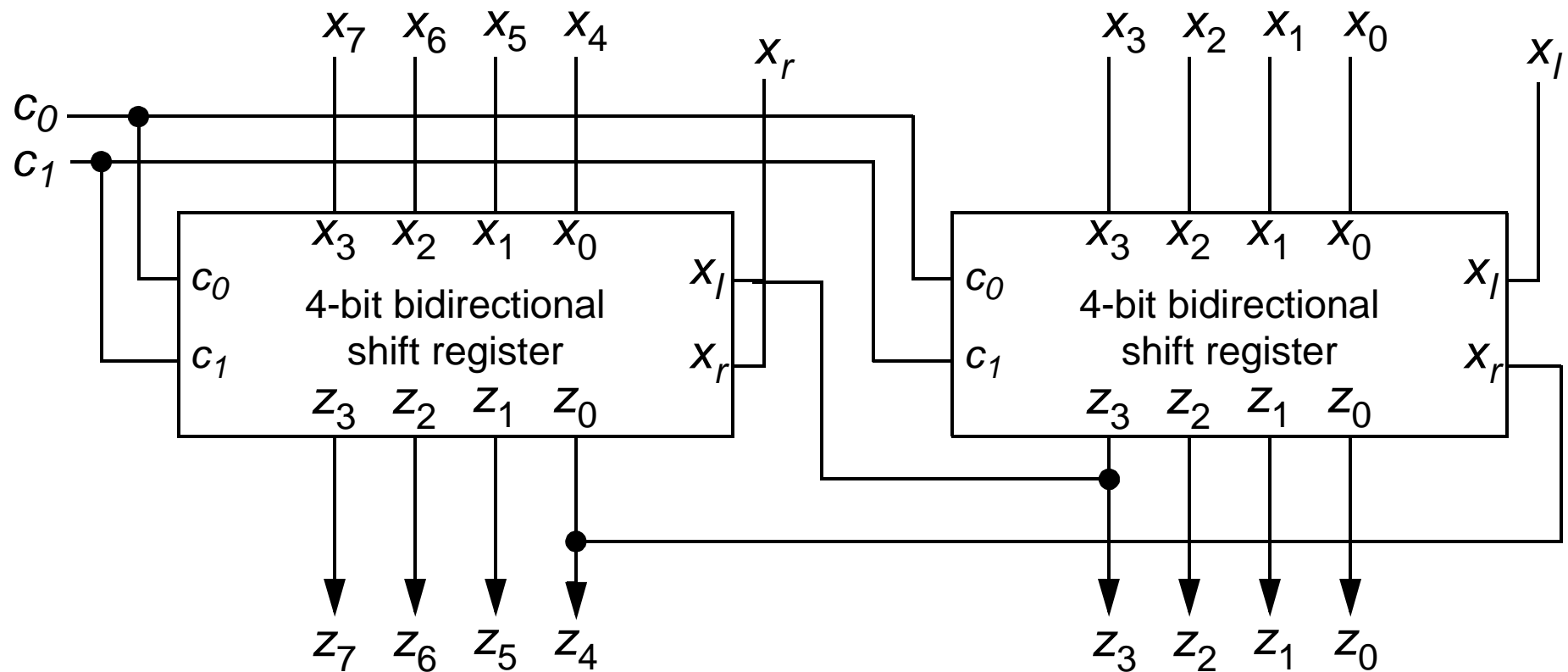
- For example, an 8-bit bidirectional shift register with parallel load can be formed as follows.



ROTATE REGISTERS

INTRODUCTION

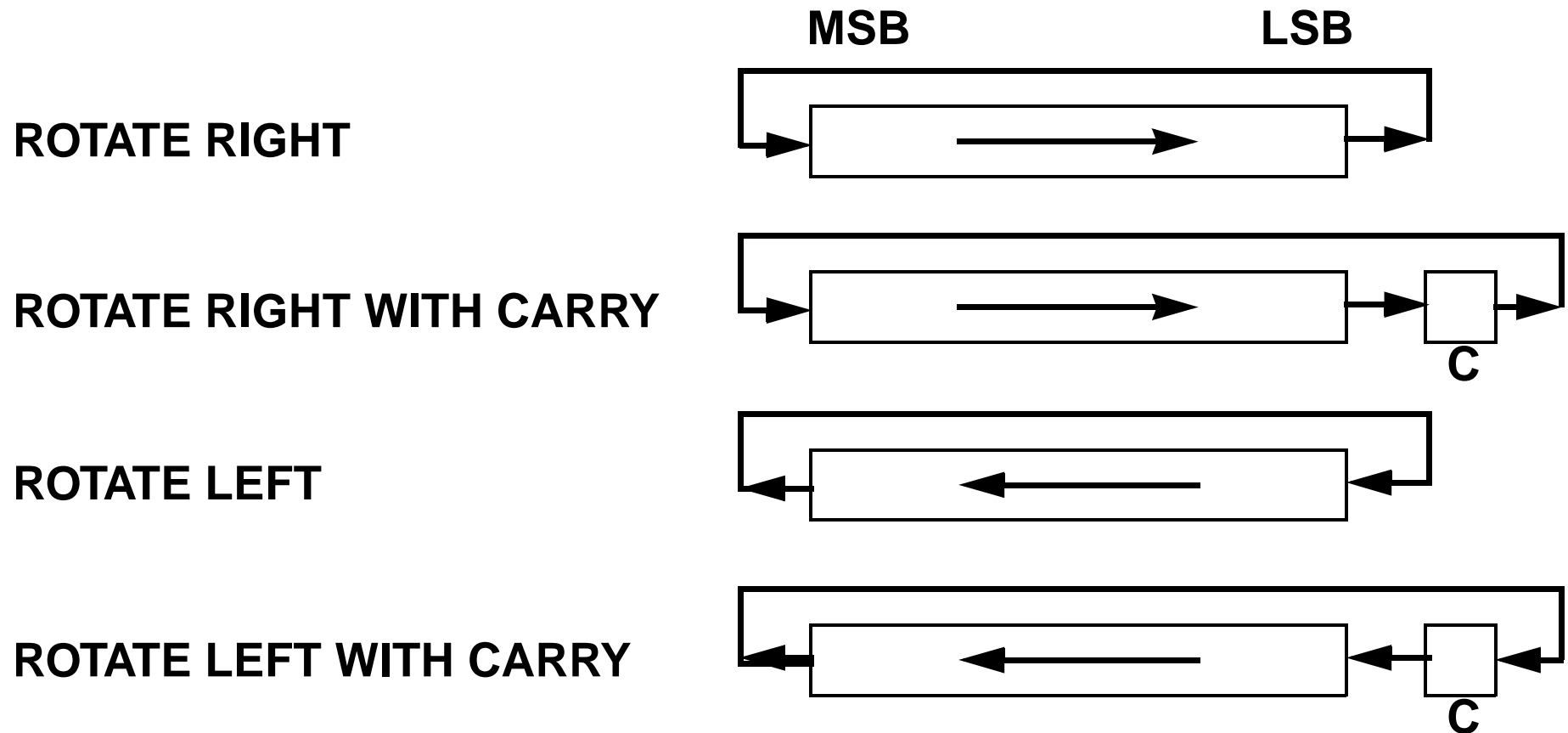
- A rotate register is the same as a logical shift register except that the discarded bit is fed back into the empty space from the shift.



ROTATE REGISTERS

USING SHIFT REGISTERS

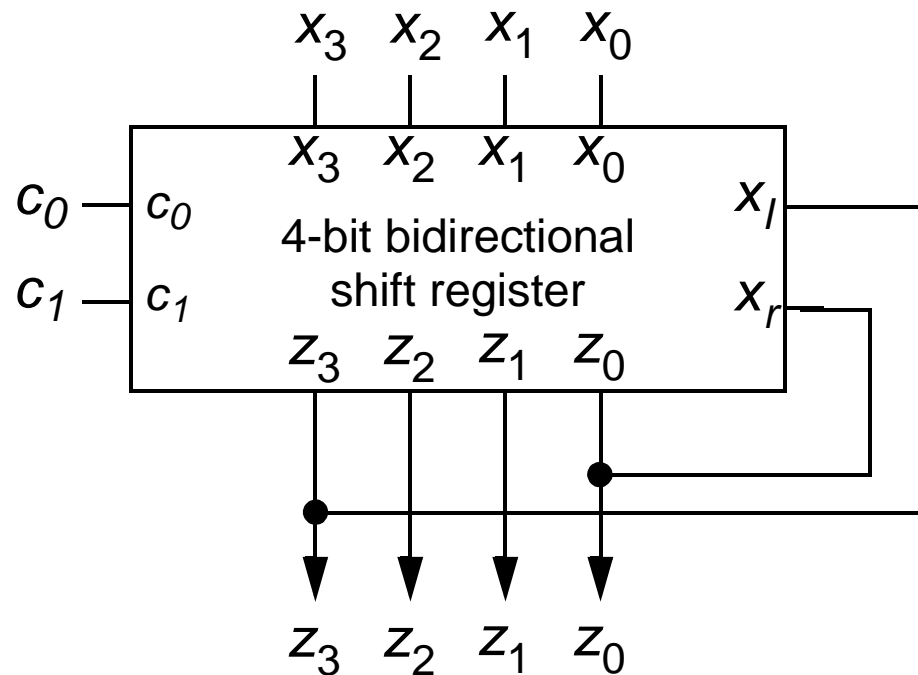- Rotate registers can actually be implemented using shift registers that have serial data inputs (such as the 4-bit bidirectional shift register discussed).
- For example, a 4-bit rotate register can be formed as follows.



- A counter is a register that on each clock pulse counts up or down, usually in binary.
- Types of counters
 - ripple counters
 - synchronous counters
 - binary counters
 - BCD counters
 - Gray-code counters
 - Ring counters (a 1 moves in a ring from one flip-flop to the next)
 - up/down counters (ability to increment or decrement)
 - counters with a parallel load (load in starting value with parallel input)


COUNTERS

MODULO- P COUNTERS

- A modulo- p counter is defined by the following equation.

$$S(t + 1) = (S(t) + x) \text{ mod } p$$

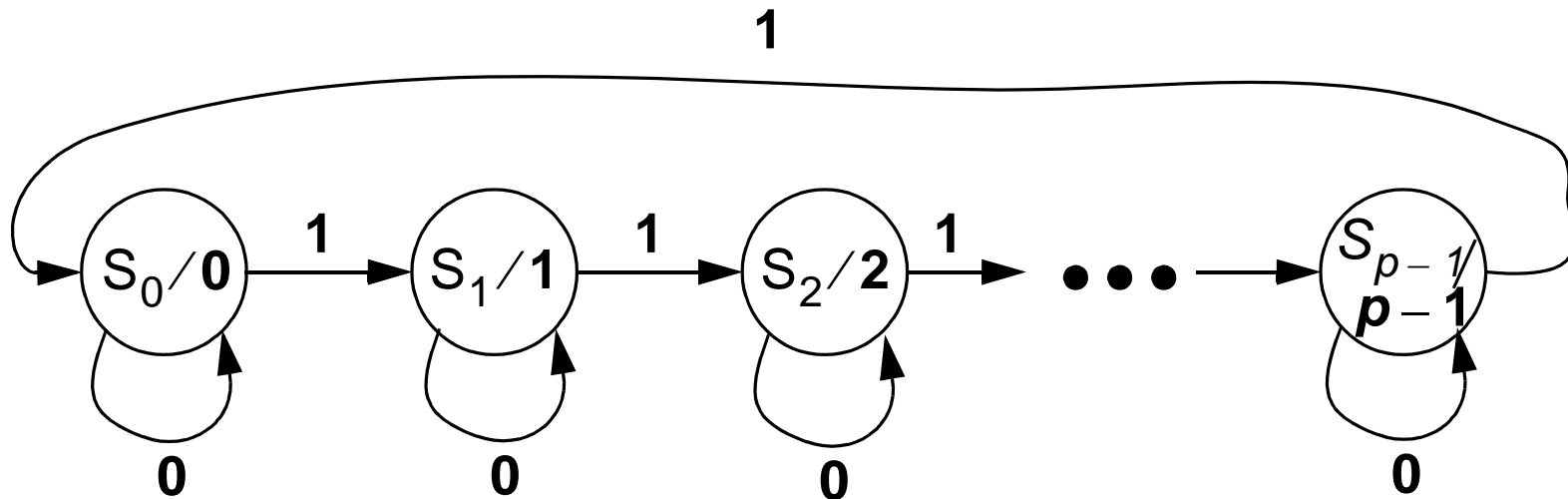- The state diagram for the modulo- p counter is as follows.




- An n -bit binary counter consists of n flip-flops and can count in binary from 0 through $2^n - 1$.
- This can be formed with a modulo- p counter where $p = 2^n$.
- Two main categories exist for counters:
 - Ripple counters
 - One flip-flop transition serves to trigger other flip-flops.
 - The clock pulse is usually only sent to the first flip-flop.
 - This requires a memory cell that can complement its value.
 - The JK flip-flop would be one approach (we have not studied this!)
 - Synchronous counters
 - Change of state is determined from the present state.
 - Clock pulse sent to all flip-flops.


COUNTERS

TOGGLE CELL

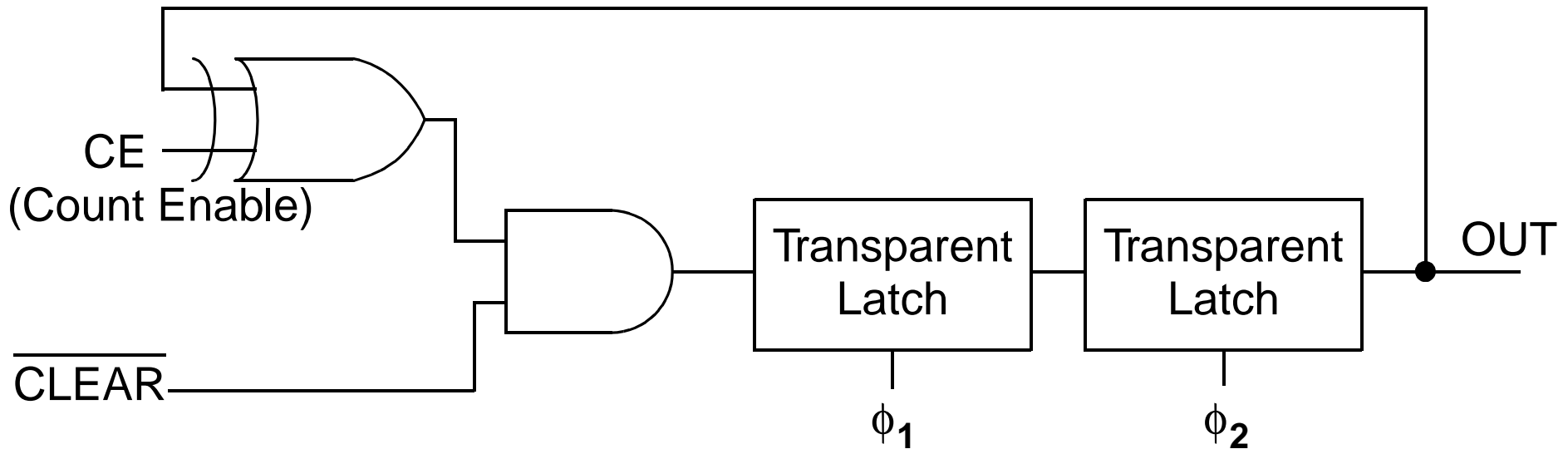- A toggle cell will be useful for implementing counters.




Present Latch Value	CE	$\overline{\text{CLEAR}}$	Next Latch Value	OUT
X	X	0	0	?
0	0	1	0	0
1	0	1	1	1
0	1	1	1	0
1	1	1	0	1

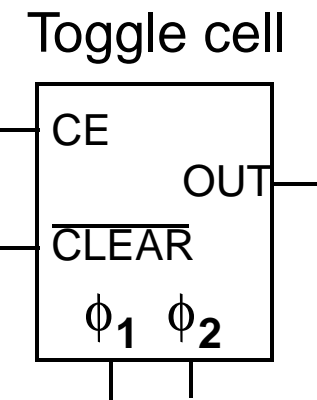

COUNTERS

RIPPLE COUNTER

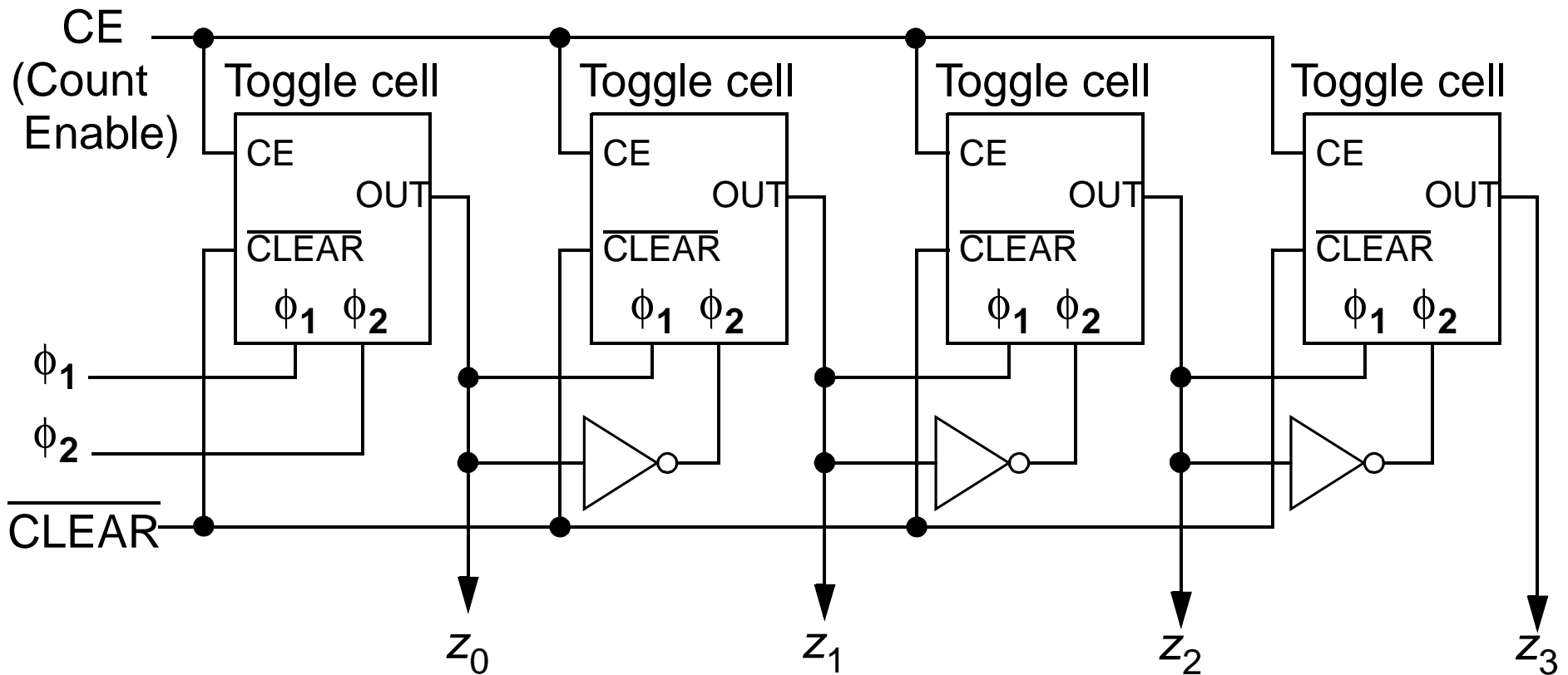- The toggle cell can be used as follows to form a ripple counter.




- Notice that the previous toggle cell is connected to the clock input of the next cell. This causes the bits to ripple through the counter.

COUNTERS

SYNCHRONOUS COUNTER

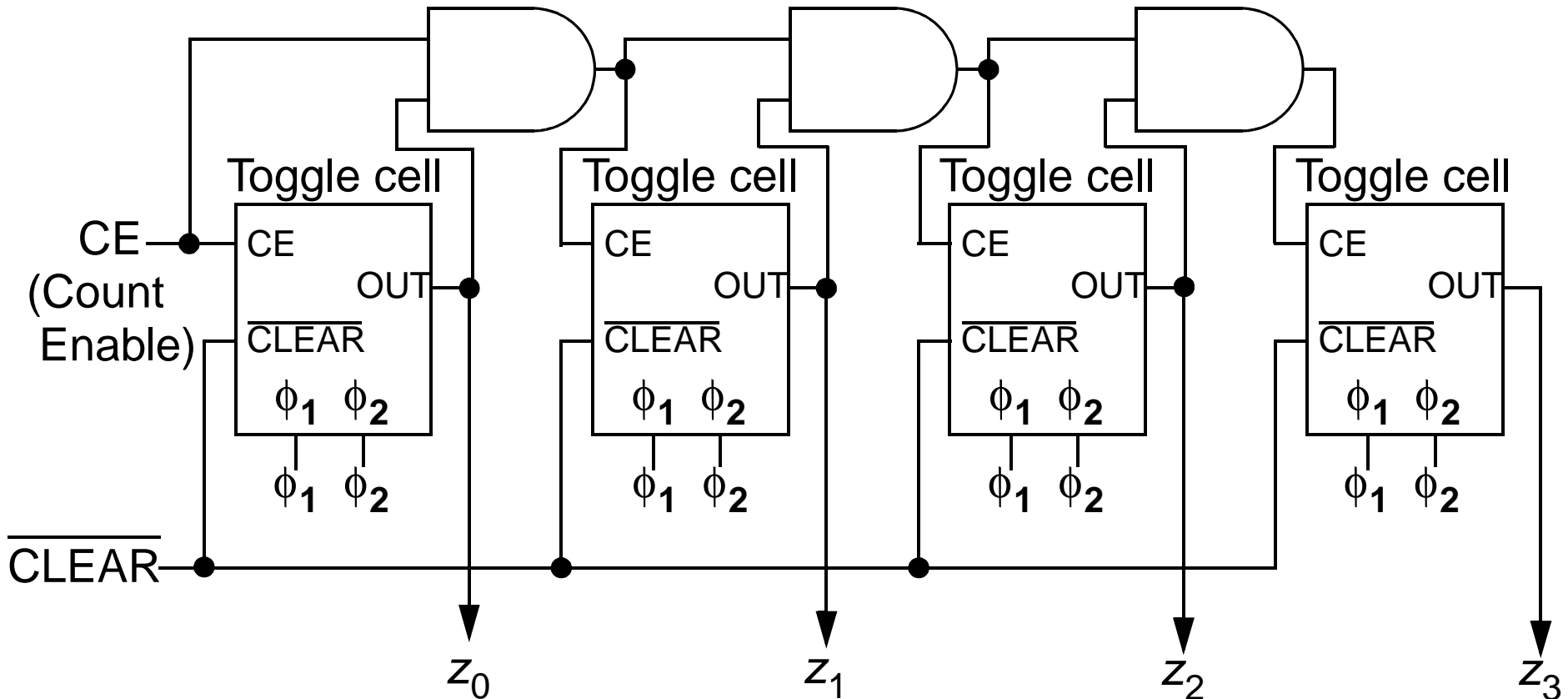- Below is an example 4-bit synchronous counter using toggle cells.




- Notice that clock is sent to all toggle cells.
- A simplified form is in Figure 5-11, pp. 269 of Mano & Kime.

COUNTERS

MORE ON MODULO- P


- Notice that the counters developed so far can count from 0 to $2^n - 1$ for n toggle cells.
- Therefore, for module- p counting, the p is currently limited to 2^n .
- How about if we wish p to be a non-power of 2?
- Need to build what can be referred to as a divide by counter.
- Given the following counter block, a general modulo- p counter can be constructed by clearing the counter after the desired maximum value.

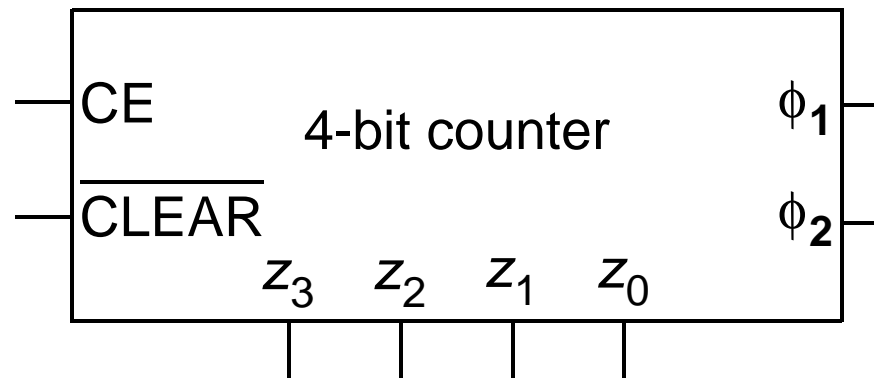

COUNTERS

BCD COUNTER (MODULO-10)

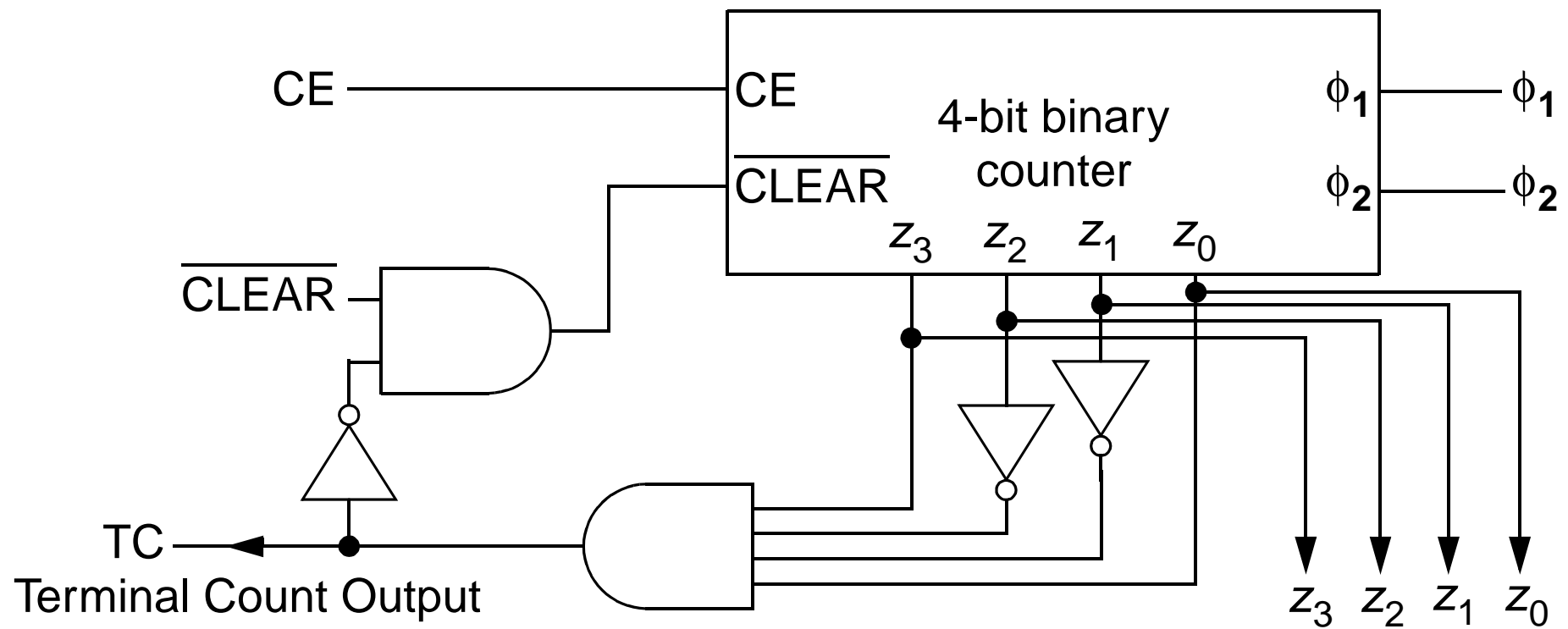- To illustrate general modulo- p counters, consider the following implementation of a single digit decimal counter using BCD.




- Notice that the counter is cleared after a value of 9 (**1001**).

COUNTERS

TERMINAL COUNT (TC)

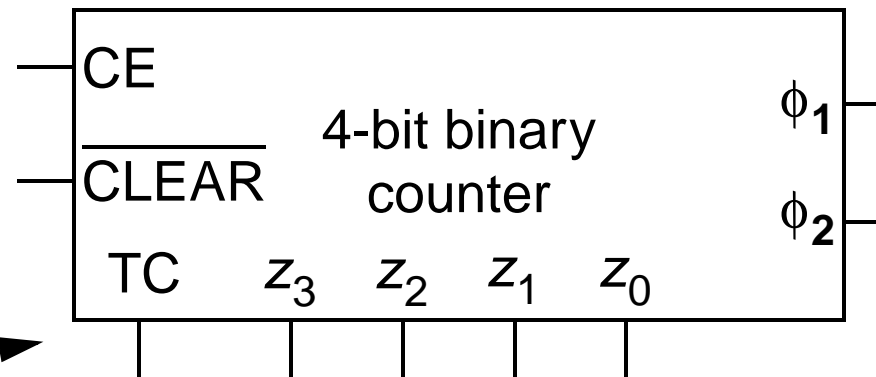- The previous BCD counter was built by deriving a terminal count (TC) output signal.
- A terminal count output signal for any counter can be useful, so, we will be included in general block diagram for a binary counter.



Notice TC output

- In this 4-bit binary counter example, TC=1 only when the output is **1111**.

COUNTERS

CASCADING COUNTERS

- With a terminal count output (TC), counters can be easily cascaded together to form larger counters.
- For instance, an 8-bit binary counter can be formed as follows.

