 


Bring this homework to class on Wednesday March 3.

HW-7. Finite State Machine - Circuit Design

Design the logic to implement the following FSM. This is the state diagram for a Mealy machine with 3 states that outputs a "1" on every third "1" received as input, no matter how many "0"s are intermingled. For example:

Input: 010110100101110110110
 Output: 000010000001000100010



This is the truth table for the logic that is needed. P1,P0 is the present state, Number the states such that 2*P1 + P0 is the number of 1's seen in the present sequence of 3. N1,N0 the next state.

P1	P0	Input	N1	N0	Output
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	0	0	1