



Chapter Six- 1st Half Pipelined Processor Delayed Controls, Hazards

EE3055
Web: www.csc.gatech.edu/copeland/jac/3055-05

1

Pipelining

  - Improve performance by increasing instruction throughput



Ideal speedup is number of stages in the pipeline. Do we achieve this?


2

Pipelining

- What makes it easy
 - all instructions are the same length
 - just a few instruction formats
 - memory operands appear only in loads and stores
- What makes it hard?
 - structural hazards: suppose we had only one memory
 - control hazards: need to worry about branch instructions
 - data hazards: an instruction depends on a previous instruction
- We'll build a simple pipeline and look at these issues
- We'll talk about modern processors and what really makes it hard:
 - exception handling
 - trying to improve performance with out-of-order execution, etc.

3


Basic Idea

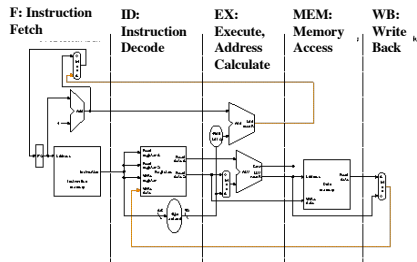

- What do we need to add to actually split the datapath into stages?

4

Pipelined Datapath

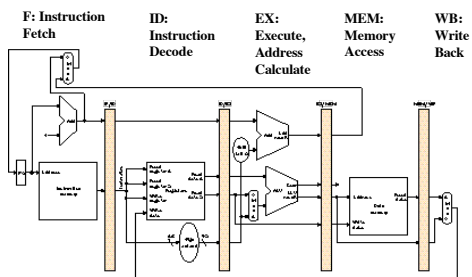

- Can you find a problem even if there are no dependencies?
- What instructions can we execute to manifest the problem?

5

Corrected Datapath


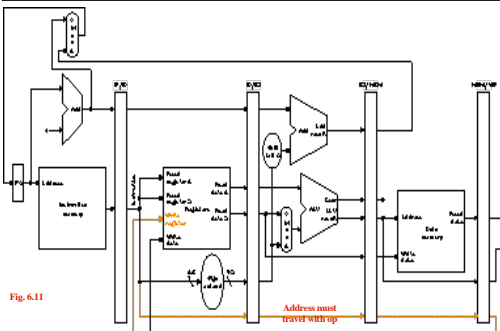


Fig. 6.11

6


Graphically Representing Pipelines

 

- Can help with answering questions like:
 - how many cycles does it take to execute this code?
 - what is the ALU doing during cycle 4?
 - use this representation to help understand datapaths

7

Pipeline Control

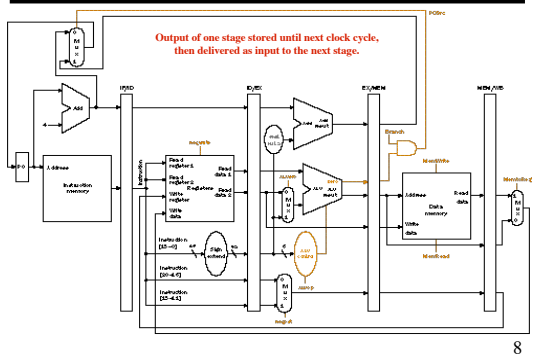

8

Pipeline control


- We have 5 stages. What needs to be controlled in each stage?
 - Instruction Fetch and PC Increment
 - Instruction Decode / Register Fetch
 - Execution
 - Memory Stage
 - Write Back
- How would control be handled in an automobile plant?
 - a fancy control center telling everyone what to do?
 - should we use a finite state machine?

9

Pipeline Control


- Pass control signals along just like the data

Instruction	Execution/Address Calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Branch	Mem Read	Mem Write	Reg write	Mem to Reg
R-format	1	1	0	0	0	0	0	1	0
lwr	0	0	0	1	0	1	0	1	1
lwl	X	0	0	1	0	0	1	0	X
swr	X	0	1	0	1	0	0	0	X

 

10


Datapath with Control

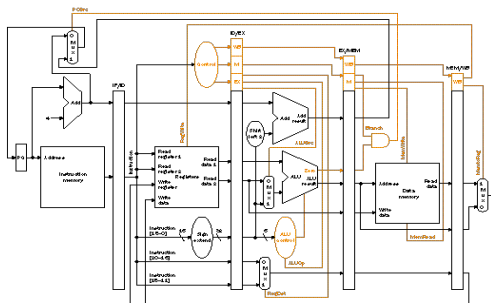

11

Dependencies

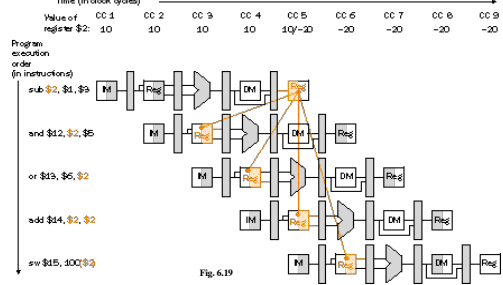- Problem with starting next instruction before first is finished
- dependencies that "go backward in time" are data hazards



12

Software Solution

- Have compiler guarantee no hazards
- Where do we insert the "nops" ?

```
sub    $2, $1, $3
and    $12, $2, $5
or     $13, $6, $2
add    $14, $2, $2
sw     $15, 100($2)
```

- Problem: this really slows us down!
- Hardware solutions - next set of slides.
