
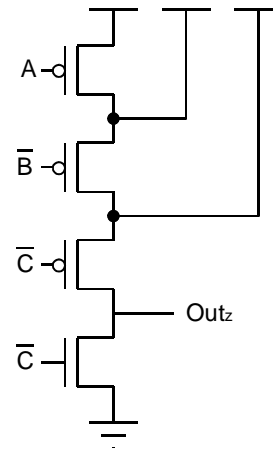
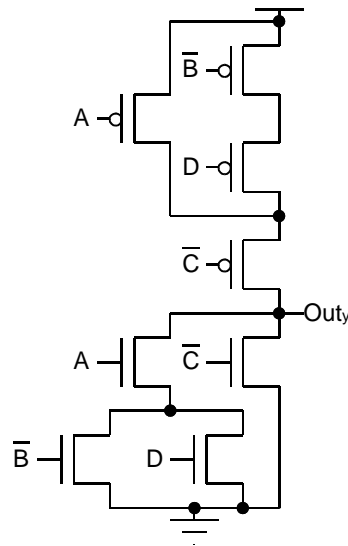


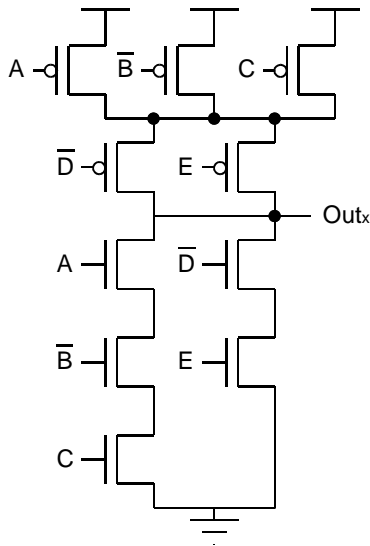Problem 1 (3 parts, 30 points)

Incomplete Circuits

For each partial switch circuit below, complete the complementary switching network so the circuit contains no floats or short. Also write the Boolean expression computed by the completed circuit. Assume the inputs and their complements are available.



$$OUT_x = (\bar{A} + B + \bar{C}) \cdot (D + \bar{E})$$

$$OUT_y = (\bar{A} + B \cdot \bar{D}) \cdot C$$

$$OUT_z = C$$

Problem 2 (1 part, 18 points)

Switch-Ready Expressions

Transform each of the following Boolean expressions to a form where they are ready for switch level implementation (i.e., there should only be bars over input variables, not over operations). The behavior of the expression should remain unchanged. **Do not implement.**

$$Out_x = \overline{A \cdot \overline{B} + C} + \overline{D}$$

$$((\overline{A} + B) \circ \overline{C}) + \overline{D} = (\overline{A} + B) \circ \overline{C} + \overline{D}$$

$$Out_y = \overline{A + \overline{B} + \overline{C}} \cdot \overline{D}$$

$$(\overline{A} \circ B) + (C + \overline{D}) = \overline{A} \circ B + C + \overline{D}$$

$$Out_z = \overline{\overline{\overline{A} \cdot B} + \overline{C}}$$


$$\overline{A} \circ B \circ C$$

Problem 3 (3 parts, 28 points)

Mixed Logic Design

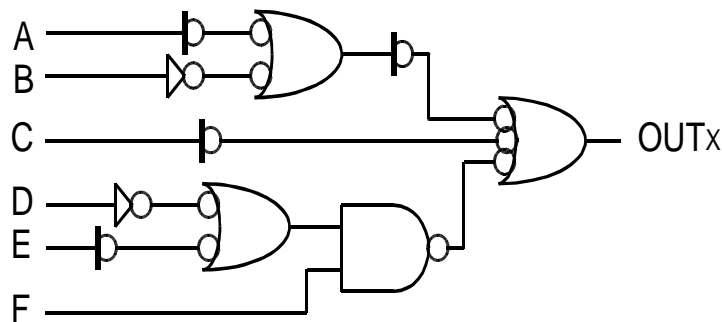Part A (10 points) Implement the following expression using multi-input **NAND** gates and inverters to minimize total transistors (switches) required. Use proper mixed logic design technique. Do not simplify the expression.

$$OUT_x = \overline{\overline{A} + B + \overline{C}} + (D + \overline{E}) \cdot F$$




switches = 22

Problem 4 (2 parts, 24 points)

Karnaugh Maps

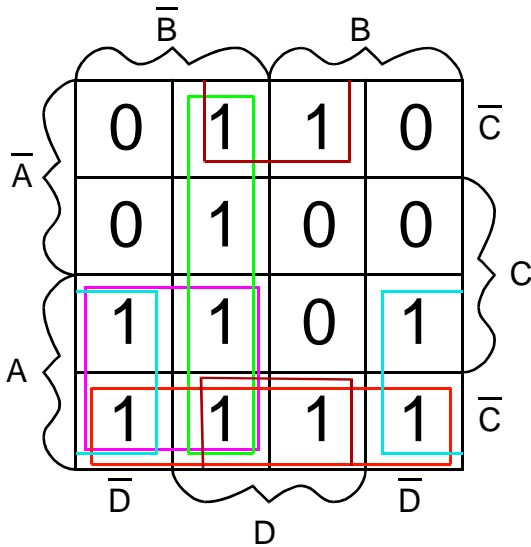Part A (12 points) For the follow expression, derive a simplified *sum of products* expression using a Karnaugh Map. Circle and list the prime implicants, indicating which are essential.

$$Out = (A + D) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C} + \bar{D})$$




prime implicants	essential?	
	yes	no
$A\bar{B}$	<input type="checkbox"/>	<input checked="" type="checkbox"/>
$A\bar{C}$	<input type="checkbox"/>	<input checked="" type="checkbox"/>
$A\bar{D}$	<input checked="" type="checkbox"/>	<input type="checkbox"/>
$\bar{B}D$	<input checked="" type="checkbox"/>	<input type="checkbox"/>
$\bar{C}D$	<input checked="" type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>

simplified **SOP** expression $\bar{B}D + \bar{C}D + A\bar{D}$

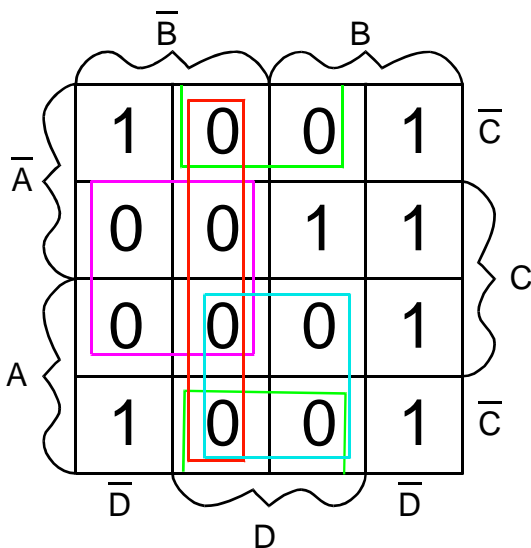Part B (12 points) For the follow expression, derive a simplified *product of sums* expression using a Karnaugh Map. Circle and list the prime implicants, indicating which are essential.

$$Out = \bar{C} \cdot \bar{D} + \bar{A} \cdot B \cdot C + B \cdot C \cdot \bar{D}$$



prime implicants	essential?	
	yes	no
$\bar{A} + \bar{D}$	<input checked="" type="checkbox"/>	<input type="checkbox"/>
$B + \bar{C}$	<input checked="" type="checkbox"/>	<input type="checkbox"/>
$B + \bar{D}$	<input type="checkbox"/>	<input checked="" type="checkbox"/>
$C + \bar{D}$	<input checked="" type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>

simplified **POS** expression $(B + \bar{C}) \cdot (\bar{A} + \bar{D}) \cdot (\bar{D} + C)$