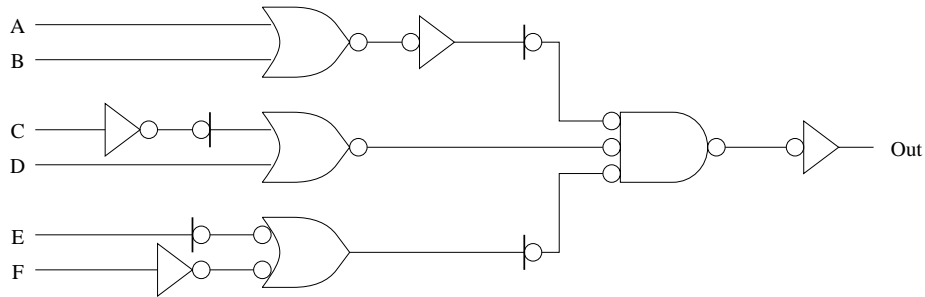



Mixed Logic Understanding

Part A You have obtained the following schematics with no description of their operation. Fortunately, the designer used a mixed logic design strategy.




$F_{(A,B,C,D,E,F)} =$ _____

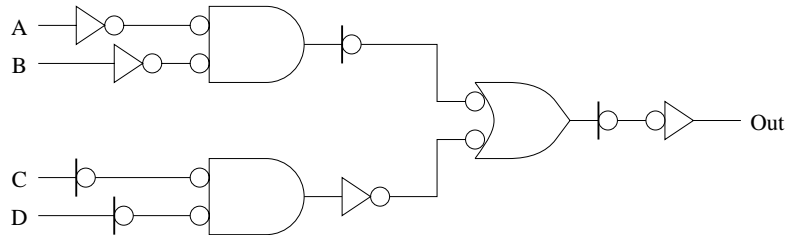Part B Express the function computed by this circuit.



$F_{(A,B,C,D)} =$ _____

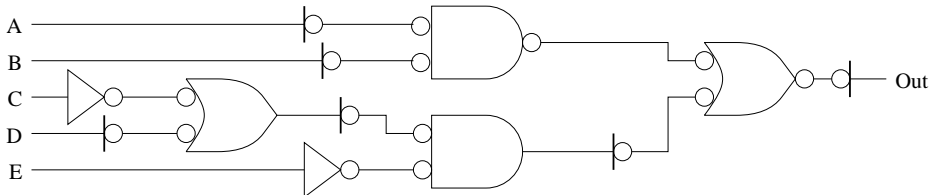Part C Express the function computed by this circuit.



$F_{(A,B,C,D,E)} =$ _____

Part D How many transistors are required for the circuit implementation above?


number of transistors = _____

Part E Now change the implementation to use NAND and NOT gates. Accomplish this only by adding buffers and changing bubble pairs.

Part F How many transistors are required for the new implementation?

number of transistors = _____

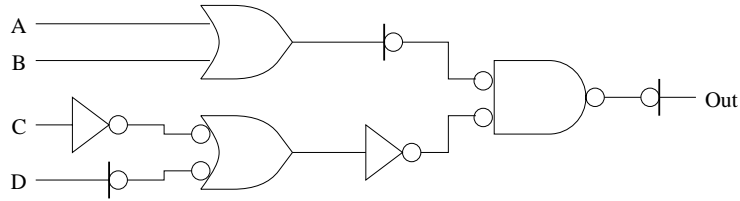Part G Express the function computed by this circuit.



$F_{(A,B,C,D)} =$ _____

Part H How many transistors are required for the circuit implementation above?


number of transistors = _____

Part I Now change the implementation to use NOR and NOT gates. Accomplish this only by adding buffers and changing bubble pairs.

Part J How many transistors are required for the new implementation?

number of transistors = _____

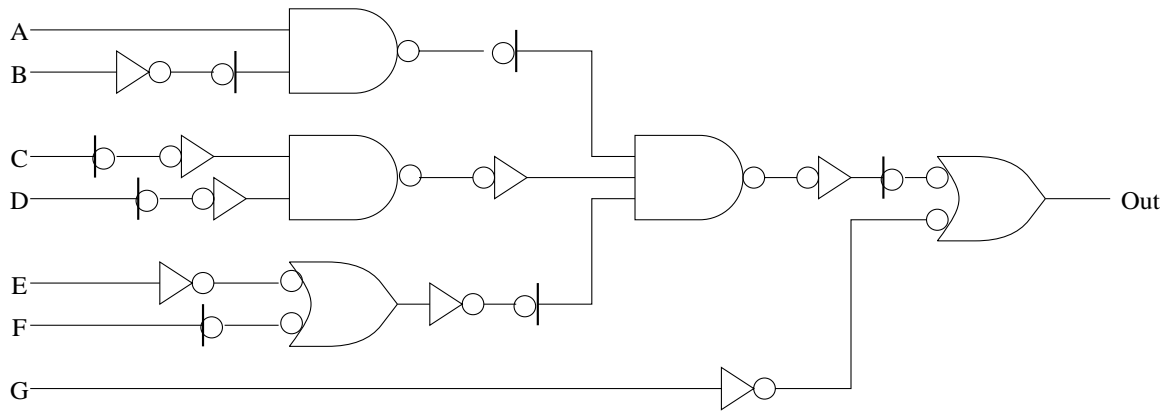Part K Express the function computed by this circuit.



$F_{(A,B,C,D,E,F,G)} =$ _____

Part L How many transistors are required for the circuit implementation above?

number of transistors = _____

Part M Now change the implementation to use 2-input and 3-input NOR and NOT gates. Accomplish this only by adding buffers and changing bubble pairs.