
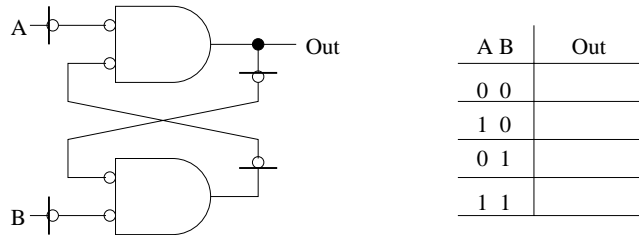


## Transparent Latches

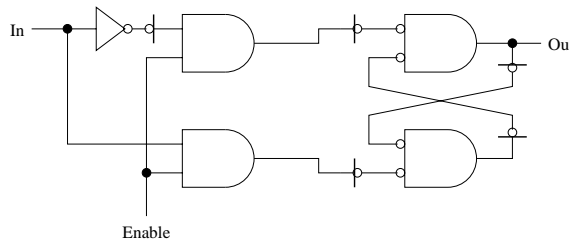**Part A** Complete the truth table to describe the circuit below:




**Part B** Now consider a transparent latch based on this circuit (show below). How many transistors are used in this implementation?



\_\_\_\_\_transistors

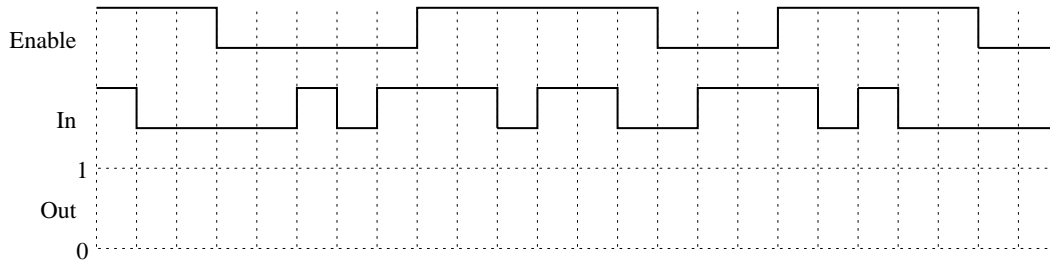**Part C** Complete the timing diagram for the latch output based on the specified inputs.




**Part D** Design a latch using four 2-input NOR gates and two inverters. Be sure to label the signals In, Out, and Enable.


**Part E** Design a transparent latch using four 2-input AND gates and five inverters. Be sure to label the signals In, Out, and Enable.

**Part F** Design a transparent latch using only four 2-input OR gates and six inverters. Be sure to label the signals In, Out, and Enable.

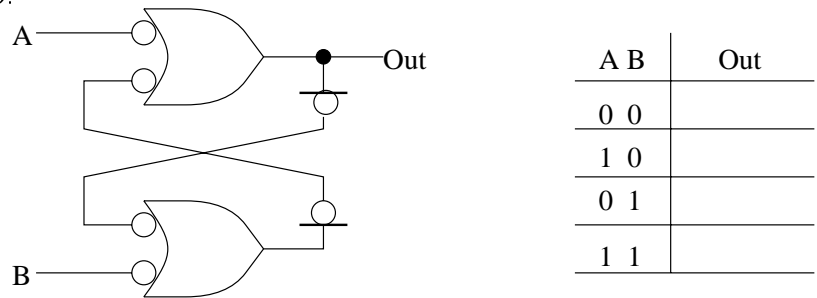**Part G** Complete the truth table to describe the circuit below. Also indicate which states denote RESET, SET, and HOLD.



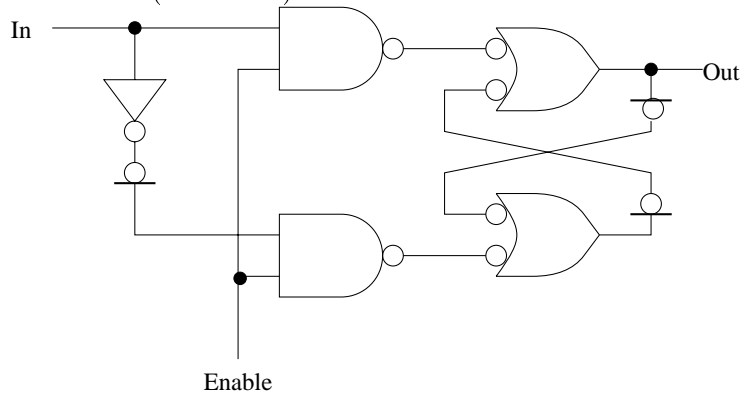**Part H** Now consider a transparent latch based on this circuit (shown below). How many transistors are used in this implementation (show work)?



\_\_\_\_\_transistors

**Part I** Complete the timing diagram for the latch output based on the specified inputs.

