

**Register File**

Consider a register file which contains 32 registers. Each register has a word width of 64 bits.

**Part A** How many one bit register cells are needed to implement this register file? (show work)

---

---

**Part B** What type of decoder is required to select the X, Y, and Z registers? (i.e., a X to Y decoder).

\_\_\_\_\_ to \_\_\_\_\_

**Part C** What is the X bus width? (in bits)

\_\_\_\_\_ bits

**Part D** How many control wires are needed to select the register to be read onto the X bus?

\_\_\_\_\_ wires