


Part B Write microcode for this datapath to compute the function:

$$R_0 = (R_1 + R_3)/2 + 4(R_2 - R_0)$$

You may modify any register once its initial value has been used. Put your answers in decimal.

cycle	X	Y	Z	WE	add/sub	+/- enable	right/left	shiftenable
1								
2								
3								
4								
5								
6								
7								
8								

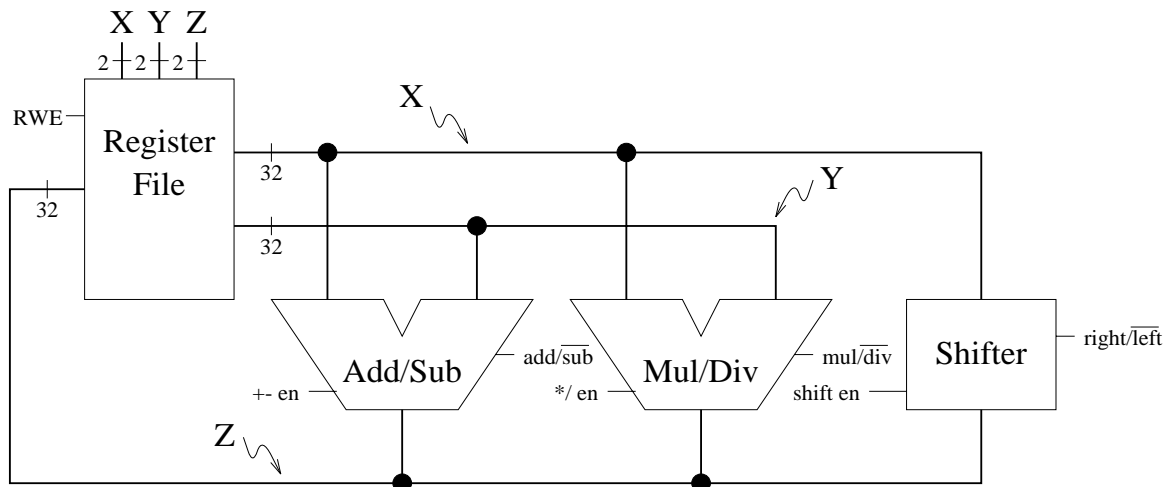Part C The datapath below incorporates an adder/subtractor, multiply/divider, and a one bit shifter. An arithmetic operation is specified by the add/sub and mul/div control lines. Subtraction is $(X - Y)$; division is (X/Y) . The shift direction is controlled by the $right/left$ control line. The enable signals determine which functional unit drives the Z bus. The datapath also contains a register file with four registers.



Write microcode for this datapath to compute the function below. The initial values of the registers should be used in the equation. Any register may be modified once its initial value has been used for the last time. Express all signals in octal notation (i.e., to select register two on the X bus, put a "2" in the X column).

Part H Write microcode for this datapath to compute the function below. For this part, use only R_0, R_1, R_2 .

$$R_0 = \frac{(3R_0 - R_1)(R_2 + R_1 - R_0)}{2}$$

cycle	X	Y	Z	RWE	add/sub	$+ - en$	mul/div	$*/en$	$right/left$	$shiften$
1										
2										
3										
4										
5										
6										
7										
8										

Part I For the datapath above, describe each microcode instruction below using register transfer notation (e.g., $R_0 \leftarrow R_1 + R_2$). Then deduce the expression computed by the microsequence.

cycle	X	Y	Z	RWE	add/sub	$+ - en$	mul/div	$*/en$	$right/left$	$shiften$	description
1	3	2	2	1	0	0	0	1	0	0	
2	2	0	2	1	0	0	0	0	0	1	
3	1	0	1	1	0	0	0	0	1	1	
4	1	0	1	1	0	0	0	0	1	1	
5	2	1	1	1	1	1	0	0	0	0	
6	1	0	0	1	0	0	0	1	0	0	

$R_0 =$ _____

