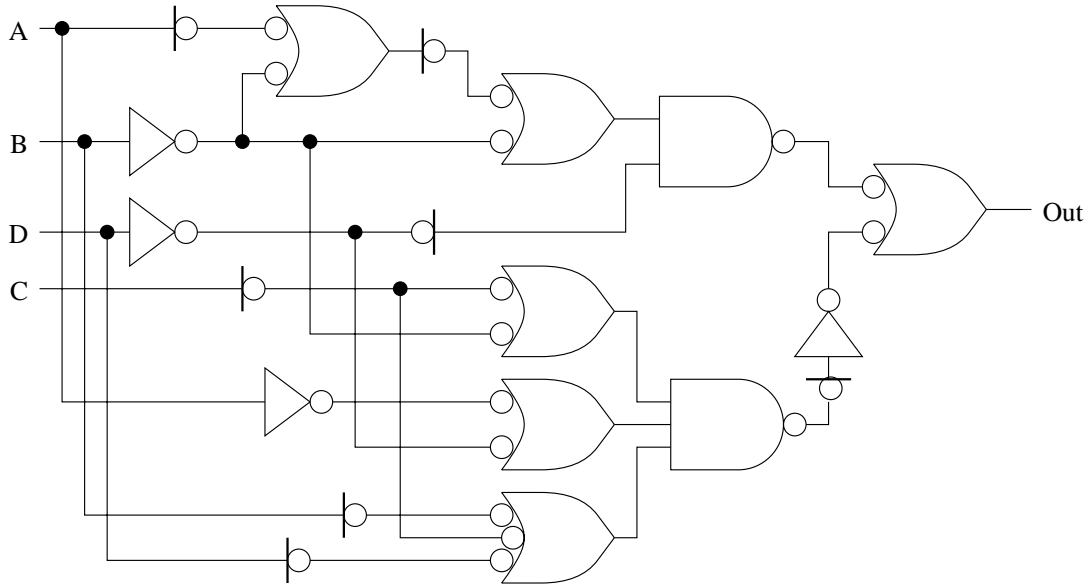


### Logic Simplification and Design

Consider the logical function:

$$Out = \overline{(\overline{A+B} + B)\overline{D}} + \overline{(\overline{C+B})(A+D)(\overline{B+C+D})}$$

**Part A** Implement the function using 2-input and 3-input NAND gates and inverters. Use a MIXED LOGIC design methodology. All bubbles must be paired; all bars must be bubbled.



**Part B** Use DeMorgan's Theorem to obtain an equivalent expression which contains ANDs and ORs of the inputs (e.g., A) and their complements (e.g.,  $\overline{A}$ ). There should be **no complements (bars)** in the final expression except those over the inputs. Do **not** simplify the expression for this part.

$$Out = (A\overline{B} + B)\overline{D} + C\overline{B} + \overline{A}\overline{D} + BCD$$

**Part C** Complete the Karnaugh map below and identify the prime implicants. Then write the simplified expression. Be sure the factor out any common terms in your solution.

|                |                |     |                |     |                |
|----------------|----------------|-----|----------------|-----|----------------|
|                | $\overline{B}$ | $B$ |                |     |                |
| $\overline{A}$ | 1              | 0   | 0              | 1   | $\overline{C}$ |
| $A$            | 1              | 1   | 1              | 1   | $C$            |
| $\overline{A}$ | 1              | 0   | 0              | 1   | $\overline{C}$ |
|                | $\overline{D}$ | $D$ | $\overline{D}$ | $D$ |                |

| prime implicant | essential?  |
|-----------------|---|
| $\overline{C}$  | yes <input checked="" type="checkbox"/> no <input type="checkbox"/> |
| $\overline{D}$  | yes <input checked="" type="checkbox"/> no <input type="checkbox"/> |
| _____           | yes <input type="checkbox"/> no <input type="checkbox"/>            |
| _____           | yes <input type="checkbox"/> no <input type="checkbox"/>            |
| _____           | yes <input type="checkbox"/> no <input type="checkbox"/>            |
| _____           | yes <input type="checkbox"/> no <input type="checkbox"/>            |

$$Out = C + \overline{D}$$

**Part D** Now reimplement the simplified expression from part C using 2-input NAND gates and inverters. Use the MIXED LOGIC design methodology. All bubbles must be paired; all bars must be bubbled.

