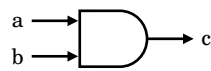


1. AND gate ($c = a \cdot b$)



a	b	$c = a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

2. OR gate ($c = a + b$)




a	b	$c = a + b$
0	0	0
0	1	1
1	0	1
1	1	1

3. Inverter ($c = \bar{a}$)



a	$c = \bar{a}$
0	1
1	0

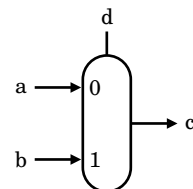4. Multiplexor
(if $d = 0$, $c = a$;
else $c = b$)



d	c
0	a
1	b

