

EXAMINATION NO. 1


NAME _____ SCORE _____ /100

INSTRUCTIONS: This exam is closed book with one sheet of notes permitted. The exam consists of 4 questions for a total of 100 points. Please show your work leading to your answers so that maximum partial credit may be given where appropriate. Be sure to turn in your exam with the problems in numerical order, firmly attached together.

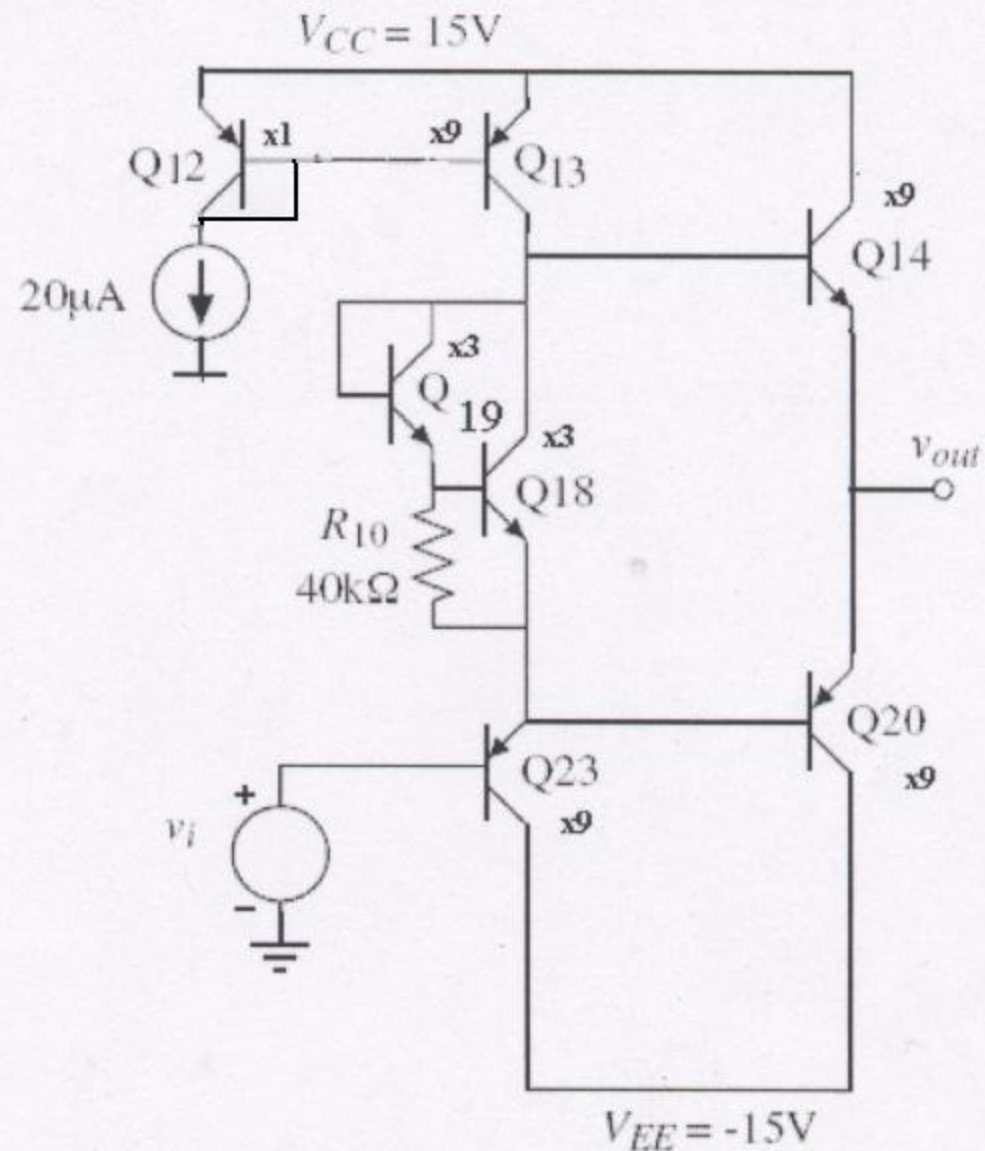Problem 1 - (25 points)

An push-pull output stage is shown. Assume that $\beta_N = \beta_P = 100$, $V_t = 26\text{mV}$, and $I_s = 1.11\text{fA}$, $V_{BE(\text{on})} = 0.6\text{V}$, $V_{CE(\text{sat})} = 0.2\text{V}$.

- a.) Find the dc value of the collector currents when $v_{OUT} = 0$.
- b.) If $R_L = 1\text{K}$, what is the \pm peak output voltage of this amplifier? What is the maximum output current that can be delivered to the 1K resistive load?
- c.) What is the maximum average power delivered to the load? What is the average power drawn from the sources? What is the efficiency of the circuit?



$$a) I_{C13} = 9 \times I_{C12} = \boxed{180 \mu\text{A}}$$

$$I_{C23} = 180 \mu\text{A}$$

$$I_{C19} = \frac{0.6}{40\text{k}} = \boxed{15 \mu\text{A}}$$

$$I_{C18} = 180 - 15 = \boxed{165 \mu\text{A}}$$

$$I_{C14} = I_{C20} = 3 \times \sqrt{I_{C19} \times I_{C18}} = \boxed{149.2 \mu\text{A}}$$

$$b) v_{out\text{max}} = 15 - V_{BE14} - V_{CE13} = 15 - 0.6 - 0.2 = \boxed{14.2\text{V}}$$

$$v_{out\text{min}} = -15 + 0.2 + 0.6 = \boxed{-14.2\text{V}}$$

$$R_L = 1\text{k} \quad i_{out\text{max}} = \frac{15 - 0.2 - V_{BE14}}{R_L} \times \frac{I_{out\text{max}}}{R_L} \rightarrow i_{out\text{max}} = \boxed{14.07}$$

$$\boxed{V_{BE14} = 0.7}$$


$$c) P_L = \frac{1}{2} I_o^2 \times R_L = \boxed{99\text{mW}}$$

$$P_{\text{supply}} = \frac{1}{\pi} \times (2V_{CC} \times \hat{I}_o) = \boxed{134\text{mW}}$$

$$\eta = \frac{P_L}{P_{\text{supply}}} \times 100 = \boxed{73.68}$$

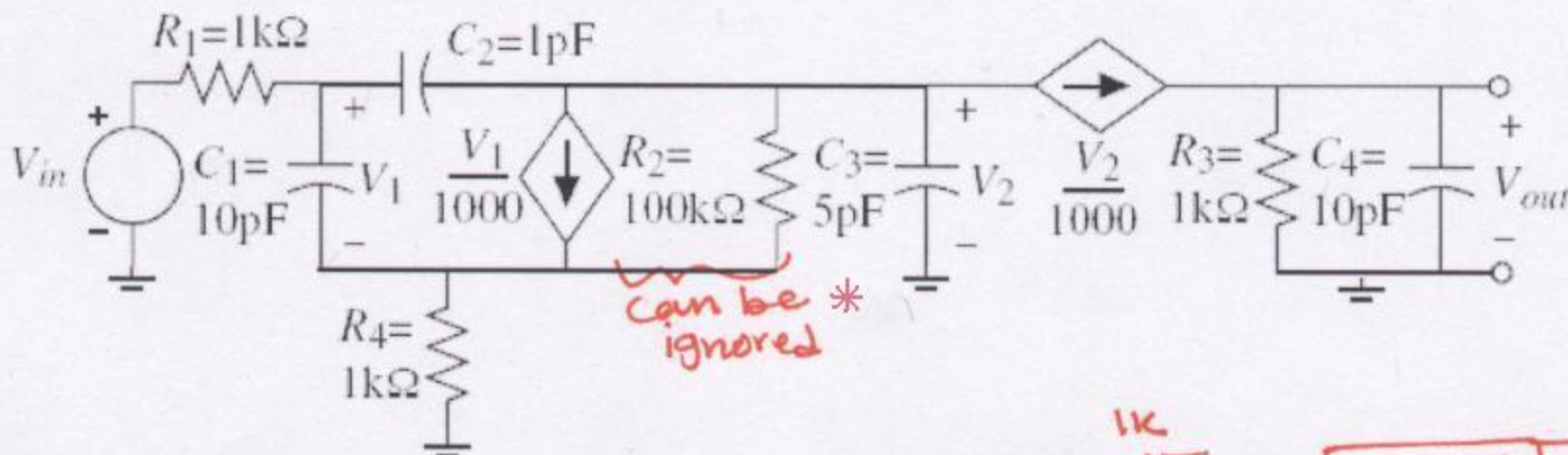
Problem 3 - (25 points)

Find the midband voltage gain, the -3dB frequency and the magnitude of sum of all the poles in Hertz for the circuit shown (Assume zeros are not dominant).



$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_2} \times \frac{V_2}{V_1} \times \frac{V_1}{V_{in}}$$
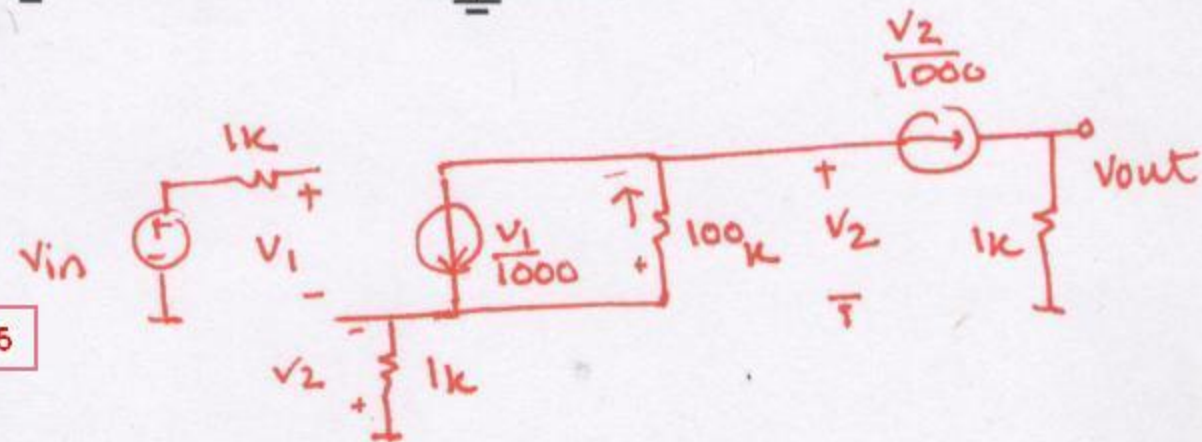
$$= 1 \times \frac{V_2}{V_1} \times \frac{V_1}{V_{in}} = -\frac{102}{100} \times \frac{102}{202} = -0.495$$



$$V_{in} = V_1 + \frac{-V_2}{1000} \times 1k \rightarrow V_{in} = V_1 + \frac{V_1 \times 100}{1000} \times 1000 \rightarrow \frac{V_{in}}{V_1} = \frac{202}{102}$$

$$+V_2 + \left(\frac{V_2 + V_1}{1000} \times 100k\right) + V_2 = 0 \rightarrow V_1 \times 100 = -V_2(102) \rightarrow \frac{V_1}{V_2} = -\frac{102}{100}$$


if ignore R2:

$$\frac{V_{out}}{V_2} = 1$$

$$V_{in} = 2V_1$$

$$V_2 = -V_1$$
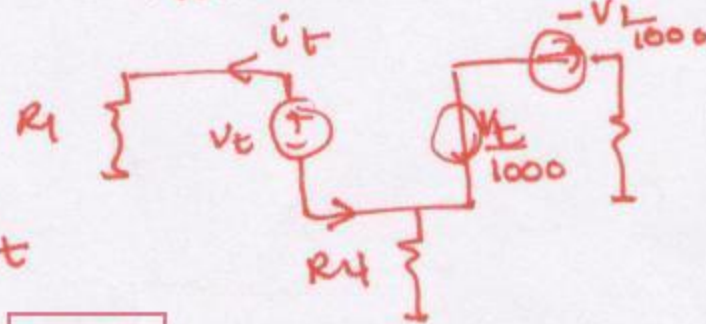
$$\rightarrow \frac{V_{out}}{V_{in}} = 1 \times (-1) \times \frac{1}{2} = -0.5$$



$$(-i_t + \frac{V_t}{1000}) \times R_4 + V_t = R_1 i_t$$

$$\rightarrow 2V_t = (R_1 + R_4) i_t \rightarrow \frac{V_t}{i_t} = 1k\Omega$$

$$\rightarrow \tau_1 = 1k \times 10pF = 10nsec$$

tau2 (for C2)


$$i_t + \frac{V_1}{1000} + \frac{V_2}{1000} = 0$$

$$V_1 = R_1 i_t - V_1 \rightarrow 2V_1 = R_1 i_t$$

$$V_2 = 2V_1 - V_t$$

$$\rightarrow i_t + \frac{i_t}{2} + \frac{R_1 i_t - V_t}{1000} = 0 \rightarrow 2.5 i_t = \frac{V_t}{1000} \rightarrow \frac{V_t}{i_t} = 2.5k$$

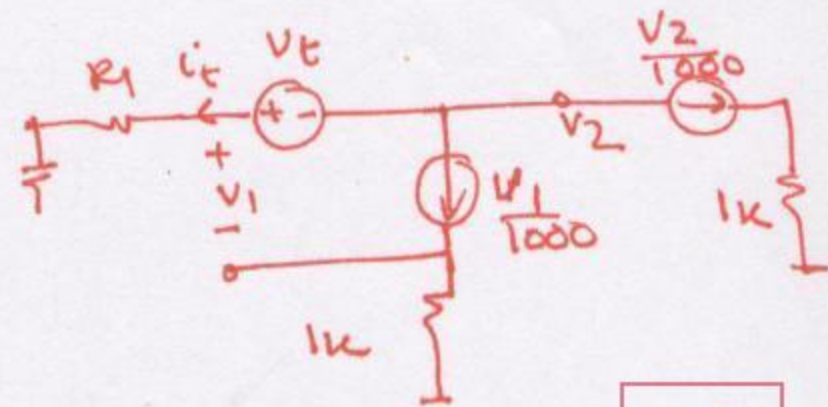
$$\rightarrow \tau_2 = 1pF \times 2.5k = 2.5nsec$$



tau3 (for C3)

$$\frac{V_t}{i_t} = 1000$$
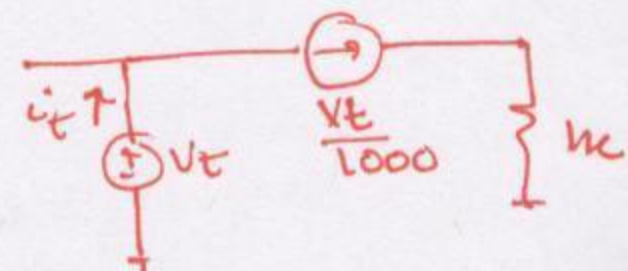
$$\rightarrow \tau_3 = 1k \times 5pF = 5nsec$$



$$\tau_4 (for C4) = 1k \times 10pF = 10nsec$$

$$\rightarrow \tau = 10n + 2.5 + 5 + 10 = 27.5nsec$$

$$\omega_{-3dB} = 36.4 Mrad/sec \quad f = 5.79 MHz$$

Extra Sheet

$$\sum_{i=1}^n P_i = \sum \frac{1}{\tau_{sc}}$$

Short circuit

$$\tau_{s1} \quad R_{s1} = 1k \parallel 1k \parallel 100k \approx 500\Omega$$

$$\rightarrow \tau_1 = 0.5 \times 10pF = 5nsec$$

$$\tau_{s2} \quad R_{s2} = 1k \parallel 1k \parallel 100k = 500\Omega$$

$$\rightarrow \tau_2 = 0.5 \mu \times 1pF = 0.5nsec$$

$$\tau_{s3} : \quad R_{s3} = R_1 \parallel R_4 \parallel 1k = 333.3\Omega$$




$$\rightarrow \tau_3 = 5pF \times 0.33 = 1.67nsec$$

$$\tau_{s4} : \quad R_{s4} = 1k$$

$$\rightarrow \tau_{s4} = 1k \times 10pF = 10nsec$$

$$\rightarrow \sum_{i=1}^n P_i = \left(\frac{1}{5} + \frac{1}{0.5} + \frac{1}{1.67} + \frac{1}{10} \right) \times 10^9 = 2.89 \times 10^9 \text{ rad/sec}$$

$$\sum_{i=1}^n P_i = 461.3 \text{ MHz}$$

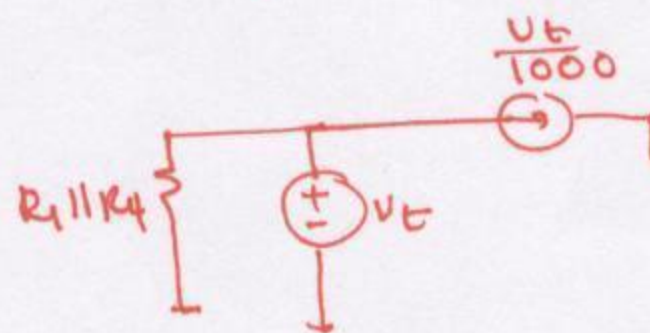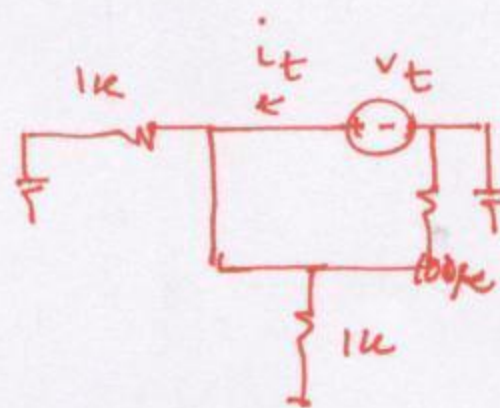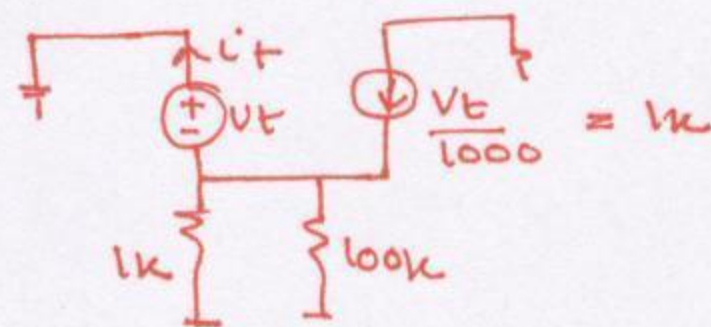

Problem 4 - (25 points)


(a) Find the values of the resistances (R_1 , R_2 , and R_3) such that $I_{out} = 10 \mu A$ for both circuits.

Assume that $\beta_N = 100$, $V_T = 26 mV$, and $V_{BE} = 0.7V$ for $I_C = 1 mA$.

(b) By comparing the values of the resistances, explain the advantage of circuit b.

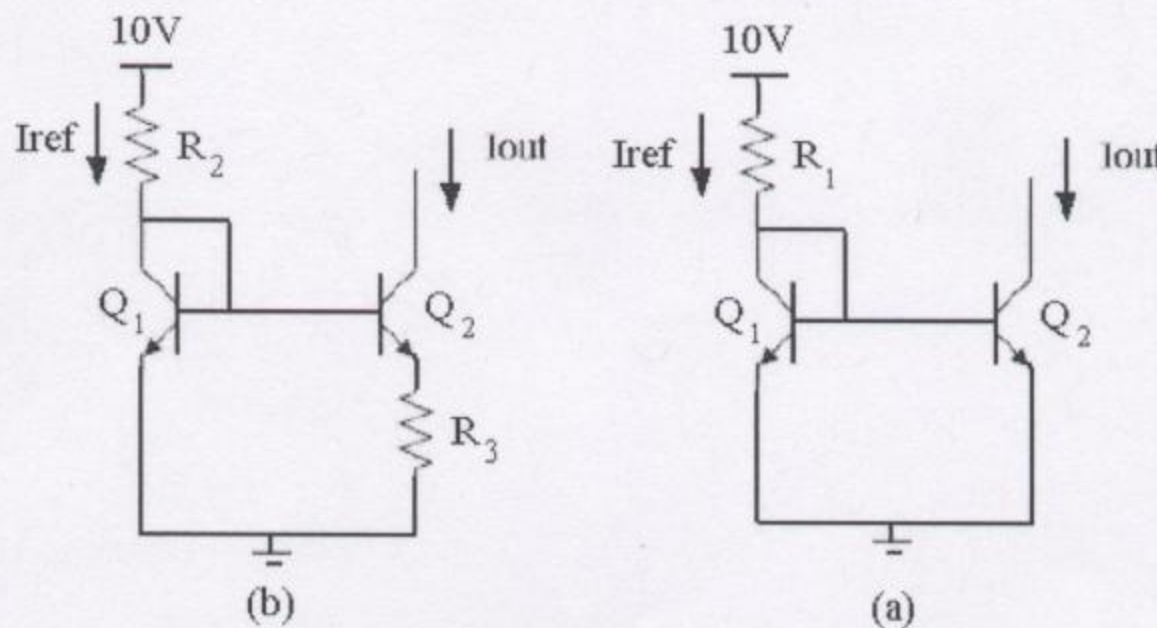(c) Compare the output resistances of the two circuits and explain the second advantage of circuit b.

Assume $V_A = 10V$. (Circuit b is a Widlar current source)



(a) $I_{ref} = 10 \mu A$ $V_{BE} = V_T \ln \frac{I_C}{I_S}$
 $\rightarrow 0.7 - V_{BE} = 26 mV \ln \frac{1 mA}{I_{ref}} \rightarrow V_{BE} = 0.58V$

$$R_1 = \frac{10 - 0.58}{10 \mu A} = 942 k\Omega$$

$$I_{out} = 10 \mu A$$

$$\text{pick } I_{ref} = 1 mA \rightarrow R_2 = \frac{10 - 0.7}{1 mA} = 9.3 k\Omega$$

$$V_{BE2} = 0.58V \rightarrow R_3 = \frac{0.7 - 0.58}{10 \mu A} = 12 k\Omega$$

(b) circuit b is better for having smaller resistances \rightarrow easier to fabricate

(c) $R_{out(a)} = r_o$

$$R_{out(b)} = r_o (1 + \beta_{m2} (R_3 \parallel r_{e1}))$$

circuit b has larger output resistance \rightarrow better for current source