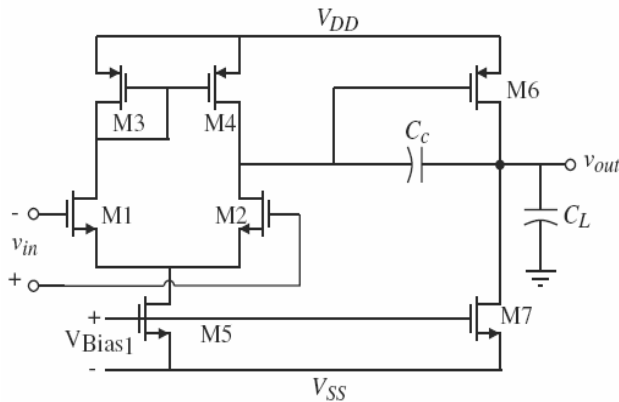


EXAMINATION NO. 2 SOLUTIONS


**Problem 1 - (35 points)**

The op amps below have identical DC currents and W/L values for transistors with the same number. Find parametric expressions for entries in the table in terms of bias currents  $I_5$  and  $I_7$ ,  $K_n'$ ,  $K_p'$ ,  $\lambda_N$ ,  $\lambda_P$ ,  $V_{TN}$ ,  $|V_{TP}|$ ,  $S=W/L$  ratios,  $V_{DD}$ ,  $V_{SS}$ ,  $C_c$ ,  $C_L$ , and identify which is larger in magnitude for the two circuits. Assume  $K_n' > K_p'$ ,  $V_{TN} = -V_{TP}$ ,  $\lambda_N < \lambda_P$ ,  $(W/L)_1 = (W/L)_2$ ,  $V_{DD} = -V_{SS}$ . The threshold voltage is larger than the ON (saturation) voltage. Ignore body effect.

**USE THE LAST SHEET TO DO YOUR WORK AND THEN WRITE YOUR FINAL ANSWER/EXPRESSION IN THE TABLE. NO PARTIAL CREDIT.**



N-channel Input Op Amp

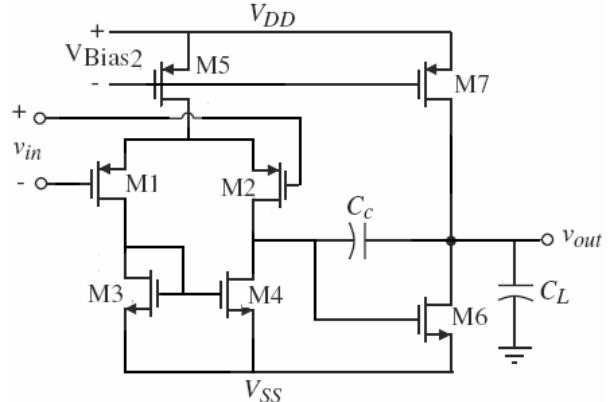

P-channel Input Op Amp

Characteristic	N-channel Input Op Amp	<,=,>	P-channel Input Op Amp
Small-signal output resistance	$(I_7(\lambda_6 + \lambda_7))^{-1}$	=	$(I_7(\lambda_6 + \lambda_7))^{-1}$
Small-signal voltage gain	$\frac{\sqrt{8K'_N K'_P S_1 S_6}}{\sqrt{I_5 I_7}(\lambda_2 + \lambda_4)(\lambda_6 + \lambda_7)}$	=	$\frac{\sqrt{8K'_N K'_P S_1 S_6}}{\sqrt{I_5 I_7}(\lambda_2 + \lambda_4)(\lambda_6 + \lambda_7)}$
Gain-bandwidth	$\frac{\sqrt{K'_N S_1 I_5}}{C_c}$	>	$\frac{\sqrt{K'_P S_1 I_5}}{C_c}$
Upper input common mode voltage	$V_{DD} -  V_{TP}  + V_{TN} - \sqrt{\frac{I_5}{K'_P S_3}}$	>	$V_{DD} -  V_{TP}  - \sqrt{\frac{2I_5}{K'_P S_5}} - \sqrt{\frac{I_5}{K'_P S_1}}$
Slew rate(due to Cc)	$\frac{I_5}{C_c}$	=	$\frac{I_5}{C_c}$
Positive ( $V_{DD}$ ) PSRR	no expression needed	<	no expression needed


Negative (V <sub>SS</sub> ) PSRR	no expression needed	>	no expression needed
<b>Phase Margin (EXTRA CREDIT)</b>	$90^\circ - \tan^{-1}\left(\frac{\sqrt{K'_N S_1 I_5}}{\sqrt{2K'_p S_6 I_7}} \frac{C_L}{C_C}\right) - \tan^{-1}\left(\frac{\sqrt{K'_N S_1 I_5}}{\sqrt{2K'_p S_6 I_7}}\right)$	<	$90^\circ - \tan^{-1}\left(\frac{\sqrt{K'_p S_1 I_5}}{\sqrt{2K'_N S_6 I_7}} \frac{C_L}{C_C}\right) - \tan^{-1}\left(\frac{\sqrt{K'_p S_1 I_5}}{\sqrt{2K'_N S_6 I_7}}\right)$

**Problem 2 - (35 points)**

The device parameters for the operational amplifier shown below are given in the table. Ignore the body effect of the MOS transistor and the internal capacitances of all the transistors.

- What resistance  $R$  in the emitter of  $Q_9$  is required to set the first stage bias currents in the emitters of  $Q_3$  and  $Q_4$  at  $10\mu A$  each?
- Calculate the overall voltage gain of the amplifier, by calculating the effective transconductances of the differential input stage and the 2<sup>nd</sup> gain stage, and their effective output resistances.
- Calculate the value of the miller capacitance  $C_c$  required to obtain a gain-bandwidth of 2MHz for this op-amp.
- Calculate the phase margin of this op-amp.

Parameter	NPN	PNP
Beta	200	50
Early voltage	130V	50V
VBE(on)	0.7V	0.7V
Vt	25mV	
	<b>MOS</b>	
lambda	0.01V <sup>-1</sup>	
μCox	100μA/V <sup>2</sup>	
VTO	0.7V	

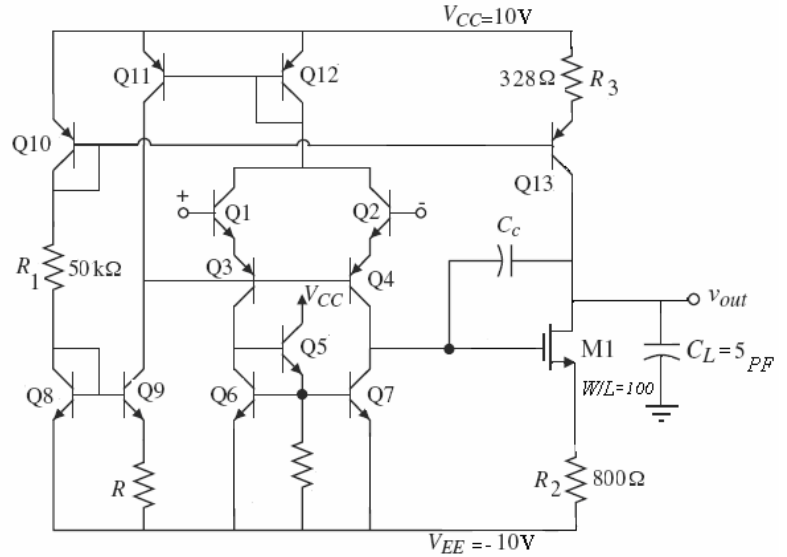

$$a) R_{I_{C9}} = V_t \ln(I_{C8}/I_{C9})$$

$$I_{C8} = (20V - 1.4V) / 50k\Omega = 0.372mA$$

$$I_{C9} = 20\mu A \rightarrow R = 3.65k\Omega$$

$$b) G_{mI} = \frac{g_{m1}}{1 + g_{m1}r_{e3}} = \frac{g_{m1}}{2} = 200 \times 10^{-6} \frac{A}{V} \quad \text{note that: } r_{e3} = \frac{1}{g_{m3}} = \frac{1}{g_{m1}}$$

$$R_I = r_{07} \parallel r_{04}(1 + g_{m4} \times r_{e2}) = r_{07} \parallel 2r_{04} = 5.65M\Omega$$

$$\text{because: } r_{07} = \frac{V_{A_{npn}}}{I_{C7}} = 13M\Omega \quad \text{and} \quad r_{04} = \frac{V_{A_{pnp}}}{I_{C4}} = 5M\Omega$$

$$\rightarrow A_{vI} = G_{mI} \times R_I = 1130$$

$$R_3 I_{C13} = V_t \ln\left(\frac{I_{C10}}{I_{C13}}\right) \Rightarrow I_{C13} = 100\mu A$$

$$G_{mII} = \frac{g_{mm1}}{1 + g_{mm1}R_2} = 0.663 \times 10^{-3} \frac{A}{V} \quad \text{note that: } g_{mm1} = \sqrt{2\mu C_{ox} \left(\frac{W}{L}\right)_{mm1} I_{mm1}} = 1.414 \times 10^{-3} \frac{A}{V}$$

$$R_{II} = r_{ds1}(1 + g_{mm1} \times R_2) \parallel r_{013}(1 + g_{m13} \times R_3) = 2.13M\Omega \parallel 1.16M\Omega = 0.749M\Omega$$

$$A_{vII} = G_{mII} R_{II} = 497$$

$$A_v = A_{vI} \times A_{vII} \cong 561,610$$

$$c) \quad GBW = \frac{G_{mII}}{C_c} \quad \Rightarrow \quad C_c = \frac{200 \times 10^{-6}}{2\pi \times 2 \times 10^6} = 15.9 \text{ pF}$$

$$d) \quad \Phi_M = 90^\circ - \tan^{-1}\left(\frac{2 \text{ MHz}}{p_2}\right) - \tan^{-1}\left(\frac{2 \text{ MHz}}{z}\right)$$

$$p_2 = \frac{G_{mII}}{C_L} = \frac{0.663 \times 10^{-3}}{5 \times 10^{-12}} = 132 \times 10^6 \text{ rad/sec} = 21.1 \text{ MHz}$$

$$z = \frac{G_{mII}}{C_c} = \frac{0.663 \times 10^{-3}}{15.9 \times 10^{-12}} = 41.69 \times 10^6 \text{ rad/sec} = 6.64 \text{ MHz}$$

$$\Rightarrow \quad \Phi_M = 90^\circ - \tan^{-1}\left(\frac{2}{21}\right) - \tan^{-1}\left(\frac{2}{6.64}\right) = 90^\circ - 5.41^\circ - 16.76^\circ = 67.82^\circ$$



- d. Show an expression for the pole associated with node 3, in terms of transistors internal capacitances, transconductances and output resistances. Identify all the components of the internal capacitances.

$$p_3 = \frac{1}{(r_{ds6} \parallel R_3)C_3}$$

$$C_3 = C_{gs7} + C_{sb7} + C_{gd6} + C_{db6}$$

$$R_3 = \frac{r_{ds7} + g_{m8}r_{ds8}r_{ds9}}{1 + g_{m7}r_{ds7}} \cong \frac{1}{g_{m7}} + \frac{g_{m8}r_{ds8}r_{ds9}}{g_{m7}r_{ds7}}$$

- e. Is there a right half plane zero in this amplifier that would affect the phase margin? If there is, provide an expression for the position of this zero.

No, because a miller configuration is not used → there is no RHZ that would affect the phase margin

- f. **(EXTRA CREDIT)** Show expressions for any pole or zero associated with node 4. Identify all the components of the internal capacitances.

$$p_4 = \frac{-g_{m3}}{C_x}$$

$$C_x = C_{gs3} + C_{gs4} + C_{db3} + C_{db1} + C_{gd1}$$

$$z_4 = \frac{-2g_{m3}}{C_x}$$