

**Homework Assignment No. 1**

This homework assignment is due in class on Friday, January 13, 2006.

The following transistor parameters should be used unless otherwise stated.

**MOSFETS**

MOSFET Parameter	n-channel	p-channel	units
$K'$	24	8	$\mu\text{A}/\text{V}^2$
$V_{T0}$	0.75	-0.75	V
$\gamma$	0.8	0.4	$\text{V}^{0.5}$
$\phi$	0.6	0.6	V
$\lambda$	0.01	0.02	$\text{V}^{-1}$

$$C_{\text{ox}} = 0.7\text{fF}/\mu\text{m}^2$$

$$\text{LD(NMOS)} = 0.45\mu\text{m}$$

$$\text{LD(PMOS)} = 0.6\mu\text{m}$$

$$n^+ \text{ diffusion to p-well (junction, bottom)} = 0.33\text{fF}/\mu\text{m}^2$$

$$n^+ \text{ diffusion sidewall (junction, sidewall)} = 0.9\text{fF}/\mu\text{m}$$

$$p^+ \text{ diffusion to substrate (junction, bottom)} = 0.38\text{fF}/\mu\text{m}^2$$

$$p^+ \text{ diffusion sidewall (junction, sidewall)} = 1.0\text{fF}/\mu\text{m}$$

$$\text{n-channel to bulk (junction, bottom)} = 0.1\text{fF}/\mu\text{m}^2$$

$$\text{n-channel to bulk (junction, sidewall)} = 0.3\text{fF}/\mu\text{m}$$

$$\text{p-channel to bulk (junction, bottom)} = 0.1\text{fF}/\mu\text{m}^2$$

$$\text{p-channel to bulk (junction, sidewall)} = 0.3\text{fF}/\mu\text{m}$$

**BJTS**

BJT Parameter	NPN	PNP (lateral)	units
$\beta$	100	50	A/A
$V_t$	26	26	mV
$I_S$	10	10	fA
$\phi_B$	0.8	0.8	V
$V_{AF}$	100	50	V

	$C_{jE0}$	$C_{jC0}$	$C_{jS0}$	n	$\phi_B$	$t_F$
Vertical NPN	100fF	1000fF	2000fF	0.5	0.8V	0.5ns
Lateral PNP	80fF	500fF	2000fF	0.5	0.8V	5ns


Problem 1 - (10 points)

A top view of a MOS transistor is shown.

(a) Identify the type of transistor (NMOS or PMOS) and its value of  $W$  and  $L$ .


(b.) Draw the cross-section A-A' approximately to scale.

(c) Assume that dc voltage of terminal 1 is 5V, terminal 2 is 3V and terminal 3 is 0V. Find the numerical value of the capacitance between terminals 1 and 2, 2 and 3, and 1 and 3. Assume that the voltage dependence for pn junction capacitances is -0.5 (this is called MJ in SPICE).

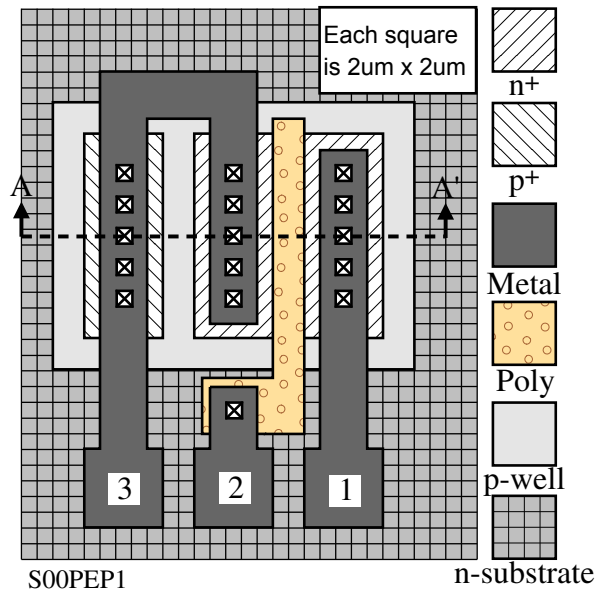


Problem 2 - (10 points)

Find the numerical values of  $I_1$ ,  $I_2$ ,  $V_D$ ,  $V_E$ , and  $V_C$  to within  $\pm 5\%$  accuracy.

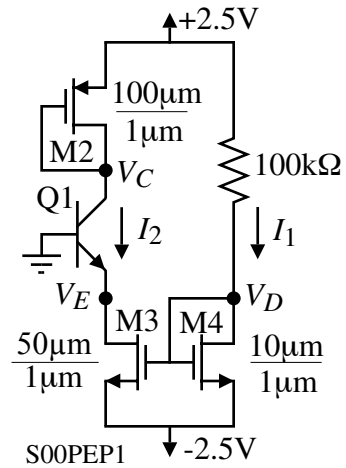

Problem 3 - (10 points)

Find the numerical values of all roots and the midband gain of the transfer function  $v_{out}/v_{in}$  of the differential amplifier shown. Assume that  $K_N' = 100\mu A/V^2$ ,  $V_{TN} = 0.7V$ , and  $\lambda_N = 0.04V^{-1}$ . The values of  $C_{gs} = 0.2pF$  and  $C_{gd} = 20fF$ .

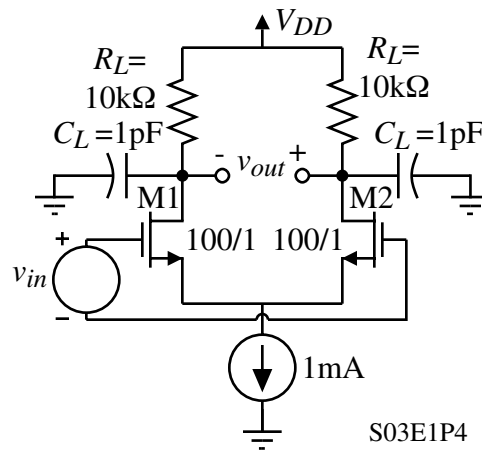


Problem 4 - (10 points)

Find the voltage transfer function of the common-gate amplifier shown. Identify the numerical values of the small-signal voltage gain,  $v_{out}/v_{in}$ , and the poles and zeros. Assume that


$I_D = 250\mu A$ ,  $K_N' = 100\mu A/V^2$ ,  $V_{TN} = 0.5V$ ,

$\lambda \approx 0V^{-1}$ ,  $C_{gs} = 0.5pF$  and  $C_{gd} = 0.1pF$ .

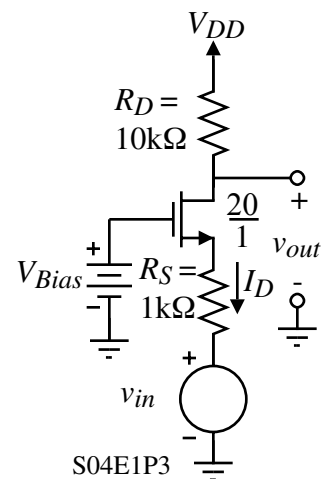

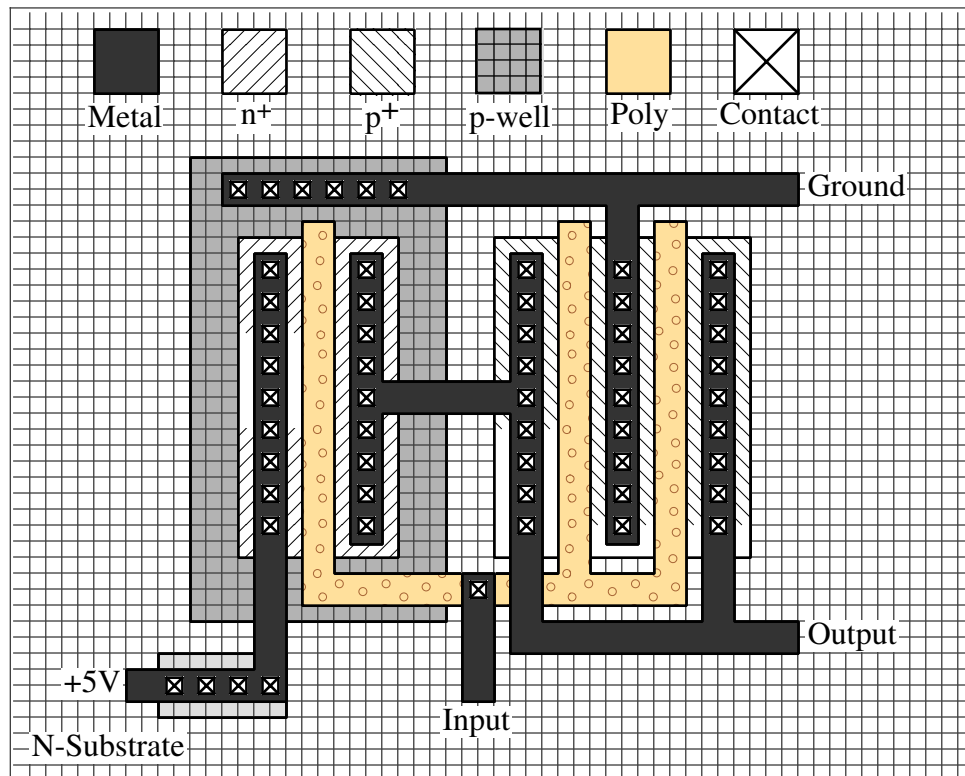Problem 5 - (10 points)

Draw the electrical schematic using the proper symbols for the transistors. Identify on your schematic the terminals that are +5V, ground, input, and output. Label the transistors on the layout as M1, M2, etc. and determine their W/L values. Assume each square in the layout is 2 micron by 2 micron. Find the area in square microns and periphery in microns for the source and drain of each transistor.



S01PEP1