

Homework Assignment No. 2

Due Friday, January 27, 2006 in class

Problem 1 - (10 points)

Problem 5.20 of Gray and Meyer. The SPICE parameters to use for this problem are:

.MODEL NPN NPN RB=200 BF=80 IS=1E-18 VAF=130

.MODEL PNP PNP RB=300 BF=20 IS=1E-18 VAF=50

.MODEL PMOS PMOS KP=26U LAMBDA=0.0125 VTO=-0.7 LD=0

Use the following table to summarize your answers for easier grading.

(a). Device Currents

| | Hand Calculations | SPICE Simulations |
|----------|-------------------|-------------------|
| I_{C1} | | |
| I_{C2} | | |
| I_{C3} | | |
| I_{C5} | | |
| I_{C6} | | |
| I_{D1} | | |
| I_{D2} | | |
| I_{D3} | | |

(b). $V_{o(max)} =$ _____ $V_{o(min)} =$ _____

$P_{max} =$ _____

(c). SPICE Results

- A plot of the DC transfer characteristic and mark on your results where clipping begins to occur.
- Plots of i_{C1} , i_{C2} , and i_{D2} for $v_o = 2V$ peak and $v_o = 4V$ peak. Assume a signal frequency of 10 KHZ. (Note: you will have to apply the appropriate dc bias and signal amplitude to achieve the desired output conditions.)
- Also use SPICE to compute the THD of the output voltage for both the 2V and 4 V conditions.

| | Hand Calculations | SPICE Simulations |
|--------------|-------------------|-------------------|
| Clipping | | |
| max | | |
| min | | |
| THD of v_o | | |
| 2V peak | NA | |
| 4V peak | NA | |

Problem 4 - (10 points)

Derive an expression for the output resistance of the MOS Wilson current mirror shown in Figure 4.15 of GHLM. You must show your work to receive credit.