

## Homework Assignment No. 9 Solutions

## Problem 1 – (10 points)

8.1(a)

$$a = 100,000$$

$$f = 10^{-3}$$

$$A = \frac{a}{1+af} = \frac{10^5}{1+10^2} = 990.1$$

$$\frac{dA}{da} = \frac{1}{(1+af)^2}$$

$$da = \frac{1}{10} \times 10^5 = 10^4$$

$$dA = \frac{10^4}{(1+10^5 \times 10^{-3})^2} = 0.98 \rightarrow \frac{dA}{A} = \frac{0.98}{990.1} = \%0.099$$


8.1(b)  $f=0.1$ 

$$\frac{\delta A}{A} = \frac{\frac{\delta a}{a}}{1+af} = \frac{0.1}{1+10^5 \times 0.1} = 9.99 \times 10^{-4} \%$$

Problem 2 – (10 points)

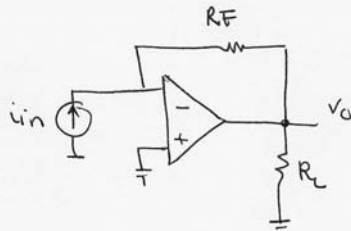8.6a

$$\begin{aligned} R_F &= 150\text{k} \\ R_L &= 110\text{k} \\ R_i &= 800\text{k} \\ R_o &= 200\Omega \\ a_v &= 75,000 \end{aligned}$$



$$f = -\frac{1}{R_f}$$

$$\begin{aligned} a &= \frac{v_o}{i_{in}} = \frac{-R_F R_i}{R_F + R_i} \times a_v \times \frac{R_L \parallel R_F}{(R_L \parallel R_F) + R_o} \\ &= -\underbrace{(150\text{k} \parallel 800\text{k})}_{126.3\text{k}} \times 75 \times 10^3 \times \frac{(110\text{k} \parallel 150\Omega)}{\underbrace{(110\text{k} \parallel 150\text{k})}_{63\text{k}} + 200\Omega} = -9.46\Omega \end{aligned}$$

$$\rightarrow T = af = 63000$$


$$Z_{in} = \frac{Z_i}{1+af} = \frac{R_F \parallel R_i}{63000} = 2\Omega$$

$$Z_{out} = \frac{Z_o}{1+af} = \frac{R_o \parallel R_F \parallel R_L}{63000} = 0.013$$

$$A = \frac{a}{1+af} = \frac{-9.46}{63000} = -149\text{k}\Omega \approx -R_F$$

Problem 3 – (10 points)

8.12

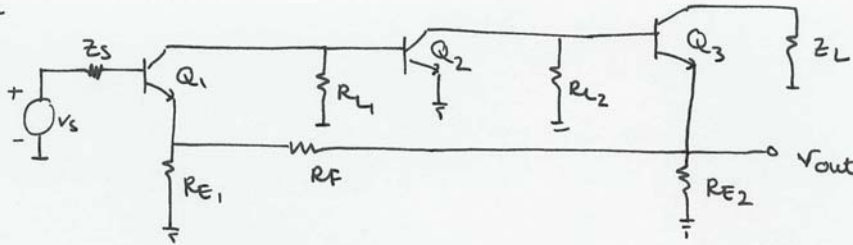

$Z_{in}, Z_{out}, A, T$

$$R_{E1} = R_{E2} = 290 \Omega$$

$$R_F = 1.9 \text{ k}\Omega$$

$$R_{L1} = 10.6 \text{ k}\Omega$$

$$R_{L2} = 6 \text{ k}\Omega$$

$$I_{C1} = 0.5 \text{ mA}$$


$$I_{C2} = 0.77 \text{ mA}$$

$$I_{C3} = 0.73 \text{ mA}$$

$$\beta = 120, V_A = 40 \text{ V}$$

$$V_b = 0$$

Series-shunt feedback

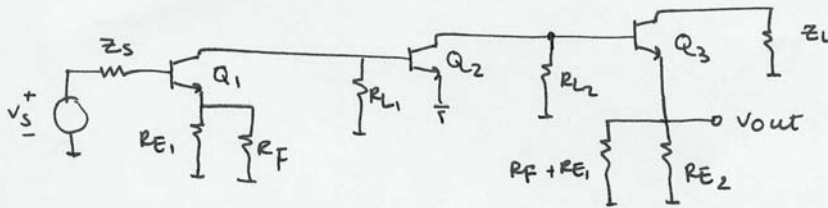

$$\frac{V_o}{V_s} = A = \frac{a}{1+af}$$

$$f = \frac{R_{E1}}{R_{E1} + R_F} = \frac{0.29}{1.9 + 0.29} = 0.132$$

$$\frac{V_{C1}}{V_s} = \frac{-g_{m1} \times (R_{L1} \parallel r_{\pi 2} \parallel r_{o1} (1 + g_{m1} (R_{E1} \parallel R_F)))}{1 + g_{m1} (R_{E1} \parallel R_F)} \times \frac{r_{\pi 3} (1 + g_{m3} (R_{E2} \parallel R_F))}{r_{\pi 3} (1 + g_{m3} (R_{E2} \parallel R_F)) + Z_L}$$

ignoring  $Z_s \rightarrow \frac{V_{C1}}{V_s} = \frac{-g_{m1} R_{out1}}{1 + g_{m1} (R_{E1} \parallel R_F)} = \underline{\underline{-9.4}}$

$$g_{m1} = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 0.02$$

$$R_{L2} = 3.896 \text{ k}\Omega$$

$$R_{out1} = 2.83 \text{ k}\Omega$$

$$R_{E1} \parallel R_F = 251 \Omega$$

$$r_{o1} = 80 \text{ k}\Omega$$

8.12 cont.

$$\frac{v_{c2}}{v_{c1}} = \left[ R_{L2} \parallel r_{o2} \parallel r_{\pi 3} (1 + g_{m3} [R_{E2} \parallel (R_F + R_{E1})]) \right] \times (-g_{m2})$$

$$g_{m2} = 0.031$$

$$r_{o2} = 51.95 \text{ k}\Omega$$

$$r_{\pi 3} = 4.1 \text{ k}\Omega$$

$$g_{m3} = 0.029$$

$$R_{E2} \parallel (R_F + R_{E1}) = 256 \Omega$$

$$\rightarrow \frac{v_{c2}}{v_{c1}} = -4.64 \mu \times 0.031 = -143.8$$

$$\frac{v_{out}}{v_{c2}} = \frac{g_{m3} \times 256}{1 + g_{m3} \times 256} = 0.88$$

$$\rightarrow \frac{v_{out}}{v_s} = (-9.4) (-143.8) (0.88) = \underline{1190} = a$$

$$\rightarrow A = \frac{a}{1 + af} = \frac{1190}{1 + \frac{1190 \times 0.29}{2.19}} = \underline{7.52} \quad T = \underline{15\%}$$

$$Z_{in} = \frac{Z_i}{(1 + af)^{-1}} = Z_i (1 + af)$$

$$Z_i = r_{\pi 1} \left[ 1 + \underbrace{g_{m1} (R_{E1} \parallel R_F)}_{5.02} \right] = 6 \text{ k} \times 6.02 = 36.12 \text{ k}$$


$$\rightarrow Z_{in} = 36.12 \text{ k} \times 15\% = \underline{5.67 \text{ M}\Omega}$$

$$Z_{out} = \frac{Z_o}{1 + af}$$


$$Z_o = \frac{1}{g_{m3}} \parallel 256 \Omega = 30.2 \Omega$$

$$\rightarrow Z_{out} = \frac{30.2}{15\%} = 0.19 \Omega$$

Problem 4 – (10 points)

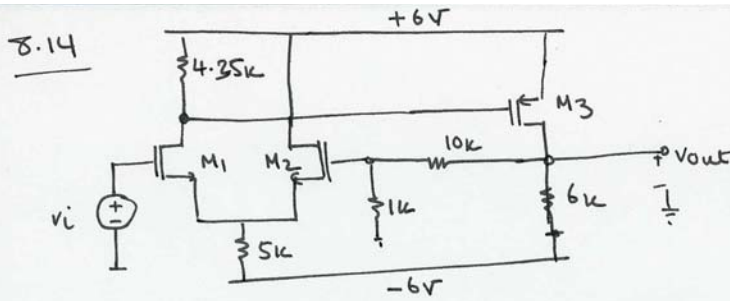

Series-shunt

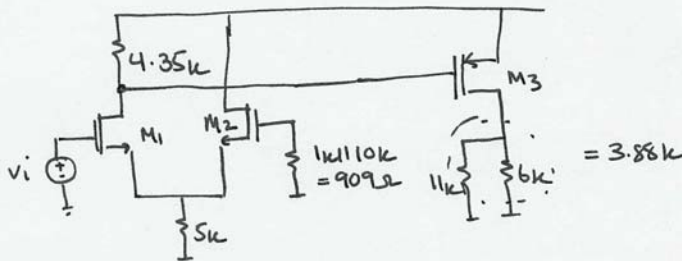

$$I_{D1} = \frac{V_{SG3}}{4.35k}$$

$$I_{D3} = \frac{6 - V_{D3}}{6k} = 1mA$$

$$I_{D3} = \frac{k'_p}{2} \left(\frac{W}{L}\right)_3 (V_{GS3} - V_{TD})^2 \rightarrow |V_{GS3}| = |V_T| = 2V$$

$$\rightarrow I_{D1} = 0.459 mA$$

$$\begin{cases} 5k \times (I_{D2} + I_{D1}) = 6 - V_{GS1} \\ V_{GS1} = 1.39V \end{cases} \rightarrow \begin{cases} I_{D1} + I_{D2} = 0.92 \\ I_{D2} = 0.46 \end{cases} \rightarrow \begin{cases} I_{D1} = 0.46 mA \\ I_{D2} = 0.46 mA \end{cases}$$

$$a = \frac{V_O}{V_i} = A_{V1} \times A_{V2}$$

$$A_{V1} = \frac{V_{D1}}{V_i} = -4.35k \times \frac{g_{m1}}{1 + g_{m1}(5k \parallel \frac{1}{g_{m2}})} = -5.32$$

$$g_{m1} = \sqrt{2k'_n \frac{W}{L} I_{D1}} = 2.35 mS$$

$$g_{m2} = \sqrt{2k'_n \frac{W}{L} I_{D2}} = g_{m1} = 2.35$$

8.14  
Cont.

$$A_{v2} = \frac{v_o}{v_{D1}} = -g_{m3} \times 3.88k = -7.76$$

$$g_{m3} = \sqrt{2\mu_p \times \frac{W}{L} \times I_{D3}} = 2 \text{ mS}$$

$$\rightarrow a = 7.76 \times 5.32 = \underline{\underline{41.27}}$$

$$f = \frac{1}{1+10} = \frac{1}{11}$$

$$T = af = 3.75$$

$$\rightarrow \frac{v_o}{v_i} = A = \frac{41.27}{1+3.75} = 8.68$$


$$z_{in} = \frac{z_i}{(1+T)^{-1}} = z_i(1+T)$$

$$z_i = \infty \rightarrow z_{in} = \infty$$

$$z_{out} = \frac{z_o}{1+T} \rightarrow z_{out} = 816.8 \Omega$$

$$z_o = 3.88k$$

Problem 5 – (10 points)

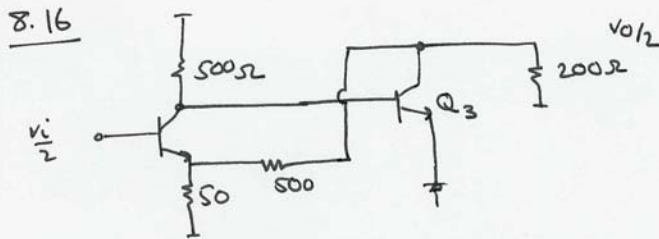

$$f = \frac{50}{50+500} = \frac{1}{11}$$

$$a = \frac{g_{m1}}{1+g_{m1} \times 45\Omega} \times (500\Omega \parallel r_{\pi 3}) \times g_{m3} \times (200\Omega \parallel 550\Omega)$$

$$T = af \quad \downarrow \quad 50 \parallel 500$$

- (a) if the 50Ω resistor increases → f increases  
 a slightly decreases (if  $g_m$  is not too large)  
 → T: increases (if  $g_m$  is too large: T stays almost constant)
- (b) if 500Ω feedback resistor increases → f decreases  
 a slightly decreases  
 → T: decreases
- (c) if 200 resistor increases → f: unchanged  
 a: increases  
 → T: increases

Problem 6 – (10 points)

**8.23**

$$\frac{V_{DD} - V_{GS2}}{10k} = I_{D2} = \frac{30\mu}{2} 20(V_{GS2} - 0.8)^2$$

$$5 - a = 3(a - 0.8)^2$$

$$= 3a^2 - 4.8a + 1.92$$

$$0 = 3a^2 - 3.8a - 3.08$$



$$a = \frac{+3.8 \pm \sqrt{3.8^2 - 4(3)(-3.08)}}{6}$$

$$V_{GS2} = 1.83V$$

$$I_{D2} = \frac{30\mu}{2} 20(1.83 - 0.8)^2$$

$$= 317\mu A = I_{D1} = I_{D5} = I_{D6}$$

small signal

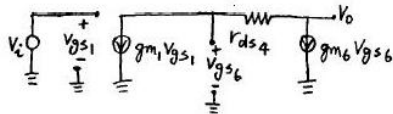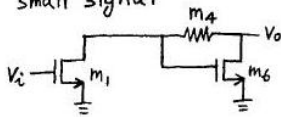

$$V_o = V_{gs6} - g_{m6} V_{gs6} r_{ds4}$$

$$g_{m1} = g_{m6}$$

$$-g_{m1} V_{gs1} = g_{m6} V_{gs6}$$

$$-V_{gs1} = V_{gs6} = -V_i$$

$$V_o = -V_i + g_{m6} V_i r_{ds4}$$

$$\frac{V_o}{V_i} = -1 + g_{m6} r_{ds4}$$

$$g_{m6} = \sqrt{2(317\mu)(60\mu)(20)}$$

$$= 872 \mu A/V$$

$$g_{ds4} = \mu_n C_{ox} \frac{W}{L} (V_{GS4} - V_{t4})$$

$$= 150\mu (V_c - 1.53 - 1.14)$$

$$= 150\mu (V_c - 2.67)$$

$$V_{t4} = V_{t0} + \gamma(\sqrt{V_{SB4} + 2\phi_f} - \sqrt{2\phi_f})$$

$$= 0.8 + 0.5(\sqrt{1.53 + 0.6} - \sqrt{0.6})$$

$$= 1.14V$$

$$V_{SB4} = V_{GS6} = V_{t6} + \sqrt{\frac{2I_{D6}}{\mu C_{ox} \frac{W}{L}_6}}$$

$$= 0.8 + \sqrt{\frac{2(317\mu)}{60\mu(20)}} = 1.53V$$

$$V_c = 3V$$

$$g_{ds4} = 150\mu(3 - 2.67)$$

$$= 49.5\mu$$

$$r_{ds4} = 20.2k$$

$$\frac{V_o}{V_i} = -1 + (872\mu)(20.2k) = 16.6$$

$$V_c = 4V$$

$$g_{ds4} = 150\mu(4 - 2.67)$$

$$= 200\mu$$

$$r_{ds4} = 5.01k$$

$$\frac{V_o}{V_i} = -1 + (872\mu)(5.01k)$$

$$= 3.37$$

$$R_o = \frac{1}{g_{m6}} = \frac{1}{872\mu} = 1.15k\Omega$$

Problem 7 – (10 points)

**B.24**

$$I_{D1} = I_{D2} = \frac{1}{2} I_{D6} = 100 \mu A = I_{D3}$$

$$I_{D8} = 200 \mu A$$

$$a = \frac{1}{2} g_{m1} (2r_{o2} \parallel r_{o3}) \frac{g_{m8} (21k)}{1 + g_{m8} (21k)}$$

$$= \frac{1}{2} (693 \mu) (222k) (0.954)$$

$$= 73.4$$

$$g_{m1} = \sqrt{2(100 \mu)(60 \mu) 40}$$

$$= 693 \mu A/V$$

$$r_{o2} = r_{o3} = \frac{1}{\lambda I_D} = \frac{1}{0.03 (100 \mu)}$$

$$= 333k$$

$$g_{m8} = \sqrt{2(200 \mu)(60 \mu) 40}$$

$$= 980 \mu A/V$$

$$f = \frac{1k}{1k + 20k} = \frac{1}{21}$$

$$T = af = 3.5$$

$$A = \frac{a}{1+T} = \frac{73.4}{4.5} = 16.3 = \frac{V_o}{V_i}$$

$$R_o = \frac{r_{out}}{1+T} = \frac{973}{4.5}$$

$$= 216 \Omega$$

$$r_{out} = 21k \parallel \frac{1}{g_{m8}}$$

$$= 21k \parallel 1.02k$$

$$= 973 \Omega$$

```
VARIABLE GAIN CMOS AMP
VDD 1 0 5V
M1 3 4 0 0 NMOS W=20U L=1U
M2 2 2 1 1 PMOS W=20U L=1U
R1 2 0 10K
M3 3 2 1 1 PMOS W=20U L=1U
M5 5 2 1 1 PMOS W=20U L=1U
M6 5 3 0 0 NMOS W=20U L=1U
M4 5 6 3 0 NMOS W=5U L=2U
VC 6 0 3V
VI 4 0 1.527V
.DC VI 1.47 1.6 0.005
.PLOT DC V(5)
.TF V(5) VI
.NODESET V(2)=3.17V V(3)=1.53V V(5)=1.53V
.MODEL NMOS NMOS KP=60U VTO=0.8 GAMMA=0.5
.MODEL PMOS PMOS KP=30U VTO=-0.8 GAMMA=0.5
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OP
.END
0**** DC TRANSFER CURVES
VI
V(5)
1.00D+00 2.0D+00 3.0D+00 4.0D+00 5.0D+00
1.470D+00 1.065D+00 *
1.475D+00 1.092D+00 *
1.480D+00 1.119D+00 *
1.485D+00 1.149D+00 *
1.490D+00 1.180D+00 *
1.495D+00 1.213D+00 *
1.500D+00 1.248D+00 *
1.505D+00 1.287D+00 *
1.510D+00 1.329D+00 *
1.515D+00 1.376D+00 *
1.520D+00 1.430D+00 *
1.525D+00 1.495D+00 *
1.530D+00 1.580D+00 *
1.535D+00 1.707D+00 *
1.540D+00 4.292D+00 *
1.545D+00 4.463D+00 *
1.550D+00 4.563D+00 *
1.555D+00 4.632D+00 *
1.560D+00 4.683D+00 *
1.565D+00 4.722D+00 *
1.570D+00 4.753D+00 *
1.575D+00 4.777D+00 *
1.580D+00 4.796D+00 *
1.585D+00 4.811D+00 *
1.590D+00 4.822D+00 *
1.595D+00 4.830D+00 *
1.600D+00 4.836D+00 *
```

```
0**** SMALL SIGNAL BIAS SOLUTION
NODE VOLTAGE
( 1) 5.0000 ( 2) 3.1718 ( 3) 1.5271 ( 4) 1.5270
( 5) 1.5259 ( 6) 3.0000
```

```
0**** MOSFETS
0 M1 M2 M3 M5 M6 M4
0MODEL NMOS PMOS PMOS PMOS NMOS NMOS
ID 3.17E-04 -3.17E-04 -3.17E-04 -3.17E-04 3.17E-04 -5.96E-08
VGS 1.527 -1.828 -1.828 -1.828 1.527 1.473
VDS 1.527 -1.828 -3.473 -3.474 1.526 -0.001
VBS 0.000 0.000 0.000 0.000 0.000 -1.527
VTH 0.800 -0.800 -0.800 -0.800 0.800 1.142
VDSAT 0.727 -1.028 -1.028 -1.028 0.727 0.332
GM 8.72E-04 6.17E-04 6.17E-04 6.17E-04 8.73E-04 1.80E-07
GDS 0.00E+0 0.00E+0 0.00E+0 0.00E+0 0.00E+0 4.97E-05
GMB 2.82E-04 1.99E-04 1.99E-04 1.99E-04 2.82E-04 3.08E-08
```

```
0**** SMALL-SIGNAL CHARACTERISTICS
0 V(5)/VI = 1.649D+01
0 INPUT RESISTANCE AT VI = 1.000D+20
0 OUTPUT RESISTANCE AT V(5) = 1.141D+03
```

# 8.24-Cont'd

```

VARIABLE GAIN CMOS AMP
VDD 1 0 5V
M1 3 4 0 0 NMOS W=20U L=1U
M2 2 2 1 1 PMOS W=20U L=1U
R1 2 0 10K
M3 3 2 1 1 PMOS W=20U L=1U
M5 5 2 1 1 PMOS W=20U L=1U
M6 5 3 0 0 NMOS W=20U L=1U
M4 5 6 3 0 NMOS W=5U L=2U
VC 6 0 4V
VI 4 0 1.527V
.DC VI 1.0 1.8 0.05
.PLOT DC V(5)
.TF V(5) VI
.NODESET V(2)=3.17V V(3)=1.53V V(5)=1.53V
.MODEL NMOS NMOS KP=60U VTO=-0.8 GAMMA=0.5
.MODEL PMOS PMOS KP=30U VTO=-0.8 GAMMA=0.5
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OP
.END
0**** DC TRANSFER CURVES
VI          V(5)
0.0D+00    2.0D+00    4.0D+00    6.0D+00    8.0D+00
-----
1.000D+00  7.255D-01  .
1.050D+00  7.496D-01  .
1.100D+00  7.806D-01  .
1.150D+00  8.197D-01  .
1.200D+00  8.687D-01  .
1.250D+00  9.299D-01  .
1.300D+00  1.003D+00  .
1.350D+00  1.089D+00  .
1.400D+00  1.188D+00  .
1.450D+00  1.303D+00  .
1.500D+00  1.441D+00  .
1.550D+00  1.607D+00  .
1.600D+00  1.803D+00  .
1.650D+00  2.038D+00  .
1.700D+00  2.339D+00  .
1.750D+00  4.054D+00  .
1.800D+00  4.132D+00  .
-----
0**** SMALL SIGNAL BIAS SOLUTION
NODE VOLTAGE
( 1) 5.0000 ( 2) 3.1718 ( 3) 1.5271 ( 4) 1.5270
( 5) 1.5268 ( 6) 4.0000

0**** MOSFETS
0      M1      M2      M3      M5      M6      M4
OMODEL NMOS  PMOS  PMOS  PMOS  NMOS  NMOS  NMOS
ID      3.17E-04 -3.17E-04 -3.17E-04 -3.17E-04 3.17E-04 -5.96E-08
VGS     1.527  -1.828  -1.828  -1.828  1.527  2.473
VDS     1.527  -1.828  -3.473  -3.473  1.527  0.000
VBS     0.000  0.000  0.000  0.000  0.000  -1.527
VTH     0.800  -0.800  -0.800  -0.800  0.800  1.142
VDSAT   0.727  -1.028  -1.028  -1.028  0.727  1.331
GM      8.72E-04 6.17E-04 6.17E-04 6.17E-04 8.73E-04 4.48E-08
GDS     0.00E+0 0.00E+0 0.00E+0 0.00E+0 0.00E+0 2.00E-04
GMB     2.82E-04 1.99E-04 1.99E-04 1.99E-04 2.82E-04 7.68E-09

0**** SMALL-SIGNAL CHARACTERISTICS
0 V(5)/VI = 3.369D+00
0 INPUT RESISTANCE AT VI = 1.000D+20
0 OUTPUT RESISTANCE AT V(5) = 1.146D+03

```

```

CMOS FEEDBACK AMP
VDD 1 0 5V
VSS 9 0 -5V
M4 2 2 1 1 PMOS W=20U L=1U
I1 2 3 100UA
M5 3 3 9 9 NMOS W=20U L=1U
M6 6 3 9 9 NMOS W=40U L=1U
M1 1 4 6 9 NMOS W=40U L=1U
M2 5 7 6 9 NMOS W=40U L=1U
M3 5 2 1 1 PMOS W=20U L=1U
M8 1 5 8 9 NMOS W=40U L=1U
M7 8 3 9 9 NMOS W=40U L=1U
RF 8 7 20K
RE 7 0 1K
VI 4 0 0V
.TF V(8) VI
.MODEL NMOS NMOS KP=60U VTO=-0.8 LAMBDA=0.03
.MODEL PMOS PMOS KP=30U VTO=-0.8 LAMBDA=0.03
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OP
.END
0**** SMALL SIGNAL BIAS SOLUTION
NODE VOLTAGE
( 1) 5.0000 ( 2) 3.6341 ( 3) -3.7989 ( 4) -0.0000
( 5) 1.4134 ( 6) -1.0776 ( 7) 0.0096 ( 8) 0.2016
( 9) -5.0000

0**** MOSFETS
0      M4      M5      M6      M1      M2      M3      M8
OMODEL PMOS  NMOS  NMOS  NMOS  NMOS  PMOS  NMOS
ID      -1.00E-04 1.00E-04 2.16E-04 1.09E-04 1.06E-04 -1.06E-04 2.33E-04
VGS     -1.366  1.201  1.201  1.078  1.087  -1.366  1.212
VDS     -1.366  1.201  3.922  6.078  2.491  -3.587  4.798
VBS     0.000  0.000  0.000  -3.922  -3.922  0.000  5.202
VTH     -0.800  0.800  0.800  0.800  0.800  -0.800  0.800
VDSAT   -0.566  0.401  0.401  0.278  0.287  -0.566  0.412
GM      3.54E-04 4.99E-04 1.06E-03 7.88E-04 7.41E-04 3.76E-04 1.13E-03
GDS     2.88E-06 2.90E-06 5.79E-06 2.77E-06 2.97E-06 2.88E-06 6.10E-06

0      M7
OMODEL NMOS
ID      2.23E-04
VGS     1.201
VDS     5.202
VBS     0.000
VTH     0.800
VDSAT   0.401
GM      1.11E-03
GDS     5.79E-06

0**** SMALL-SIGNAL CHARACTERISTICS
0 V(8)/VI = 1.662D+01
0 INPUT RESISTANCE AT VI = 1.000D+20
0 OUTPUT RESISTANCE AT V(8) = 1.707D+02

```

Problem 8 – (10 points)

Solution

$$R_{out}(g_{m2}=0) = 2R \parallel (r_{ds1} + r_{ds2}) = \frac{2R(r_{ds1} + r_{ds2})}{2R + r_{ds1} + r_{ds2}}$$

RR(port shorted) = ?

$$v_r = 0 - v_{s2} = -g_{m2}v_t \left( \frac{r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2}} \right)$$

$$\Rightarrow RR(\text{port shorted}) = \frac{g_{m2}r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2}}$$

RR(port open) = ?

$$v_r = -g_{m2}v_t \left( \frac{r_{ds2}(r_{ds1} + R)}{r_{ds1} + r_{ds2} + 2R} \right)$$


$$\Rightarrow RR(\text{port open}) = \frac{g_{m2}r_{ds2}(r_{ds1} + R)}{r_{ds1} + r_{ds2} + 2R}$$

$$\therefore R_{out} = \frac{2R(r_{ds1} + r_{ds2})}{2R + r_{ds1} + r_{ds2}} \left[ \frac{1 + \frac{g_{m2}r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2}}}{1 + \frac{g_{m2}r_{ds2}(r_{ds1} + R)}{r_{ds1} + r_{ds2} + 2R}} \right] = 2R \left( \frac{r_{ds1} + r_{ds2} + g_{m2}r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2} + 2R + g_{m2}r_{ds2}(r_{ds1} + R)} \right)$$

Using the assumptions of  $g_m > g_{ds} > (1/R)$  we can simplify  $R_{out}$  as


$$R_{out} \approx 2R \left( \frac{g_{m2}r_{ds1}r_{ds2}}{g_{m2}r_{ds2}R} \right) = \underline{\underline{2r_{ds1}}}$$

What is the insight? Well there are two feedback loops, one a series (the normal cascode) and one a shunt. Apparently they are working against each other and the effective output resistance is pretty much what it would be if there were two transistors in series without any feedback.

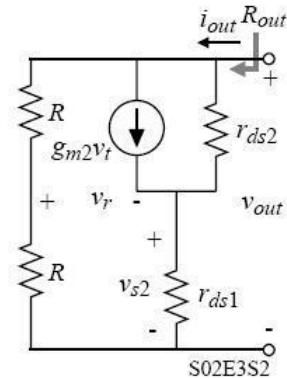

Problem 9- (10 points)

(a)  $g_{m2}$  is the controlled source.

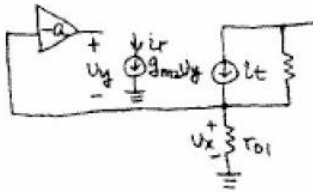

$$R_{out}(g_{m2}=0) = r_{o1} + r_{o2}$$

$$R(\text{short}) = (r_{o1} || r_{o2})(a+1)g_{m2}$$

$$R(\text{open}) = 0$$



$$R_{out} = R_{out}(g_{m2}=0) \frac{1+R(\text{short})}{1+R(\text{open})}$$

$$= (r_{o1} + r_{o2}) \frac{1 + (r_{o1} || r_{o2})(a+1)g_{m2}}{1+0}$$

$$= r_{o1} + r_{o2} + (a+1)g_{m2}r_{o1}r_{o2}$$

$$\approx a g_{m2}r_{o1}r_{o2}$$

(b)  $a$  is the controlled source.

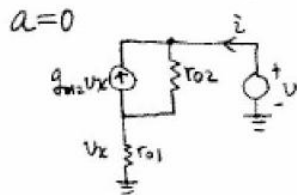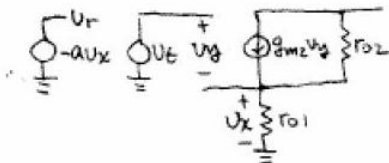

$$\frac{v_x}{r_{o1}} = g_{m2} v_x + \frac{v_x - v}{r_{o2}}$$

$$R_{out}(a=0) = \frac{v}{i} = \frac{v}{v_x / r_{o1}}$$

$$= g_{m2} r_{o1} r_{o2} + r_{o1} - r_{o2}$$

$$\approx g_{m2} r_{o1} r_{o2}$$

The output is short

$$v_x = g_{m2}(v_t - v_x)(r_{o1} || r_{o2})$$

$$v_x = \frac{g_{m2}(r_{o1} || r_{o2})}{1 + g_{m2}(r_{o1} || r_{o2})} v_t$$

$$R(\text{short}) = a \frac{g_{m2}(r_{o1} || r_{o2})}{1 + g_{m2}(r_{o1} || r_{o2})}$$

$$R(\text{open}) = 0 \quad (v_x = 0 \text{ when the output is open})$$

$$R_{out} = R_{out}(a=0) \frac{1+R(\text{short})}{1+R(\text{open})}$$

$$\approx g_{m2} r_{o1} r_{o2} \frac{1 + \frac{g_{m2}(r_{o1} || r_{o2})}{1 + g_{m2}(r_{o1} || r_{o2})}}{1+0}$$

$$\approx a g_{m2} r_{o1} r_{o2}$$


(c) The results are the same, as they should be, even though the terms  $R_{out}(k=0)$ ,  $R(\text{open})$ , and  $R(\text{short})$  differ in (a) and (b).

Problem 10- (10 points)

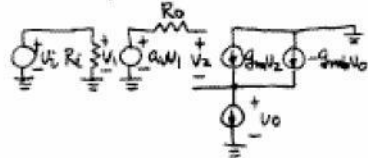8.30

(a)

The basic amplifier without the feedback signal inserted at the inverting input of the op amp



$$g_m = \sqrt{2k \frac{W}{L} I_D} = \sqrt{2 \times 180 \times 10^{-6} \times 100 \times 0.5 \times 10^{-3}}$$

$$= 4.2 \times 10^{-3} \text{ A/V}$$

$$g_{mb} = \frac{\gamma}{2\sqrt{2f_3 + V_{SB}}} g_m = \frac{\gamma}{2\sqrt{2f_3}} g_m$$

$$= \frac{0.3}{2\sqrt{2 \times 0.3}} 4.2 \times 10^{-3} = 6.1 \times 10^{-4} \text{ A/V}$$

$$V_o = g_m(a_v V_i - V_o) \frac{1}{g_{mb}}$$

$$a = \frac{V_o}{V_i} = a_v \frac{g_m}{g_m + g_{mb}}$$

$$f = 1$$


$$a_f = a_v \frac{g_m}{g_m + g_{mb}} = 1000 \frac{4.2}{4.2 + 0.61} = 838$$

$$A = \frac{a}{1 + a_f} = \frac{838}{1 + 838} = 0.999$$

$$r_{ia} = R_i$$

$$R_{in} = r_{ia}(1 + a_f) = R_i(1 + a_f)$$
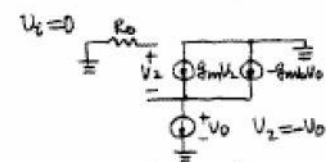
$$= 1 \text{ M}(1 + 838) = 839 \text{ M}\Omega$$




$$r_{oa} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} = \frac{1}{g_m + g_{mb}}$$

$$R_{out} = \frac{r_{oa}}{1 + a_f} = \frac{1}{g_m + g_{mb} (1 + a_f)}$$

$$= \frac{1}{4.2 \times 10^{-3} + 8.1 \times 10^{-4} (1 + 838)}$$

$$= 0.238 \Omega$$

(b)

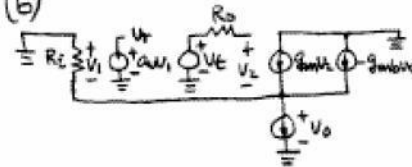

$$V_o = g_m(V_i - V_o) \left( \frac{1}{g_{mb}} \parallel R_i \right)$$

$$V_o = \frac{g_m}{\frac{1}{R_i} + g_m + g_{mb}}$$

$$R = a_v \frac{g_m}{\frac{1}{R_i} + g_m + g_{mb}}$$

$$\approx a_v \frac{g_m}{g_m + g_{mb}}$$

$$= 838$$

$$A_{oo} = \frac{V_o}{V_i} \Big|_{a_v \rightarrow \infty} = 1 \quad (V_i = 0 \text{ and } V_o = V_i)$$

$$d = \frac{V_o}{V_i} \Big|_{a_v \rightarrow \infty} = \frac{\frac{1}{g_m} \parallel \frac{1}{g_{mb}}}{R_i + \frac{1}{g_m} \parallel \frac{1}{g_{mb}}}$$

$$= \frac{1}{g_m + g_{mb}}$$

$$\approx \frac{1}{(g_m + g_{mb}) R_i}$$

$$= \frac{1}{(4.2 \times 10^{-3} + 8.1 \times 10^{-4}) (10^6)}$$

$$= 2.00 \times 10^{-4}$$


$$A = A_{oo} \frac{R}{1 + R} + \frac{d}{1 + R}$$

$$= 1 \frac{838}{1 + 838} + \frac{2.00 \times 10^{-4}}{1 + 838}$$

$$= 0.999$$

8-30 cont.

$$a_v = 0$$

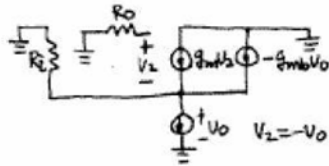

$$R_{in}(a_v=0) = R_i + \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \approx R_i = 1\text{M}\Omega$$

$$R(\text{short}) = R = 838$$

$$R(\text{open}) = 0 \quad (v_1 = 0)$$

$$R_{in} = R_{in}(a_v=0) \frac{1 + R(\text{short})}{1 + R(\text{open})} \approx R_i \frac{1 + R}{1 + 0}$$

$$= R_i(1 + R) = 1\text{M}(1 + 838) = 839\text{M}\Omega$$

$$R_{out}(a_v=0) = R_i \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \approx \frac{1}{g_m} \parallel \frac{1}{g_{mb}}$$

$$= \frac{1}{g_m + g_{mb}} = \frac{1}{4.2 \times 10^{-3} + 8.1 \times 10^{-4}} = 200\Omega$$

$$R(\text{short}) = 0 \quad (v_o = 0)$$

$$R(\text{open}) = R$$

$$R_{out} = R_{out}(a_v=0) \frac{1 + R(\text{short})}{1 + R(\text{open})}$$

$$\approx \frac{1}{g_m + g_{mb}} \frac{1 + 0}{1 + R} = \frac{1}{g_m + g_{mb} (1 + R)}$$

$$= 200 \frac{1}{1 + 838} = 0.238\Omega$$