

Homework Assignment No. 12 Solutions

Problem 1 – (10 points)

Problem 7.5-5. Find the equivalent rms noise voltage of the op amp designed in Example 6.5-2 over a bandwidth of 1Hz to 100kHz. Use the values for KF of Example 7.5-1.

Solution

The circuit for this amplifier is shown.

The W/L ratios in microns are:

$$S_1 = S_2 = 12/1$$

$$S_3 = S_4 = 16/1$$

$$S_5 = 7/1$$

$$S_5 = 8.75/1$$

$$S_6 = S_7 = S_8 = S_{14} \\ = S_{15} = 40/1$$

$$S_9 = S_{10} = S_{11} = \\ S_{12} = 18.2/1$$

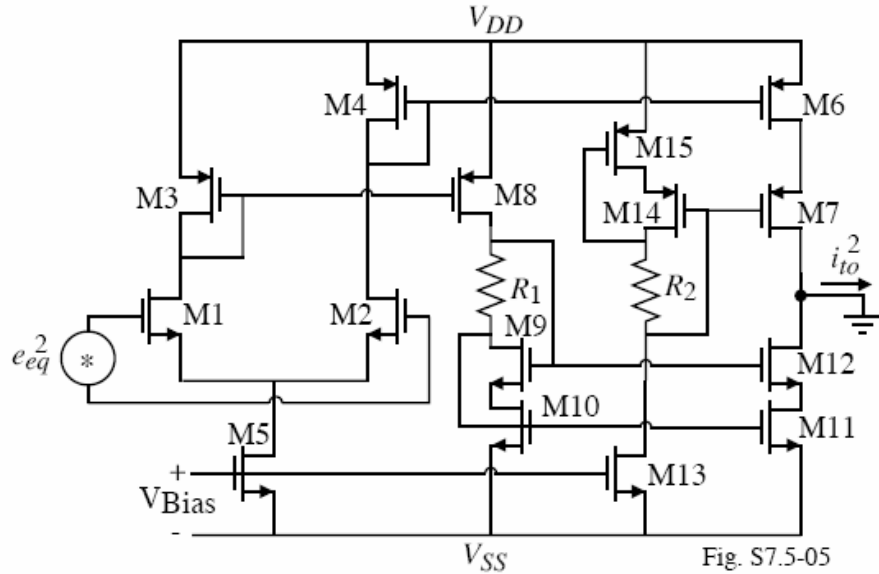


Fig. S7.5-05

Find the short circuit noise current at the output, i_{to}^2 , due to each noise-contributing transistor in the circuit (we will not include M7, M9, M12 and M14 because they are cascodes and their effective g_m is small. The result is,

$$i_{to}^2 = 2g_{m1}^2 e_{n1}^2 \left(\frac{g_{m8}^2}{g_{m3}^2} \right) + 2g_{m8}^2 e_{n3}^2 + 2g_{m8}^2 e_{n8}^2 + 2g_{m11}^2 e_{n10}^2$$

where we have assumed that $g_{m1}=g_{m2}$, $g_{m3}=g_{m4}$, $g_{m6}=g_{m8}$, and $g_{m10}=g_{m11}$ and $e_{n1}=e_{n2}$, $e_{n3}=e_{n4}$, $e_{n6}=e_{n8}$, and $e_{n10}=e_{n11}$. Dividing i_{to}^2 by the transconductance gain gives

$$e_{eq}^2 = \frac{i_{to}^2}{g_{m1}g_{m8}/g_{m3}^2} = 2e_{n1}^2 + 2\left(\frac{g_{m3}^2}{g_{m1}^2}\right)e_{n3}^2 + 2\left(\frac{g_{m3}^2}{g_{m1}^2}\right)e_{n8}^2 + 2\left(\frac{g_{m3}^2g_{m11}^2}{g_{m1}^2g_{m8}^2}\right)e_{n10}^2$$

The values of the various parameters are:

$$g_{m1} = 251\mu S, g_{m3} = 282.5\mu S, g_{m8} = 707\mu S, \text{ and } g_{m11} = 707\mu S.$$

$$\therefore e_{eq}^2 = 2e_{n1}^2 \left[1 + 1.266 \left(\frac{e_{n3}^2}{e_{n1}^2} + \frac{e_{n8}^2}{e_{n1}^2} + \frac{e_{n10}^2}{e_{n1}^2} \right) \right]$$

Problem 7.5-5 – Continued

1/f Noise:

Using the results of Ex. 7.5-1 we get $B_N = 7.36 \times 10^{-22} (\text{V}\cdot\text{m})^2$ and $B_p = 2.02 \times 10^{-22} (\text{V}\cdot\text{m})^2$

$$e_{n1}^2 = \frac{B_N}{fW_1L_1} = \frac{7.36 \times 10^{-22}}{f \cdot 12 \times 10^{-12}} = \frac{6.133 \times 10^{-11}}{f} \text{ V}^2/\text{Hz}$$

$$\frac{e_{n3}^2}{e_{n1}^2} = \frac{B_P f W_1 L_1}{B_N f W_3 L_3} = \frac{B_P W_1 L_1}{B_N W_3 L_3} = \frac{2.02 \cdot 12}{7.36 \cdot 16} = 0.2058$$

$$\frac{e_{n8}^2}{e_{n1}^2} = \frac{B_P f W_1 L_1}{B_N f W_8 L_3} = \frac{B_P W_1 L_1}{B_N W_8 L_3} = \frac{2.02 \cdot 12}{7.36 \cdot 40} = 0.0823$$

$$\frac{e_{n10}^2}{e_{n1}^2} = \frac{B_N f W_1 L_1}{B_N f W_{10} L_{10}} = \frac{B_P W_1 L_1}{B_N W_3 L_3} = \frac{12}{18.2} = 0.6593$$

$$\therefore e_{eq}^2 = 2 \frac{6.133 \times 10^{-11}}{f} [1 + 1.266(0.2058 + 0.0823 + 0.6593)] = 2 \frac{6.133 \times 10^{-11}}{f} 2.1995$$

$$e_{eq}^2 = \frac{2.1995 \times 10^{-10}}{f} \text{ V}^2/\text{Hz}$$

Thermal noise:

$$e_{n1}^2 = \frac{8kT}{3g_{m1}} = \frac{8 \cdot 1.38 \times 10^{-23} \cdot 300}{3 \cdot 251 \times 10^{-6}} = 4.398 \times 10^{-17} \text{ V}^2/\text{Hz}$$

$$\frac{e_{n3}^2}{e_{n1}^2} = \frac{g_{m1}}{g_{m3}} = \frac{251}{282.4} = 0.8888 \quad \text{and} \quad \frac{e_{n8}^2}{e_{n1}^2} = \frac{e_{n10}^2}{e_{n1}^2} = \frac{g_{m1}}{g_{m8}} = \frac{251}{707} = 0.355$$

The corner frequency is $f_c = 2.698 \times 10^{-10} / 2.66 \times 10^{-16} = 1.01 \times 10^6$ Hz. Therefore in a 1Hz to 100kHz band, the noise is $1/f$. Solving for the *rms* value gives,

$$\begin{aligned} V_{eq}^2(\text{rms}) &= \int_1^{100,000} \frac{2.698 \times 10^{-10}}{f} df = 2.698 \times 10^{-10} [\ln(100,000) - \ln(1)] \\ &= 3.1062 \times 10^{-9} \text{ V}^2(\text{rms}) \end{aligned}$$

$$\therefore V_{eq}(\text{rms}) = \underline{55.73 \mu\text{V}(\text{rms})}$$

Problem 2 – (10 points)

Applying the half-circuit principle, it can be seen that each ½ circuit consists of a cascade of two common-source (CS) stages – the first with a diode connected PMOS load and the other with an NMOS load.

The half circuit representation is shown along-side.

The gain of the first stage is:

$$A_{v1} = G_m R_{out} = \frac{g_{m1}}{g_{m3}}$$

In general for a CS stage with an active load, the primary noise contributors can be represented as shown below (for the second CS stage in the problem). From the figure along-side, we have:

$$i_{n5}^{-2} = 4kT \left(\frac{2}{3} \right) g_{m5} + \frac{K_P g_{m5}^2}{C_{OX} (WL)_5 f}$$

$$i_{n7}^{-2} = 4kT \left(\frac{2}{3} \right) g_{m7} + \frac{K_N g_{m7}^2}{C_{OX} (WL)_7 f}$$

Therefore the input referred noise at the gate of M5 is given by:

$$v_{o1}^{-2} = \frac{i_{n5}^2 + i_{n7}^2}{g_{m5}^2}$$

Similarly, the noise at the gate of M1 due to M1 and diode connected M3 can be expressed as:

$$v_{in(1,3)}^{-2} = \frac{i_{n1}^2 + i_{n3}^2}{g_{m1}^2}$$


$$\text{Where, } i_{n1}^{-2} = 4kT \left(\frac{2}{3} \right) g_{m1} + \frac{K_N g_{m1}^2}{C_{OX} (WL)_1 f} \text{ and } i_{n3}^{-2} = 4kT \left(\frac{2}{3} \right) g_{m3} + \frac{K_P g_{m3}^2}{C_{OX} (WL)_3 f}$$

Therefore the total noise referred to the input (gate of M1) is:

$$v_{in}^{-2} = v_{in(1,3)}^{-2} + \frac{v_{o1}^2}{A_{v1}^2} = \frac{(i_{n1}^2 + i_{n3}^2)}{g_{m1}^2} + \frac{(i_{n5}^2 + i_{n7}^2) \times g_{m3}^2}{g_{m5}^2 \times g_{m1}^2}. \text{ Therefore for one half-circuit,}$$

$$v_{in}^{-2} = \frac{g_{m5}^2 \times (i_{n1}^2 + i_{n3}^2) + (i_{n5}^2 + i_{n7}^2) \times g_{m3}^2}{g_{m5}^2 \times g_{m1}^2}$$

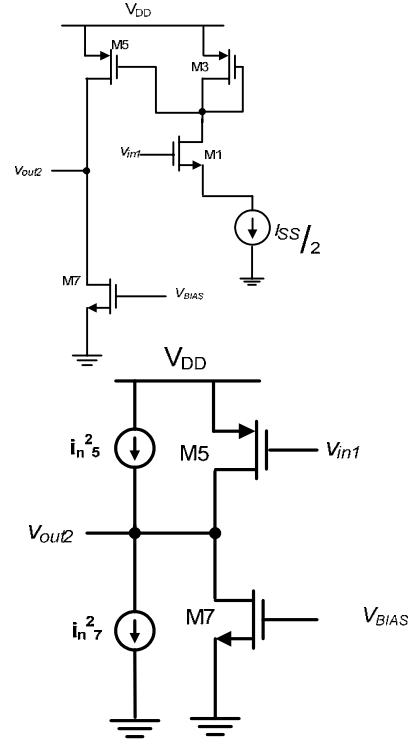Considering only the thermal noise, the total input referred noise is:



$$V_{in(THERMAL)}^{-2} = 2 \times \frac{g_{m5}^2 \left[4kT \left(\frac{2}{3} \right) (g_{m1} + g_{m3}) \right] + g_{m3}^2 \left[4kT \left(\frac{2}{3} \right) (g_{m5} + g_{m7}) \right]}{g_{m5}^2 \times g_{m1}^2}$$

Considering only the flicker noise, the total input referred noise is:

$$V_{in(FLICKER)}^{-2} = 2 \times \frac{g_{m5}^2 \left[\frac{K_N g_{m1}^2}{C_{OX}(WL)_1 f} + \frac{K_P g_{m3}^2}{C_{OX}(WL)_3 f} \right] + g_{m3}^2 \left[\frac{K_P g_{m5}^2}{C_{OX}(WL)_5 f} + \frac{K_N g_{m7}^2}{C_{OX}(WL)_7 f} \right]}{g_{m5}^2 \times g_{m1}^2}$$

Equating the thermal noise and flicker noise to find the flicker noise corner frequency (f_c), we have:

$$\left\{ g_{m5}^2 \left[\frac{K_N g_{m1}^2}{C_{OX}(WL)_1} + \frac{K_P g_{m3}^2}{C_{OX}(WL)_3} \right] + g_{m3}^2 \left[\frac{K_P g_{m5}^2}{C_{OX}(WL)_5} + \frac{K_N g_{m7}^2}{C_{OX}(WL)_7} \right] \right\} \frac{1}{f_c} = g_{m5}^2 \left[4kT \left(\frac{2}{3} \right) (g_{m1} + g_{m3}) \right] + g_{m3}^2 \left[4kT \left(\frac{2}{3} \right) (g_{m5} + g_{m7}) \right]$$

Numerical Calculations:

All transistors in saturation,

$(W/L)_{1,2} = 50/0.6$, $(W/L)_{3,4} = 10/0.6$, $(W/L)_{5,6} = 20/0.6$ and $(W/L)_{7,8} = 56/0.6$

$\mu_n C_{OX} = 75 \mu A/V^2$ and $\mu_p C_{OX} = 30 \mu A/V^2$ and $I_{SS} = 0.5 \text{ mA}$

Therefore $\rightarrow I_1 = I_2 = I_3 = I_4 = 0.25 \text{ mA}$ and $I_5 = I_6 = I_7 = I_8 = 0.5 \text{ mA}$

Using $g_m = \sqrt{2\mu C_{OX} \left(\frac{W}{L} \right) I_D}$, we obtain:

$$g_{m1} = g_{m2} = 1.768 \text{ mS}$$

$$g_{m3} = g_{m4} = 0.5 \text{ mS}$$

$$g_{m5} = g_{m6} = 1 \text{ mS}$$

$$g_{m7} = g_{m8} = 2.646 \text{ mS}$$

Using the above, we obtain, the following values for the thermal and flicker noise powers

$$V_{in(THERMAL)}^{-2} = 2.247 \times 10^{-17} \text{ V}^2 / \text{Hz}$$

Assuming $t_{ox} = 100 \text{ \AA}$, we obtain $C_{OX} = 34.53 \times 10^{-4}$. Therefore the total flicker noise is given by:

$$V_{in(FLICKER)}^{-2} = \frac{3.2417 \times 10^{-8}}{f} \text{ V}^2 / \text{Hz}$$

Equating the noise powers to find the flicker noise corner frequency, we obtain: $f_c = 1.44 \text{ GHz}$.

Problem 3 – (10 points)

Assumptions:

- $V_{OD} = V_{GS} - V_{TH}$
- Only thermal noise of drain current considered

Also, we know for a MOS transistor, we have:

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2I_D}{V_{OD}} \quad \text{and} \quad r_o = \frac{1}{\lambda I_D}$$

Dynamic range of the circuit is defined as:

$$DR = \frac{V_{out-swing}}{V_{noise-out}}$$

where $V_{out-swing}$ is the maximum output voltage swing of the amplifier and $V_{noise-out}$ is the total output referred voltage noise.

We know for a folded cascode amplifier,

$$G_m = g_{m1}$$

and

$$R_{out} = g_{m4} r_{o4} r_{o5} \parallel g_{m2} r_{o2} (r_{o1} \parallel r_{o3}),$$

which on expansion, yields

$$R_{out} = \frac{g_{m2} g_{m4} r_{o1} r_{o2} r_{o3} r_{o4} r_{o5}}{g_{m4} r_{o4} r_{o5} (r_{o1} + r_{o3}) + g_{m2} r_{o1} r_{o2} r_{o3}}$$

Since from the above, we see that **both** G_m and R_{out} are dependent on the over-drive voltage, we need to consider the effect of variation of V_{OD} on both. Substituting for g_m and R_{out} in terms of V_{OD} , we obtain the following expressions for G_m and R_{out}

$$G_m = g_{m1} = \frac{2I_D}{V_{OD}}$$

$$R_{out} = \frac{2}{5} \times \frac{1}{V_{OD} \lambda^2 I_D}$$


Expression for output swing in terms of the over-drive voltage:

Output swing of a folded cascode amplifier:

$$V_{out-swing} = V_{DD} - 4V_{OD}$$

Expression for the output referred noise as a function of over-drive voltage:

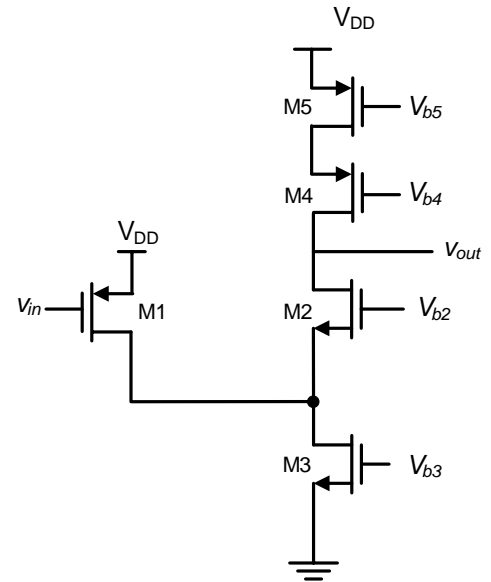The major noise contributors in the folded cascode amplifier are: M1, M3 and M5. Therefore we first obtain the noise contributions of each of these noise sources at the output.



$$v_{n-out(1)}^{-2} = \left[4kT \left(\frac{2}{3g_{m1}} \right) \right] \times g_{m1}^2 R_{out}^2$$

$$v_{n-out(3)}^{-2} = \left[4kT \left(\frac{2}{3g_{m3}} \right) \right] \times g_{m3}^2 R_{out}^2$$

$$v_{n-out(5)}^{-2} = \left[4kT \left(\frac{2}{3g_{m5}} \right) \right] \times g_{m5}^2 R_{out}^2$$

Therefore taking the superposition of these noise sources, we have the output referred noise given by:

$$v_{n-out}^{-2} = 4kT \left(\frac{2}{3} \right) \times [g_{m1} + g_{m3} + g_{m5}] \times R_{out}^2$$

Therefore substituting expressions for g_m and R_{out} into the above, we obtain the total output referred noise power as:

$$v_{n-out}^{-2} = 4kT \times \left(\frac{2}{3} \right) \times \left(\frac{32}{25} \right) \times \frac{1}{V_{OD}^3 \lambda^4 I_D}$$

Therefore the output referred noise voltage can be expressed as a function of V_{OD} as:

$$v_{n-out} = B \times \frac{1}{(V_{OD})^{3/2}}$$

Dynamic Range calculations:

Initial expression for the dynamic range (DR_1):

$$DR_1 = \frac{(V_{DD} - 4V_{OD})(V_{OD})^{3/2}}{B}$$

After the over-drive voltage changes to 75% of its original value, the new dynamic range (DR_2) is given by:

$$DR_2 = \frac{(V_{DD} - 3V_{OD}) \left(\frac{3}{4} V_{OD} \right)^{3/2}}{B}$$

Therefore, finding the difference between the initial and final dynamic ranges, we can find the variation in the dynamic range caused by 25% reduction in V_{OD}

$$\Delta DR = DR_1 - DR_2 = \frac{(V_{OD})^{3/2}}{B} \left[\frac{V_{DD} - 7V_{OD}}{4} \right]$$

Problem 4 – (10 points)

Problem 7.6-1 - If the W and L of all transistor in Fig. 7.6-3 are $100\mu\text{m}$ and $1\mu\text{m}$, respectively, find the lowest supply voltage that gives a zero value of $ICMR$ if the dc current in M5 is $100\mu\text{A}$.

Solution:

$$I_5 = 100 \mu\text{A}, \text{ and } \left(\frac{W}{L}\right) = 100$$

$$V_{IC}(\text{max}) = V_{DD} + V_{T1}(\text{min}) - V_{dsat3}$$

and, $V_{IC}(\text{min}) = V_{dsat1} + V_{T1}(\text{max}) + V_{dsat5}$

The input common-mode range is

$$ICMR = V_{IC}(\text{max}) - V_{IC}(\text{min})$$

For $ICMR=0$

$$V_{DD} = V_{dsat1} + V_{dsat5} + V_{dsat3} + V_{T1}(\text{max}) - V_{T1}(\text{min})$$

or,
$$V_{DD} = \sqrt{\frac{2I_1}{K'_N S_1}} + \sqrt{\frac{2I_5}{K'_N S_5}} + \sqrt{\frac{2I_3}{K'_P S_3}} + V_{T1}(\text{max}) - V_{T1}(\text{min})$$

or,
$$V_{DD} = \underline{0.671\text{V}}$$

Problem 5 – (10 points)

Problem 7.4-3 - Derive Eq. (17). If $A = 2$, at what value of v_{in}/nV_t will $i_{out} = 5I_5$ or $5I_b$ if $b=1$?

Solution

Start with the following relationships:

$$i_1 + i_2 = I_5 + A(i_2 - i_1) \quad \text{Eq. (15)}$$

and $\frac{i_2}{i_1} = \exp\left(\frac{v_{in}}{nV_t}\right)$ Eq. (16)

Defining $i_{out} = b(i_2 - i_1)$ solve for i_2 and I_1 .

$$i_1 + i_1 \exp\left(\frac{v_{in}}{nV_t}\right) = I_5 + Ai_1 \exp\left(\frac{v_{in}}{nV_t}\right) - Ai_1$$

or $i_1[(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)] = I_5 \quad \rightarrow \quad i_1 = \frac{I_5}{(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)}$

Similarly for i_2 ,

$$i_2 = \frac{I_5 \exp\left(\frac{v_{in}}{nV_t}\right)}{(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)}$$

$$\therefore i_{out} = b(i_2 - I_1) = i_{out} = (i_2 - I_1) = \frac{I_5 \left(\exp\left(\frac{v_{in}}{nV_t}\right) - 1 \right)}{(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)} \quad \text{Eq. (17)}$$

Setting $i_{out} = 5I_5$ and solving for $\frac{v_{in}}{nV_t}$ gives,

$$5[3 - \exp\left(\frac{v_{in}}{nV_t}\right)] = \exp\left(\frac{v_{in}}{nV_t}\right) - 1 \quad \rightarrow \quad 16 = 6 \exp\left(\frac{v_{in}}{nV_t}\right) \quad \rightarrow \quad \exp\left(\frac{v_{in}}{nV_t}\right) = 2.667$$

$$\therefore \frac{v_{in}}{nV_t} = \ln(2.667) = \underline{\underline{0.9808}}$$