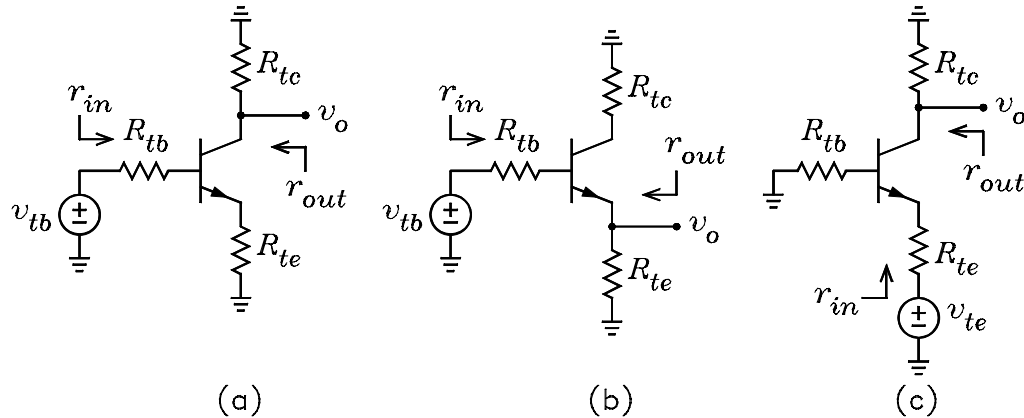


ECE3040 – Assignment 7

1. This problem illustrates several different methods for solving the single-stage amplifier circuits. Some are more difficult than others, but all give the same numerical answers when numbers are used.



(a) Figure (a) shows a common-emitter amplifier.

1. If  $R_{te} = 0$ , use the pi model with  $i'_c = g_m v_{be}$ , voltage division, and Ohm's Law to show that

$$v_o = g_m \times \frac{v_{tb} r_\pi}{R_{tb} + r_\pi} \times [-(r_o \parallel R_{tc})]$$

Show that  $r_{in} = R_{tb} + r_\pi$  and  $r_{out} = r_o \parallel R_{tc}$ .

2. If  $R_{te} = 0$ , use the pi model with  $i'_c = \beta i_b$  and Ohm's Law to show that

$$v_o = \beta \times \frac{v_{tb}}{R_{tb} + r_\pi} \times [-(r_o \parallel R_{tc})]$$

3. Show that the two above answers are equivalent. To show this, you must use  $\beta = g_m r_\pi$ .
4. If  $R_{te} = 0$ , use the simplified T model with  $i'_c = \alpha i'_e$  and Ohm's Law to show that

$$v_o = \alpha \times \frac{v_{tb}}{r'_e} \times [-(r_o \parallel R_{tc})] \quad r'_e = \frac{R_{tb}}{1 + \beta} + r_e$$

5. If  $R_{te} \neq 0$  and  $r_o = \infty$ , use the simplified T model to show that  $v_o$  is given by

$$v_o = -v_{tb} \frac{\alpha R_{tc}}{r'_e + R_{te}} \quad r'_e = \frac{R_{tb}}{1 + \beta} + r_e$$

(b) Figure (b) shows a common-collector amplifier.

1. Use superposition, voltage division, and Ohm's Law with the pi model to show that

$$\begin{aligned} v_{be} &= v_{tb} \frac{r_\pi}{R_{tb} + r_\pi} - v_o \frac{r_\pi}{R_{tb} + r_\pi} \\ v_o &= v_{tb} \frac{r_o \parallel R_{te}}{R_{tb} + r_\pi + r_o \parallel R_{te}} + i'_c [r_o \parallel R_{te} \parallel (r_\pi + R_{tb})] \end{aligned}$$

Use the equation  $i'_c = g_m v_{be}$  and the above two equations to show that

$$v_o = v_{tb} \frac{\frac{r_0 \| R_{te}}{R_{tb} + r_\pi + r_0 \| R_{te}} + g_m \frac{r_\pi}{R_{tb} + r_\pi} [r_0 \| R_{te} \| (r_\pi + R_{tb})]}{1 + g_m \frac{r_\pi}{R_{tb} + r_\pi} [r_0 \| R_{te} \| (r_\pi + R_{tb})]}$$

Show that  $r_{in} = R_{tb} + r_{ib}$ , where  $r_{ib} = r_\pi + (1 + \beta)(r_0 \| R_{te})$ .

2. Use voltage division with the simplified T model to show that

$$v_o = v_{tb} \frac{r_0 \| R_{te}}{r'_e + r_0 \| R_{te}} \quad r'_e = \frac{R_{tb}}{1 + \beta} + r_e$$

Which is the simpler solution, this one or the one above? Show that  $r_{out} = r'_e \| r_0 \| R_{te}$ .

3. Can you show that the above two answers for  $v_o$  are the same? You must use  $\beta = g_m r_\pi$  and  $r_e = r_\pi / (1 + \beta)$  to do this.

(c) Figure (c) shows a common-base amplifier.

1. For  $R_{tb} = 0$  and  $r_0 = \infty$ , use the pi model with  $i'_c = g_m v_{be}$ , superposition, voltage division, and Ohm's Law to show that

$$v_{be} = -v_{te} \frac{r_\pi}{R_{te} + r_\pi} - i'_c (R_{te} \| r_\pi) = -v_{te} \frac{r_\pi}{R_{te} + r_\pi} - g_m v_{be} (R_{te} \| r_\pi)$$

Solve this equation to obtain

$$v_{be} = -v_{te} \frac{\frac{r_\pi}{R_{te} + r_\pi}}{1 + g_m (R_{te} \| r_\pi)}$$

Show that  $v_o$  is given by

$$v_o = +v_{te} \frac{\frac{g_m r_\pi}{R_{te} + r_\pi} R_{tc}}{1 + g_m (R_{te} \| r_\pi)}$$

2. For  $R_{tb} = 0$  and  $r_0 = \infty$ , use the T model and Ohm's Law to show that

$$i'_e = \frac{-v_{te}}{R_{te} + r_e}$$

Show that  $v_o$  is given by

$$v_o = +v_{te} \frac{\alpha R_{tc}}{R_{te} + r_e}$$

Show that  $r_{in} = R_{te} + r_e$  and  $r_{out} = R_C$ .

3. Show that the two above answers for  $v_o$  are equivalent. To do this, you must use  $\beta = g_m r_\pi$  and  $\alpha = \beta / (1 + \beta)$
4. For  $R_{tb} \neq 0$  and  $r_0 = \infty$ , use the simplified T model to show that


$$i'_e = -\frac{v_{te}}{R_{te} + r'_e} \quad r'_e = \frac{R_{tb}}{1 + \beta} + r_e$$

Show that  $v_o$  is given by


$$v_o = +v_{te} \frac{\alpha R_{tc}}{R_{te} + r'_e}$$

For  $R_{tb} = 0$ , show that this reduces to the answer obtained with the T model. Show that  $r_{in} = R_{te} + r'_e$ .

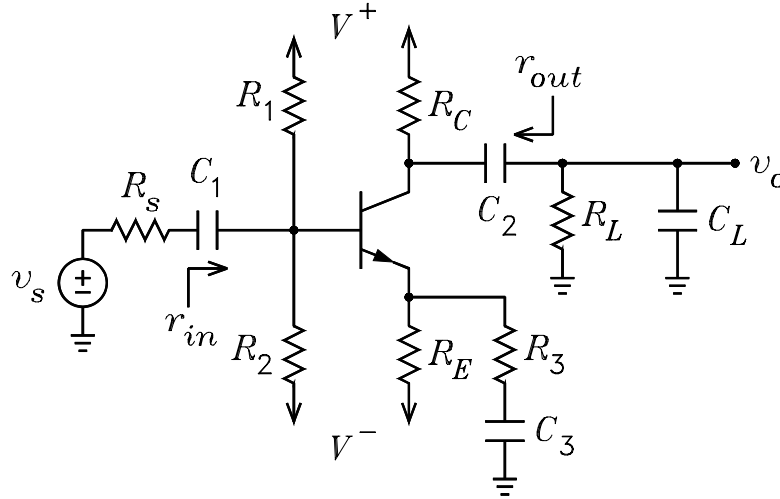
2. The figure shows a CE amplifier. For the dc analysis, all capacitors are open circuits. For the ac signal analysis,  $C_1$ ,  $C_2$ , and  $C_3$  are to be considered to be short circuits.  $C_L$  represents the load capacitance which is usually negligible in the frequency band of interest. It is to be considered to be an open circuit for the ac signal analysis. It is given that  $R_1 = 430\text{ k}\Omega$ ,  $R_2 = 30\text{ k}\Omega$ ,  $R_3 = 0$ ,  $R_C = 12\text{ k}\Omega$ ,  $R_E = 1\text{ k}\Omega$ ,  $R_s = 1.2\text{ k}\Omega$ ,  $R_L = 20\text{ k}\Omega$ ,  $\beta = 99$ ,  $r_0 = 50\text{ k}\Omega$ ,  $V_{BE} = 0.65\text{ V}$ ,  $V_T = 25\text{ mV}$ ,  $V^+ = 24\text{ V}$ , and  $V^- = -24\text{ V}$ .



- Show that  $V_{BB} = -20.87\text{ V}$ ,  $R_{BB} = 28.04\text{ k}\Omega$ ,  $I_E = 1.937\text{ mA}$ ,  $V_C = 0.986\text{ V}$ ,  $V_B = -21.41\text{ V}$ , and  $V_{CB} = 22.4\text{ V}$ .
  - Show that  $v_{tb} = 0.959v_s$ ,  $R_{tb} = 1.151\text{ k}\Omega$ ,  $R_{te} = 0$ , and  $R_{tc} = 7.5\text{ k}\Omega$ .
  - Use all four expressions from problem 1a to show that  $v_o = -253.6v_s$ .
  - If  $R_s = 0$ , show that  $v_o = -500.3v_s$ . What is the main reason the gain changes so much for this case?
  - Show that  $r_{in} = 1.069\text{ k}\Omega$  and  $r_{out} = 9.677\text{ k}\Omega$ .
3. The figure shows a CC amplifier. For the dc analysis, all capacitors are open circuits. For the ac signal analysis,  $C_1$  and  $C_2$  are to be considered to be short circuits. It is given that  $R_1 = 183.5\text{ k}\Omega$ ,  $R_2 = 593\text{ k}\Omega$ ,  $R_E = 5.8\text{ k}\Omega$ ,  $R_s = 1.2\text{ k}\Omega$ ,  $R_L = 20\text{ k}\Omega$ ,  $\beta = 99$ ,  $r_0 = 50\text{ k}\Omega$ ,  $V_{BE} = 0.65\text{ V}$ ,  $V_T = 25\text{ mV}$ ,  $V^+ = 24\text{ V}$ , and  $V^- = -24\text{ V}$ .

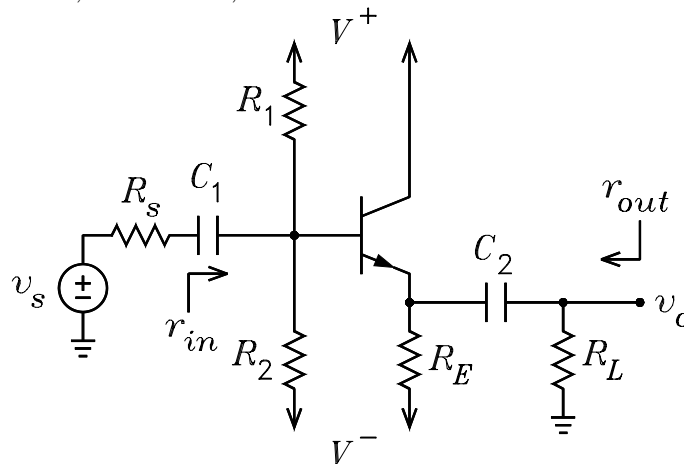

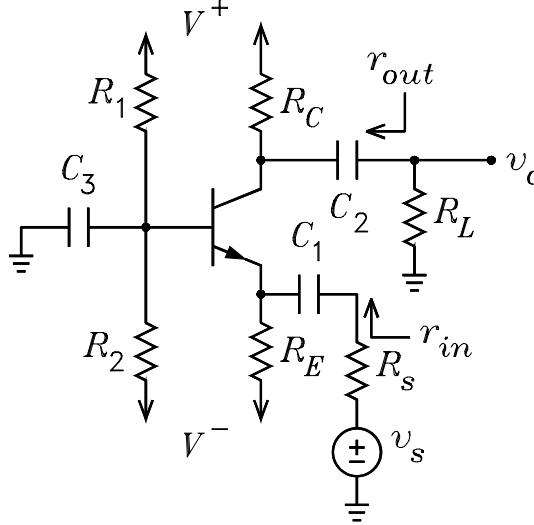- (a) Show that  $V_{BB} = 12.66 \text{ V}$ ,  $R_{BB} = 140.1 \text{ k}\Omega$ ,  $I_E = 5 \text{ mA}$ ,  $V_C = 24 \text{ V}$ ,  $V_B = 5.65 \text{ V}$ , and  $V_{CB} = 18.35 \text{ V}$ .
- (b) Show that  $v_{tb} = 0.992v_s$ ,  $R_{tb} = 1.19 \text{ k}\Omega$  and  $R_{te} = 4.496 \text{ k}\Omega$ .
- (c) Use all three expressions from problem 1b to show that  $v_o = 0.988v_s$ .
- (d) If  $R_s = 0$ , show that  $v_o = 0.996v_s$ .
- (e) Show that  $r_{in} = 106.9 \text{ k}\Omega$  and  $r_{out} = 16.83 \Omega$ .
4. The figure shows a CE amplifier. For the dc analysis, all capacitors are open circuits. For the ac signal analysis,  $C_1$ ,  $C_2$ , and  $C_3$  are to be considered to be short circuits. It is given that  $R_1 = 430 \text{ k}\Omega$ ,  $R_2 = 30 \text{ k}\Omega$ ,  $R_3 = 0$ ,  $R_C = 12 \text{ k}\Omega$ ,  $R_E = 1 \text{ k}\Omega$ ,  $R_s = 50 \Omega$ ,  $R_L = 20 \text{ k}\Omega$ ,  $\beta = 99$ ,  $r_0 = \infty$ ,  $V_{BE} = 0.65 \text{ V}$ ,  $V_T = 25 \text{ mV}$ ,  $V^+ = 24 \text{ V}$ , and  $V^- = -24 \text{ V}$ .



- (a) Show that  $V_{BB} = -20.87 \text{ V}$ ,  $R_{BB} = 28.04 \text{ k}\Omega$ ,  $I_E = 1.937 \text{ mA}$ ,  $V_C = 0.986 \text{ V}$ ,  $V_B = -21.41 \text{ V}$ , and  $V_{CB} = 22.4 \text{ V}$ .
- (b) Show that  $v_{te} = 0.952v_s$ ,  $R_{te} = 47.62 \Omega$ ,  $R_{tb} = 0$ , and  $R_{tc} = 7.5 \text{ k}\Omega$ .
- (c) Use all three expressions from problem 1c to show that  $v_o = 116.8v_s$ .
- (d) If  $R_s = 0$ , show that  $v_o = -575.3v_s$ . What is the main reason the gain changes so much for this case?
- (e) Show that  $r_{in} = 12.74 \Omega$  and  $r_{out} = 12 \text{ k}\Omega$ .