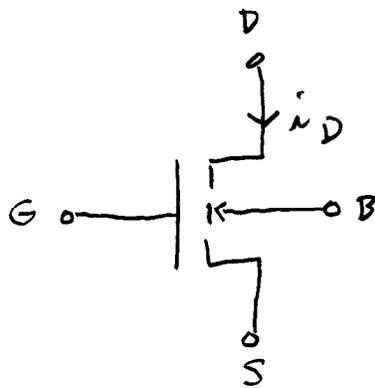


6/14/4

①

Modeling the Body Effect

The pi model must be modified if the body is not connected to the source.



$$i_D = k (v_{GS} - V_{TH})^2$$

$$V_{TH} = V_{T0} + \gamma \left[\sqrt{\phi - v_{BS}} - \sqrt{\phi} \right]$$

If v_{BS} varies, V_{TH} varies and i_D varies. We define the body transconductance as follows

$$g_{mb} = \frac{di_D}{dv_{BS}}$$

This can be shown to be

6/14/4 (2)

$$g_{mb} = \frac{\gamma}{2\sqrt{\phi - V_{BS}}} \cdot 2\sqrt{K I_D}$$

We define the transconductance ratio as η

$$\eta = \frac{g_{mb}}{g_m}$$

where $g_m = 2\sqrt{K I_D}$. It follows that η is given by


$$\eta = \frac{\gamma}{2\sqrt{\phi - V_{BS}}}$$

The small-signal drain current is given by

$$i_d = g_m v_{gs} + g_{mb} v_{bs} + \frac{v_{ds}}{r_o}$$

The pi model can be redrawn as follows:


6/14/4 (3)

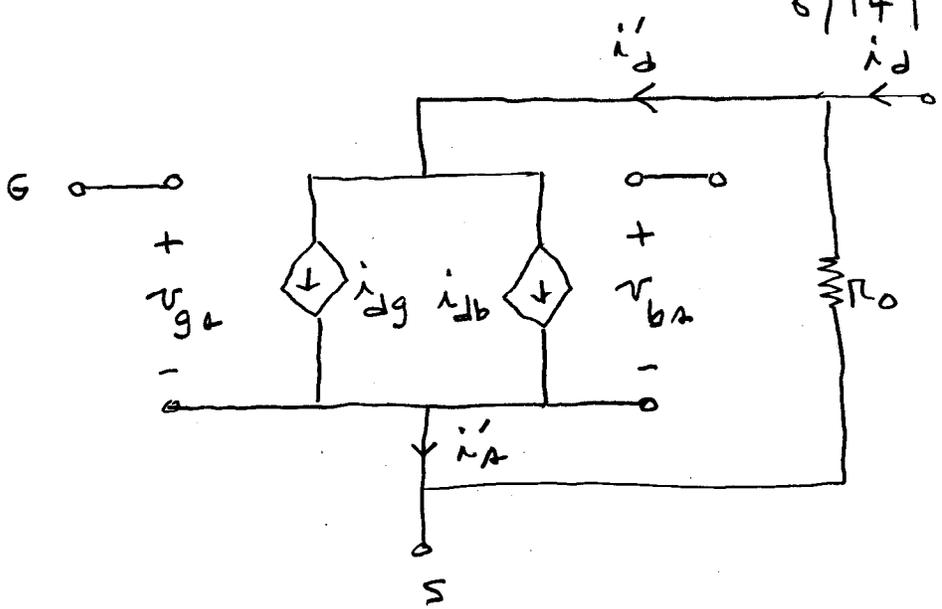

$$i_{dg} = g_m v_{gA}$$

$$i_{db} = g_{mb} v_{bA} = \eta g_m v_{bA}$$

The corresponding T model is

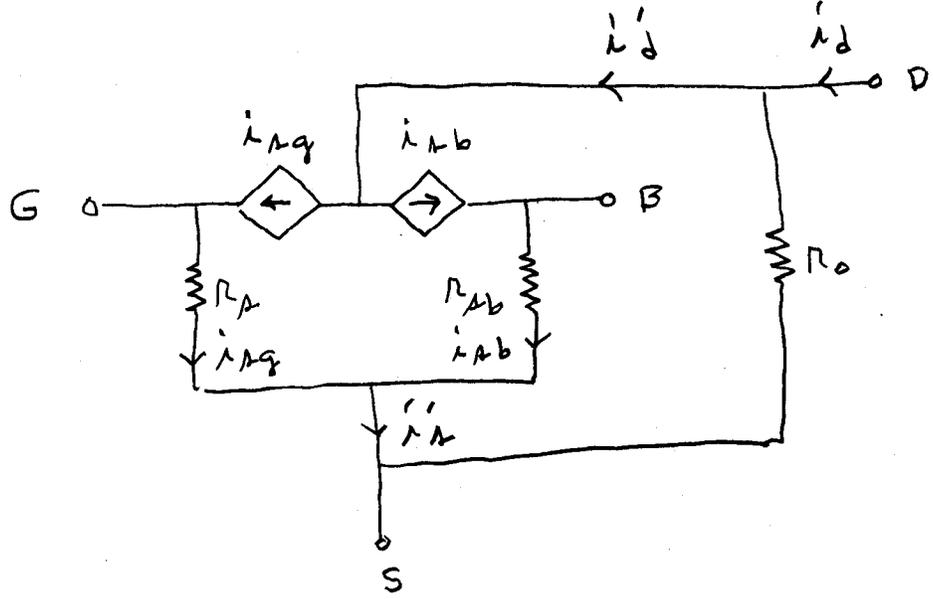


where

$$R_A = \frac{1}{g_m} \quad R_{AB} = \frac{1}{g_{mb}} = \frac{1}{\eta g_m} = \frac{R_A}{\eta}$$

6/14/4 (4)

The Common-Source Amplifier

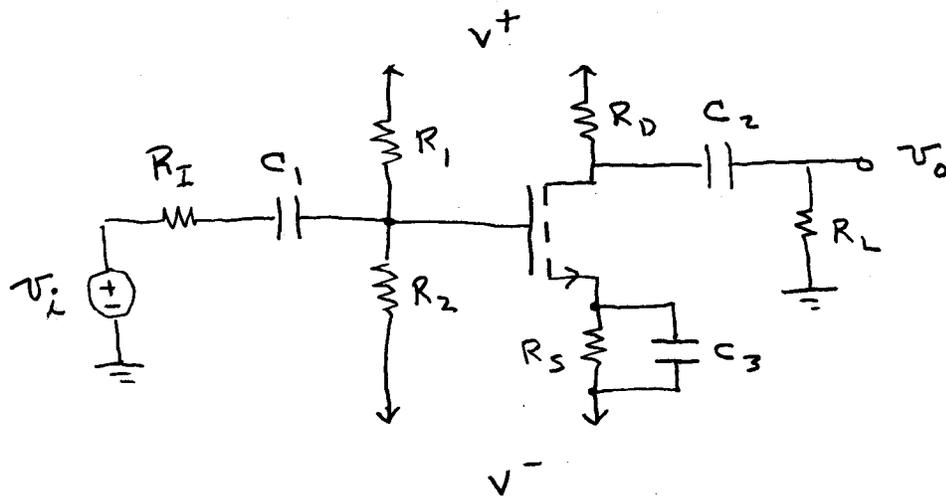

The Q point values are calculated with C_1 , C_2 , and C_3 open circuited. We assume this solution is known.

For a sinusoidal signal, the complex impedance of a capacitor is given by


$$Z_c = \frac{1}{j\omega C}$$

If ωC is sufficiently large, Z_c can be made small enough to be considered an ac short


6/14/4 (5)

circuit. We assume each C can be considered to be an ac short.

The ac equivalent circuit is as follows:

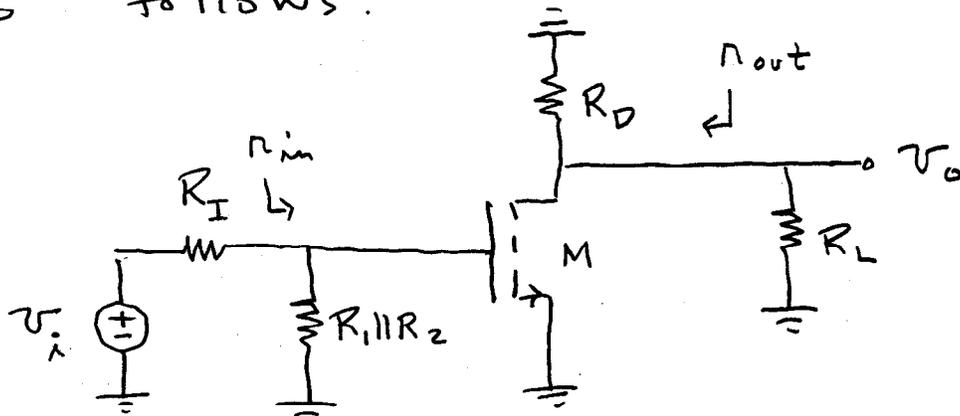

Replace M with its pi model

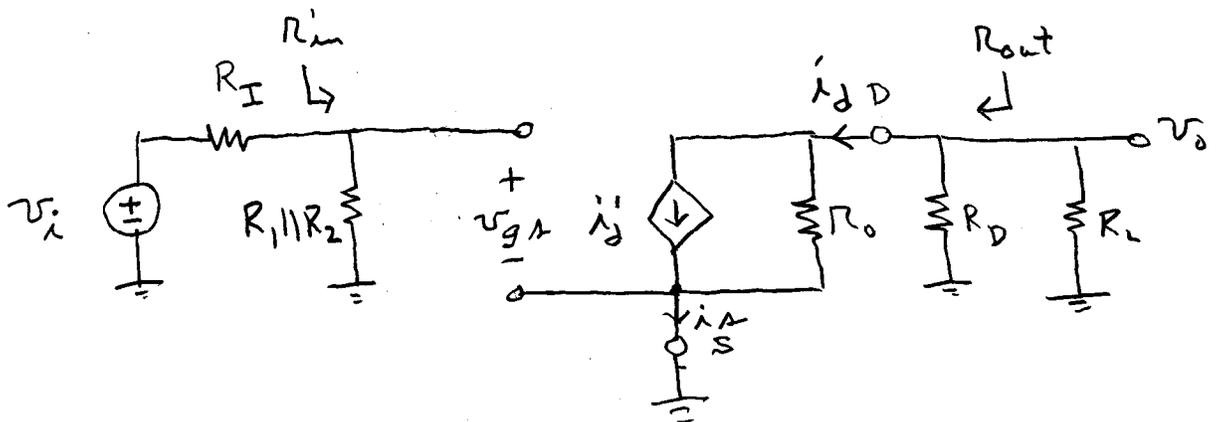

$$i'_d = g_m v_{gs} \quad g_m = 2\sqrt{K I_D}$$

$$R_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D}$$

6/14/4 (6)

We can write

$$v_{gs} = v_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2}$$

$$v_o = -\hat{i}_d' r_o \parallel R_D \parallel R_L$$

$$= -g_m v_{gs} r_o \parallel R_D \parallel R_L$$

$$= -g_m v_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} r_o \parallel R_D \parallel R_L$$

The voltage gain is given by

$$A_v = \frac{v_o}{v_i}$$

$$= \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} g_m (-r_o \parallel R_D \parallel R_L)$$

Note that this is of the form

$$A_v = \frac{v_{gs}}{v_i} \times \frac{\hat{i}_d'}{v_{gs}} \times \frac{v_o}{\hat{i}_d'}$$

6/14/4 (7)


The input and output resistances are given by

$$R_{in} = R_1 \parallel R_2$$

$$R_{out} = r_o \parallel R_D$$


Note that A_v is negative. This means that the output voltage is inverted when compared to the input voltage.

The Common Drain Amplifier

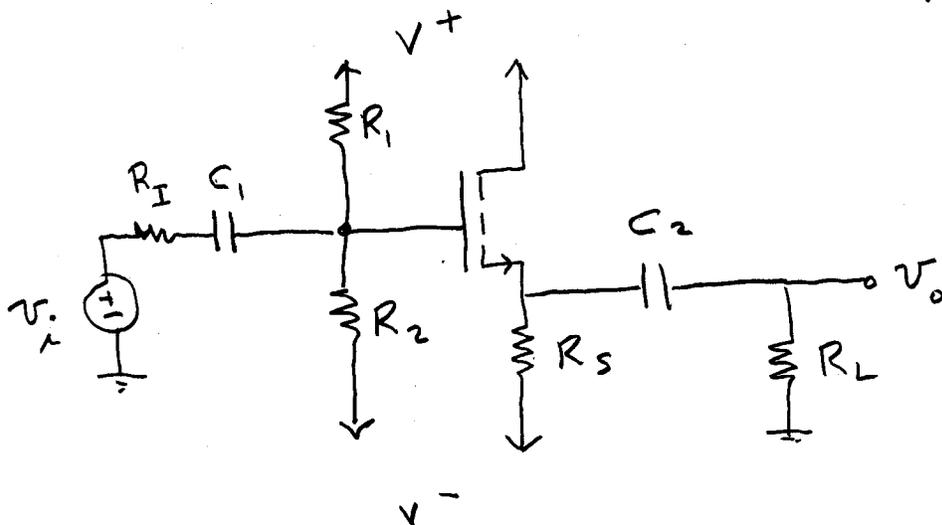


6/14/4 (8)

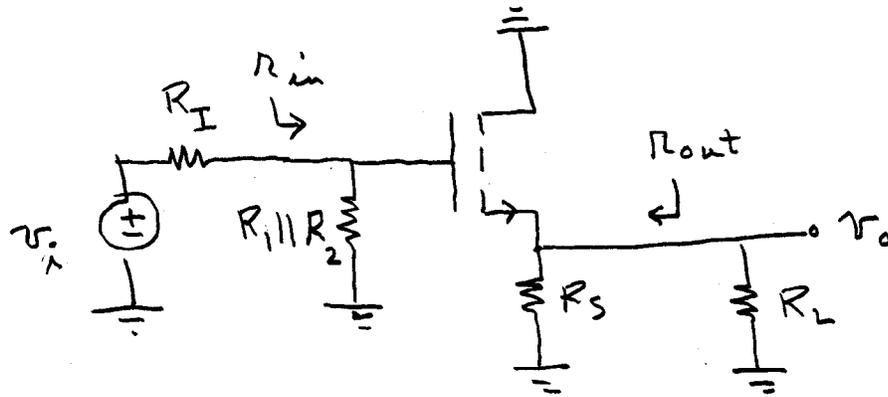We assume that we know the Q point solution, g_m , and R_o . Assume the capacitors are ac short circuits. The ac circuit is



Replace the MOSFET with its pi model

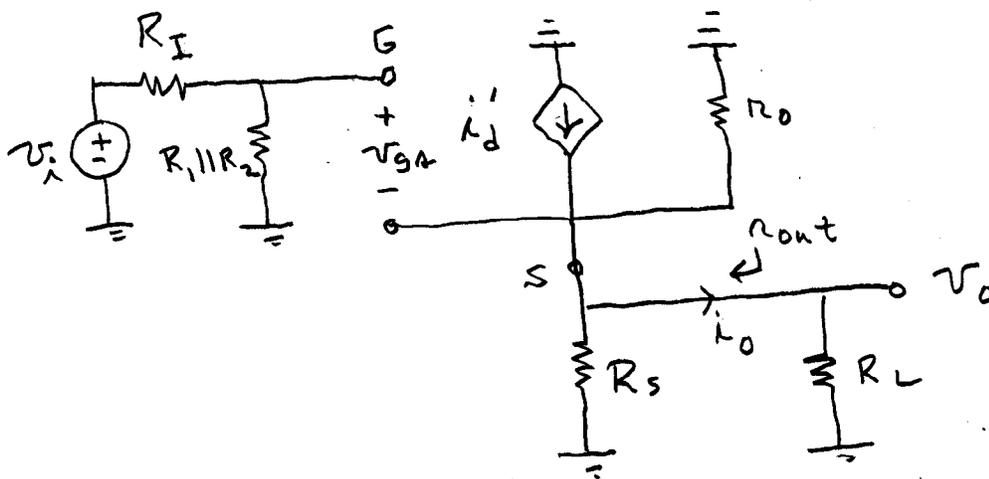

6/14/4 (9)

$$v_{gt} = v_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} - v_o$$

$$v_o = i_d' r_o \parallel R_S \parallel R_L$$

$$= g_m \left(v_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} - v_o \right) r_o \parallel R_S \parallel R_L$$

$$\Rightarrow v_o \left[1 + g_m (r_o \parallel R_S \parallel R_L) \right]$$

$$= g_m v_i \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} r_o \parallel R_S \parallel R_L$$

Thus the voltage gain is given by

$$A_v = \frac{v_o}{v_i}$$

$$= \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} \frac{g_m (r_o \parallel R_S \parallel R_L)}{1 + g_m (r_o \parallel R_S \parallel R_L)}$$


The gain is positive or non-inverting

6/15/4 ①

The input resistance is given by

$$R_{in} = R_1 \parallel R_2$$

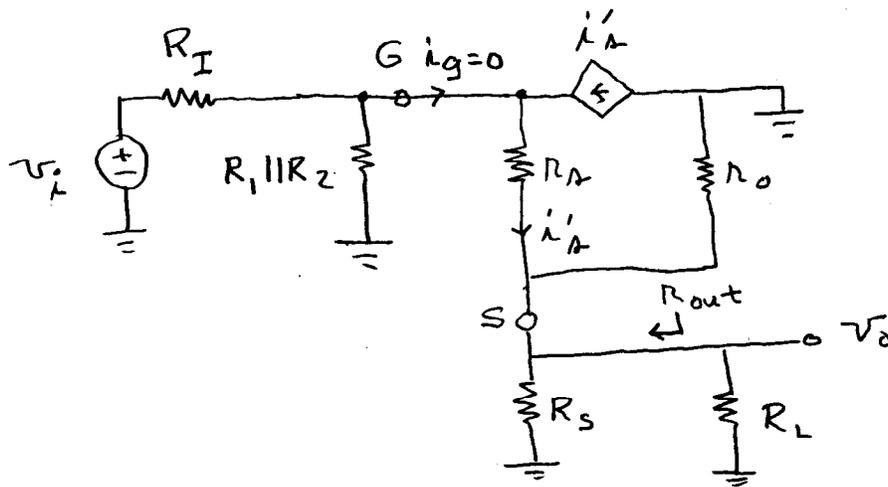To solve for the output resistance, it is much simpler to use the T model. The circuit is



Set $v_g = 0$ to solve for R_{out} .


Because $i_g = 0$, the voltage at the gate node is zero. Thus R_A connects from S to ground and we have

$$R_{out} = R_A \parallel R_O \parallel R_S$$

6/15/4 (2)

where $r_A = 1/g_m$

The Common Gate Amplifier

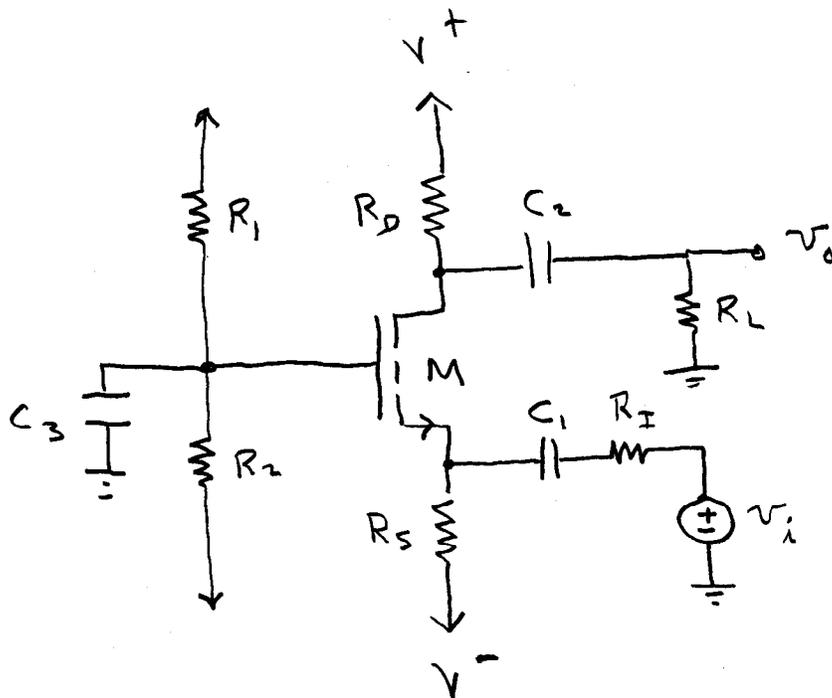

Assume we know the Q point solution from which we can calculate


$$g_m = 2\sqrt{K I_D}$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D}$$


The ac circuit is obtained by zeroing the dc supplies and

6/15/4 (3)

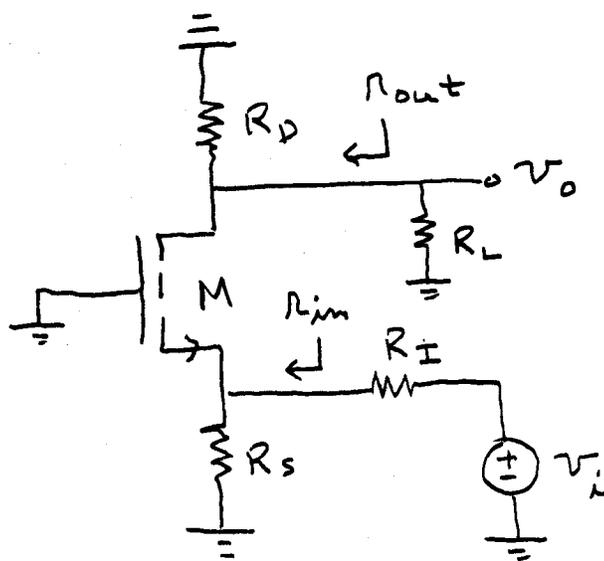replacing the capacitors with ac short circuits.



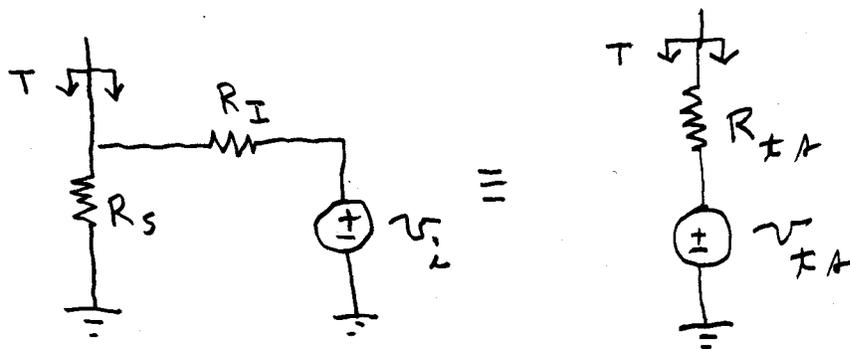
The solution for v_o and r_{out} is simplified by replacing the circuit looking out of the source by a Thévenin equivalent



6/15/4 (4)

$$V_{tA} = V_A \frac{R_s}{R_I + R_s} \quad R_{tA} = R_s \parallel R_I$$

Next we replace M with its pi model

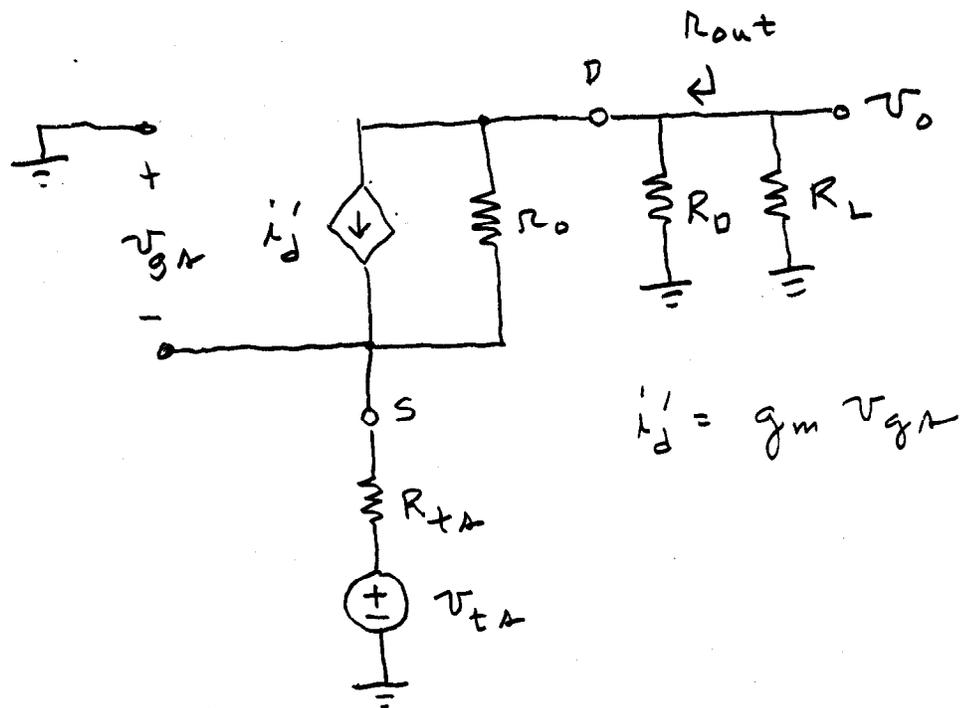


Note that neither end of R_o connects to ground. This greatly complicates the analysis. We will obtain an approximate solution by assuming the current through R_o can be neglected. That is, we let $R_o = \infty$.

6/15/4

5

The circuit becomes

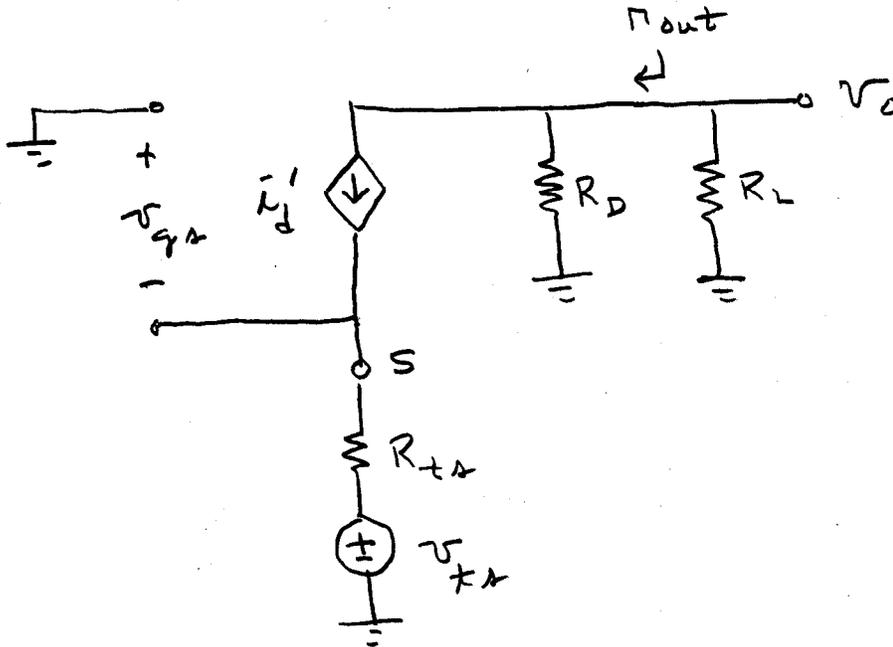

$$v_o = -i'_d R_D \parallel R_L$$

$$i'_d = g_m v_{gs}$$

$$v_{gs} = v_g - v_s$$

$$= 0 - (v_{tA} + i'_d R_{tA})$$

$$\Rightarrow i'_d = -g_m (v_{tA} + i'_d R_{tA})$$

$$\Rightarrow i'_d [1 + g_m R_{tA}] = -g_m v_{tA}$$

6/15/4

⑥

$$\Rightarrow \hat{v}_d = \frac{-g_m}{1 + g_m R_{tA}} v_{tA}$$

$$\Rightarrow v_o = \frac{+g_m R_D \parallel R_L}{1 + g_m R_{tA}} v_{tA}$$

$$= \frac{g_m R_D \parallel R_L}{1 + g_m R_S \parallel R_I} v_i \frac{R_S}{R_I + R_S}$$

$$\Rightarrow A_v = \frac{v_o}{v_i}$$


$$= \frac{R_S}{R_I + R_S} \frac{g_m R_D \parallel R_L}{1 + g_m R_S \parallel R_I}$$

Note that the gain is non-inverting. The output resistance is

$$R_{out} = R_D$$

To obtain the input resistance, we replace M with its T model.

6/15/4 (7)

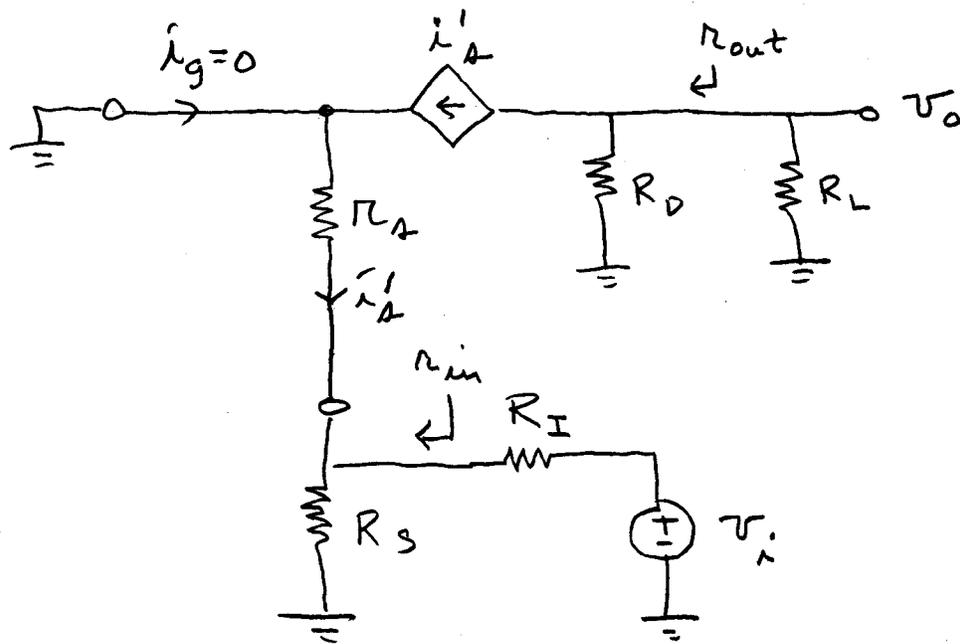

With $v_i = 0$, we have

$$R_{in} = R_A \parallel R_S$$


where $R_A = \frac{1}{g_m}$

Note that the common-gate analysis is approximate because we have omitted R_D . This is often done in hand calculations when one end of R_D does not connect to ac ground.


6/15/4 (8)

The Body Effect

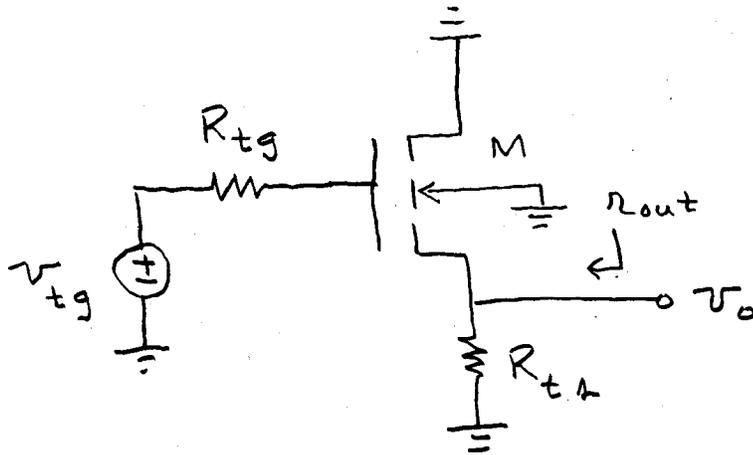So far we have neglected the body effect. To illustrate how it affects the solution, we will consider the common drain amplifier. Consider the ac circuit



Replace M with its pi model

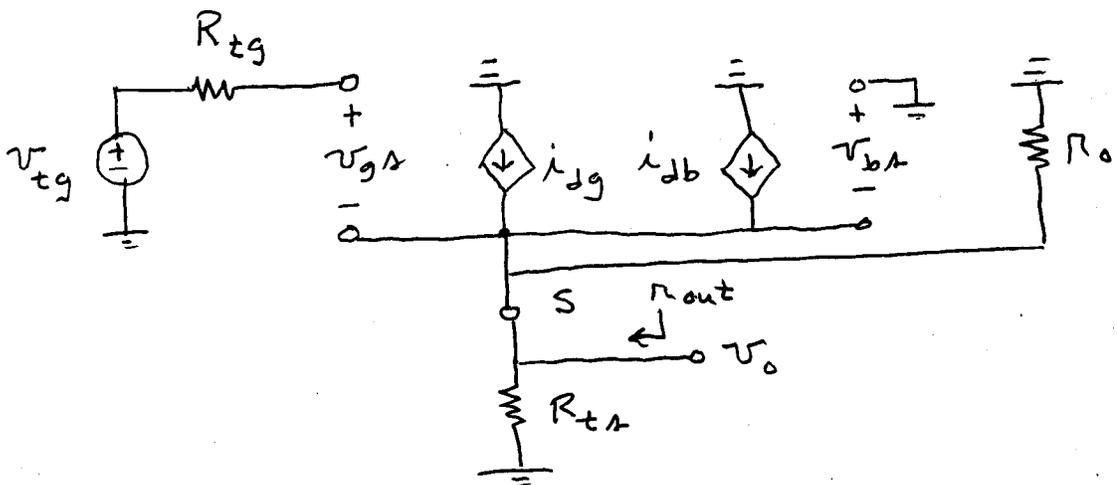

6/15/4 ⑨

$$v_o = (\hat{i}_{dq} + \hat{i}_{db}) (R_o \parallel R_{tA})$$

$$\hat{i}_{dq} = g_m v_{tq} = g_m (v_{tq} - v_o)$$

$$\hat{i}_{db} = g_{mb} v_{bA} = g_{mb} (0 - v_o)$$

$$\Rightarrow v_o = [g_m (v_{tq} - v_o) - g_{mb} v_o] R_o \parallel R_{tA}$$

$$\Rightarrow v_o [1 + (g_m + g_{mb}) R_o \parallel R_{tA}] = g_m (R_o \parallel R_{tA}) v_{tq}$$

$$\Rightarrow A_v = \frac{v_o}{v_{tq}}$$

$$= \frac{g_m (R_o \parallel R_{tA})}{1 + (g_m + g_{mb}) (R_o \parallel R_{tA})}$$

But $g_{mb} = \eta g_m$


$$\Rightarrow A_v = \frac{g_m (R_o \parallel R_{tA})}{1 + g_m (1 + \eta) (R_o \parallel R_{tA})}$$

Note that the body effect has reduced the voltage gain.

6/15/4

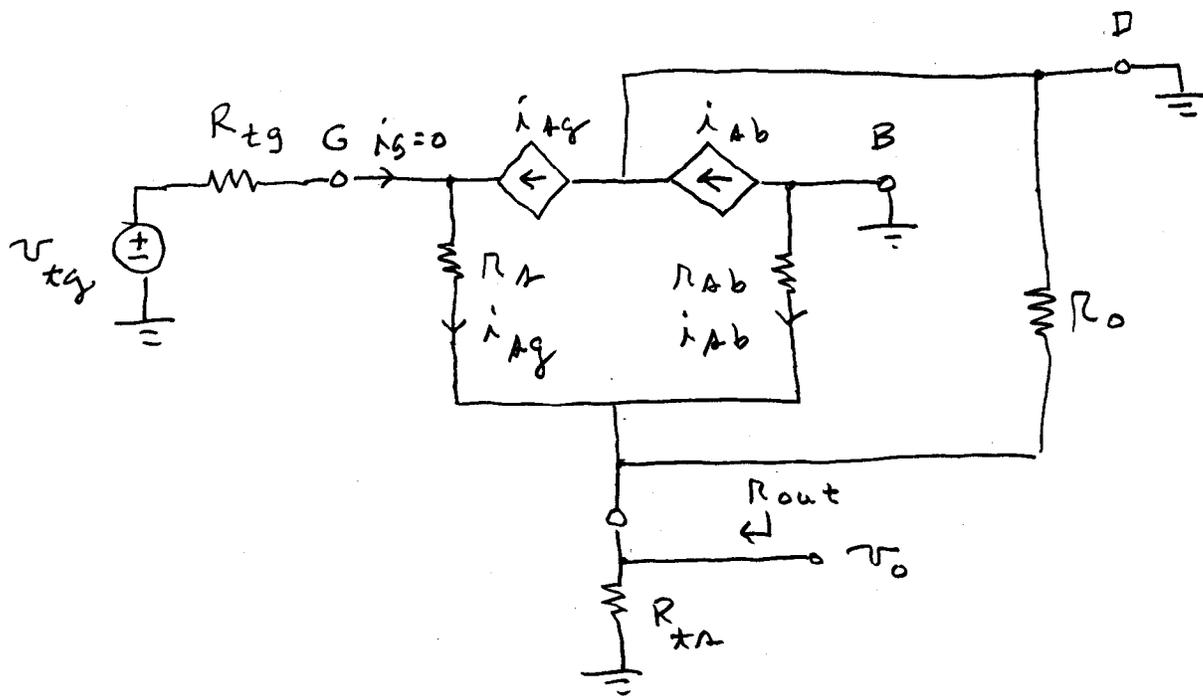(10)

To obtain the output resistance, we use the T model.



Set $v_{xg} = 0$ to solve for R_{out} .

Because $i_g = 0$, the top of R_A connects to ac ground.

$$\Rightarrow R_{out} = R_A \parallel R_{Ab} \parallel R_{xA}$$

where $R_A = \frac{1}{g_m}$

$$R_{Ab} = \frac{1}{g_{mb}} = \frac{1}{\eta g_m} = \frac{R_A}{\eta}$$

6/16/4 ①

Note that


$$R_A \parallel R_{Ab} = \frac{R_A \times \frac{R_A}{\eta}}{R_A + \frac{R_A}{\eta}} = \frac{\frac{R_A}{\eta}}{1 + \frac{1}{\eta}} = \frac{R_A}{1 + \eta}$$

Thus another expression for R_{out} is

$$R_{out} = \frac{R_A}{1 + \eta} \parallel R_{tA}$$

Numerical Example

Common Source Amplifier

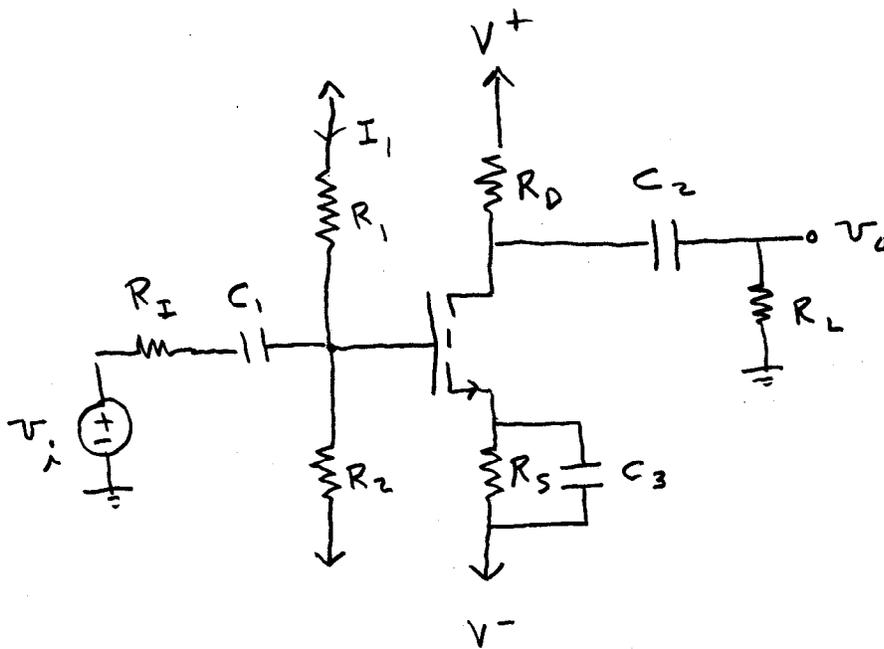

We are given $V^+ = +18V$, $V^- = -18V$,
 $K = 0.001 \text{ A/V}^2$, $V_{TH} = 1.5V$, $R_D = 50 \text{ k}\Omega$,
 $R_I = 1 \text{ k}\Omega$, $R_L = 1 \text{ k}\Omega$

6/16/4 (2)

We desire $I_D = 2 \text{ mA}$ and $V_{DS} = 10 \text{ V}$.

To calculate a value for R_D and R_S , we need V_D and V_S . Let

$$V_D = -4 \text{ V.}$$

$$\Rightarrow V_S = V_D - V_{DS} = -14 \text{ V.}$$

$$R_D = \frac{V^+ - V_D}{I_D} = 11 \text{ k}\Omega$$

$$R_S = \frac{V_S - V^-}{I_D} = 2 \text{ k}\Omega$$

To calculate R_1 and R_2 , we need V_G and I_1 .

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_{TH} = 2.914 \text{ V.}$$

$$V_G = V_{GS} + V_S = -11.086 \text{ V}$$

$$\text{Let } I_1 = 23.05 \mu\text{A}$$

$$\Rightarrow R_1 = \frac{V^+ - V_G}{I_1} = 1.262 \text{ M}\Omega$$

6/16/4 (3)

$$R_2 = \frac{V_G - V^-}{I_1} = 300 \text{ k}\Omega$$

$$g_m = 2\sqrt{kI_D} = \frac{1}{353.553}$$

The voltage gain is given by

$$A_v = \frac{v_o}{v_i}$$


$$= \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} g_m \left[-(r_o \parallel R_D \parallel R_L) \right]$$

$$= -2.536$$

This is a fairly low gain. Let us investigate the effect of adding a common drain stage between the amplifier and the load resistor R_L . The new circuit is

6/17/4

①

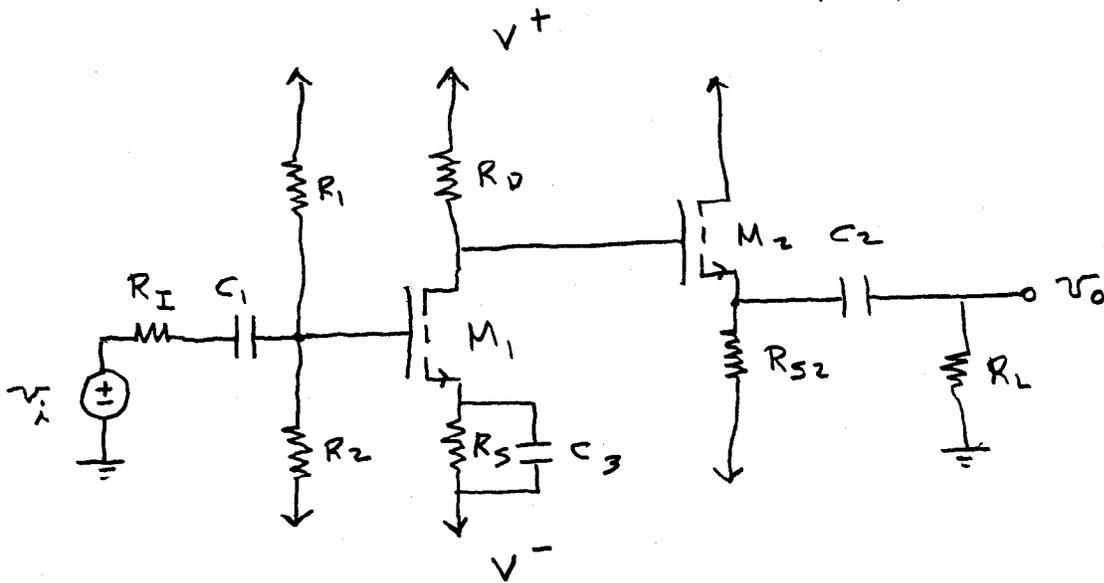

Let us choose R_{S2} to bias M_2
at $I_{D2} = I_{D1} = 2 \text{ mA}$

$$\Rightarrow V_{GS2} = V_{GS1} = 2.914 \text{ V.}$$

$$\begin{aligned} V_{S2} &= V_{G2} - V_{GS2} \\ &= (V^+ - I_{D1} R_{D1}) - V_{GS2} \\ &= -6.914 \text{ V.} \end{aligned}$$

$$R_2 = \frac{V_{S2} - V^-}{I_{D2}} = 5.543 \text{ k}\Omega$$

Because $I_{D2} = I_{D1}$, it follows that

$$g_{m2} = g_{m1} = \frac{1}{353.553}$$

6/17/4 (2)

We also assume that $R_{o2} = R_{o1} = 50 \text{ k}\Omega$

The new gain of the circuit is

$$A_v = \frac{R_1 \parallel R_2}{R_I + R_1 \parallel R_2} * g_{m1} * (-R_{o1} \parallel R_D) \\ * \frac{g_{m2} (R_{o2} \parallel R_{S2} \parallel R_L)}{1 + g_{m2} (R_{o2} \parallel R_{S2} \parallel R_L)} \\ = -17.83$$

The gain has increased by a factor

$$\frac{17.83}{2.536} = 7.032$$

In decibels, the change in gain is

$$20 \log(7.032) = 16.942 \text{ dB}$$

Thus the addition of a stage which has a gain less than

6/17/4 (3)

unity has increased the overall gain of the amplifier. In effect, M_2 has removed the load R_L from the drain output of M_1 . This causes the gain of M_1 to increase. Because M_2 has a low output resistance, it can drive R_L without its gain changing much. Thus an overall increase in gain is achieved.


M_2 is commonly called a buffer output stage. It isolates R_L from M_1 so that a higher gain can be obtained from M_1 .

6/17/4

④

Summary Results


CS Amplifier

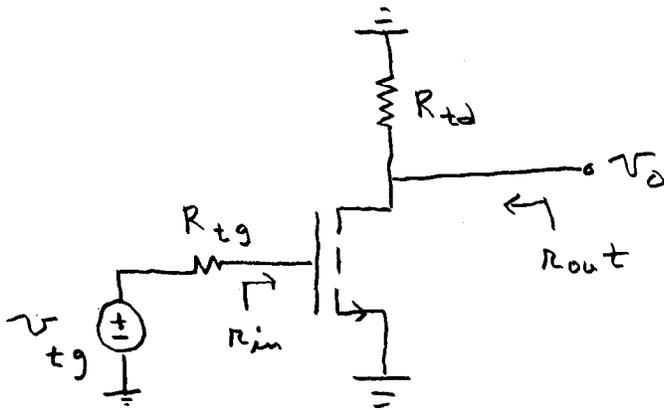

$$A_v = \frac{v_o}{v_{tg}} = -g_m (r_o \parallel R_{td})$$

$$R_{in}' = \infty \quad R_{out} = r_o \parallel R_{td}$$

CD Amplifier

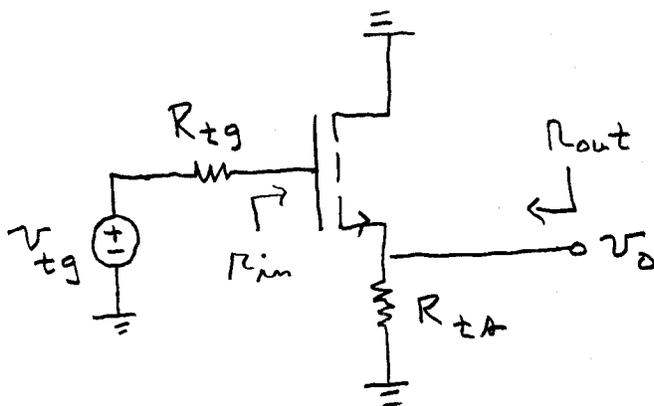

6/17/4 (5)

$$A_v = \frac{v_o}{v_{tq}} = \frac{g_m (r_o \parallel R_{tA})}{1 + g_m (r_o \parallel R_{tA})}$$

$$R_{in} = \infty \quad R_{out} = r_o \parallel R_{tA} \parallel R_{tA}$$

$$R_{tA} = 1/g_m$$


If the body lead connects to ac ground rather than to the source

$$A_v = \frac{v_o}{v_{tq}} = \frac{g_m (r_o \parallel R_{tA})}{1 + (1 + \eta) g_m (r_o \parallel R_{tA})}$$

$$R_{in} = \infty \quad R_{out} = \frac{r_o}{1 + \eta} \parallel R_{tA} \parallel R_{tA}$$

$$\eta = \frac{g_{mb}}{g_m} \quad R_{tA} = \frac{1}{g_m}$$

Common - Gate Amplifier

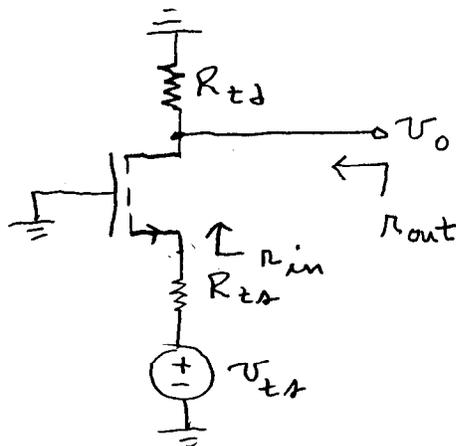

6/17/4 (6)

Because neither end of R_o connects to ac ground, we go with an approximate solution by assuming $R_o = \infty$.

$$A_v = \frac{v_o}{v_{in}} = \frac{g_m R_{td}}{1 + g_m R_{td}}$$

$$R_{in} = R_A = \frac{1}{g_m} \quad R_{out} = R_{td}$$

Let us compare the CS and CG gains. We assume $R_o = \infty$ for each.

$$\text{CS} - A_v = -g_m R_{td}$$

$$\text{CG} - A_v = \frac{+g_m R_{td}}{1 + g_m R_{td}}$$

Aside from the difference in signs, the CG amplifier gain is lower by a factor

$$\frac{1}{1 + g_m R_{td}}$$

6/17/4 (7)

If $R_{ts} = 0$, the gains are the same. As R_{ts} increases, the CG gain decreases. This if a high gain is desired, the CG stage should not be used with a source having a high R_{ts} .