

ECE 3040 Microelectronic Circuits Quiz 8


July 7, 2004

Professor Leach

Name _____

Instructions. Print your name in the space above. The quiz is closed-book and closed-notes. The quiz consists of one problem. **Honor Code Statement:** *I have neither given nor received help on this quiz.*
 Initials _____

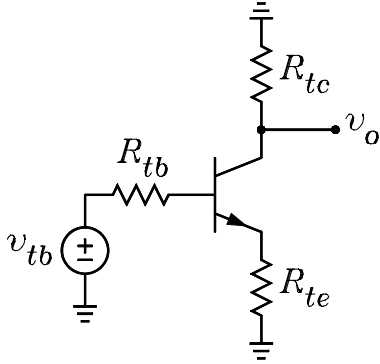1. The figure shows the ac signal circuit of a common-emitter amplifier. It is given that $I_E = 2\text{ mA}$, $\beta = 99$, $r_o = \infty$, and $V_T = 0.025\text{ V}$, $g_m = I_C/V_T$, $r_\pi = V_T/I_B$, $r_e = V_T/I_E$, and $r'_e = R_{tb}/(1 + \beta) + r_e$.
 - (a) Let $R_{te} = 0$ and $R_{tb} = 3.3\text{ k}\Omega$. Replace the transistor with the π model and use $i'_c = g_m v_{be}$. Write the appropriate equations and solve for the value of R_{tc} such that $v_o/v_{tb} = -200$.
 - (b) Let $R_{te} = 0$ and $R_{tc} = 3.3\text{ k}\Omega$. Replace the transistor with the T model and use $i'_e = \alpha i'_c$. Write the appropriate equations and solve for the value of R_{tb} such that $v_o/v_{tb} = -50$.
 - (c) Let $R_{tb} = 1\text{ k}\Omega$, $R_{te} = 50\ \Omega$, and $R_{tc} = 10\text{ k}\Omega$. Use the simplified T model to solve for v_o/v_{tb} .



Solutions: (see the class notes for the small-signal circuits) $g_m = I_C/V_T = \alpha I_E/V_T = 0.079\text{ S}$, $r_\pi = V_T/I_B = (1 + \beta) V_T/I_E = 1.25\text{ k}\Omega$, $\alpha = \beta/(1 + \beta) = 0.99$, $r_e = V_T/I_E = 12.5\ \Omega$, $r'_e = R_{tb}/(1 + \beta) + r_e = 22.5\ \Omega$

(a)

$$\begin{aligned} v_o &= -i'_c R_{tc} = -[g_m (v_{be})] R_{tc} = -\left[g_m \left(v_{tb} \frac{r_\pi}{R_{tb} + r_\pi} \right) \right] R_{tc} \\ \Rightarrow R_{tc} &= \frac{R_{tb} + r_\pi}{g_m r_\pi} \left(-\frac{v_o}{v_{tb}} \right) = \frac{3300 + 1250}{0.079 * 1250} (200) = 9.192\text{ k}\Omega \end{aligned}$$

(b)

$$\begin{aligned} v_o &= -i'_c R_{tc} = -[\alpha (i'_e)] R_{tc} \quad v_{tb} = i_b R_{tb} + i'_e r_e = \frac{i'_e}{1 + \beta} R_{tb} + i'_e r_e = i'_e \left(\frac{R_{tb}}{1 + \beta} + r_e \right) \\ \Rightarrow i'_e &= \frac{v_{tb}}{\frac{R_{tb}}{1 + \beta} + r_e} \Rightarrow v_o = -\left[\alpha \left(\frac{v_{tb}}{\frac{R_{tb}}{1 + \beta} + r_e} \right) \right] R_{tc} \\ \Rightarrow R_{tb} &= (1 + \beta) \left[\alpha R_{tc} \left(\frac{v_o}{v_{tb}} \right)^{-1} - r_e \right] = (1 + 99) \left[0.99 \times 3300 \left(\frac{1}{50} \right)^{-1} - 12.5 \right] = 5.284\text{ k}\Omega \end{aligned}$$

(c)

$$\begin{aligned} v_o &= -i'_c R_{tc} = -[\alpha (i'_e)] R_{tc} = -\left[\alpha \left(\frac{v_{tb}}{\frac{R_{tb}}{1 + \beta} + R_{te} + r_e} \right) \right] R_{tc} \\ \Rightarrow \frac{v_o}{v_{tb}} &= \frac{\alpha R_{tc}}{\frac{R_{tb}}{1 + \beta} + R_{te} + r_e} = \frac{0.99 \times 10000}{\frac{1000}{1 + 99} + 50 + 12.5} = -136.5 \end{aligned}$$