

ECE 3040 Quiz 9 – July 20, 2005


Professor Leach

Name _____

Instructions. Print your name in the space above. The quiz is closed-book and closed-notes. The quiz consists of two problems. Draw a box around all numerical answers. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials _____

Formula summary: $\alpha = \beta / (1 + \beta)$, $r_\pi = V_T / I_B$, $g_m = I_C / V_T$, $r_e = V_T / I_E$, $r'_e = (1 - \alpha) R_{tb} + r_e$, $r_o = (V_A + V_{CE}) / I_C$, $I_{C(npn)} = I_S \exp(V_{BE} / V_T)$, $I_{C(pnp)} = I_S \exp(V_{EB} / V_T)$, $I_C = \alpha I_E = \beta I_B$

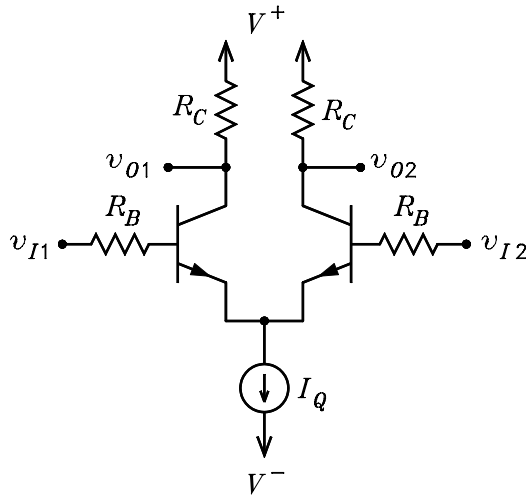1. The figure shows a differential amplifier. It is given that $R_B = 1 \text{ k}\Omega$, $R_C = 10 \text{ k}\Omega$, $I_Q = 1 \text{ mA}$, $V_{CE} = 10 \text{ V}$, $V_A = \infty$, $V_T = 25 \text{ mV}$, and $\beta = 99$.
 - (a) What are the numerical values of g_m , r_π , r_o , r_e , and r'_e ?
 - (b) Draw the simplified small-signal T model and use it to solve for the numerical values of i'_{e1} and i'_{e2} as functions of v_{i1} and v_{i2}
 - (c) Use the solution for i'_{e1} and i'_{e2} to solve for the numerical values of v_{o1} and v_{o2} as functions of v_{i1} and v_{i2} .



$$R_B := 1000 \quad R_C := 10000 \quad I_Q := 0.001 \quad V_{CE} := 10 \quad V_T := 0.025 \quad \beta := 99$$

$$\alpha := \frac{\beta}{1 + \beta} \quad \alpha = 0.99$$

$$g_m := \frac{\alpha \cdot I_Q}{2 \cdot V_T} \quad g_m^{-1} = 50.505 \quad r_e := \frac{2 \cdot V_T}{I_Q} \quad r_e = 50 \quad r'_e := \frac{R_B}{1 + \beta} + r_e \quad r'_e = 60$$

$$i'_{e1} = \frac{v_{i1} - v_{i2}}{2 \cdot r'_e} \quad i'_{e1} = \frac{v_{i1} - v_{i2}}{120} \quad i'_{e2} = -i'_{e1} \quad A_v := \frac{-\alpha \cdot R_C}{2 \cdot r'_e} \quad A_v = -82.5$$

$$v_{o1} = A_v \cdot (v_{i1} - v_{i2}) \quad v_{o1} = -82.5 \cdot (v_{i1} - v_{i2}) \quad v_{o2} = -v_{o1} \quad v_{o2} = 82.5 \cdot (v_{i1} - v_{i2})$$

2. The figure shows a complementary CC amplifier. Each BJT has the saturation current $I_S = 3 \times 10^{-14} \text{ A}$. Assume $V_T = 0.025 \text{ V}$.

(a) If cutin is defined as the base-emitter voltage at which the collector current is 0.2 mA , solve for the numerical value of the cutin voltage for the two transistors.

$$I_S := 3 \cdot 10^{-14} \quad V_T := 0.025 \quad I_C := 0.0002 \quad V_{BE1} := V_T \cdot \ln\left(\frac{I_C}{I_S}\right) \quad V_{BE1} = 0.7$$

$$V_{EB2} := V_{BE1}$$

- (b) Sketch and label the graph of v_O versus v_I . See the Class Notes.
(c) If v_I is a sine wave of amplitude $V_1 > V_\gamma$, sketch and label the waveform of v_O versus time. See the Class Notes.

