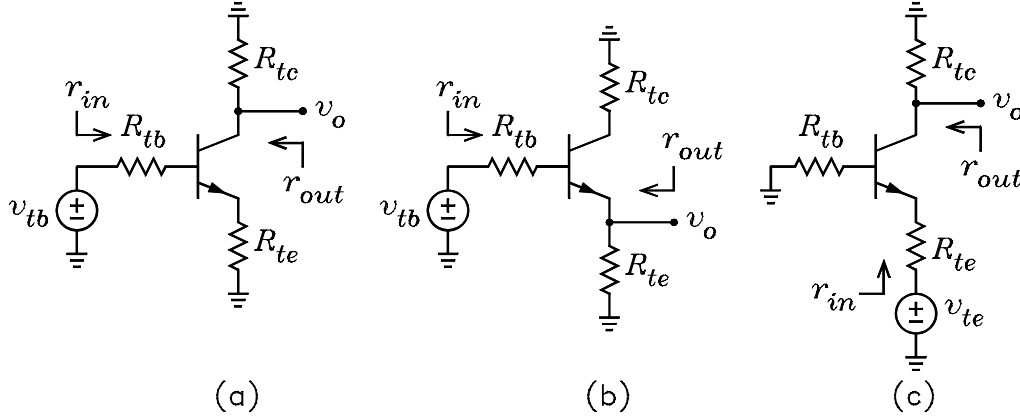


## ECE3050 Homework Set 6

The figures show a common-emitter amplifier, a common-collector amplifier, and a common-base amplifier. For each circuit, it is given that  $R_{tb} = 1\text{ k}\Omega$ ,  $R_{te} = 100\ \Omega$ , and  $R_{tc} = 10\text{ k}\Omega$ . The transistors have the values  $I_E = 1.5\text{ mA}$ ,  $V_T = 25\text{ mV}$ ,  $\beta = 99$ ,  $r_x = 50\ \Omega$ , and  $r_o = \infty$ .



1. For each transistor, show that  $g_m = 59.4\text{ mS}$ ,  $r_\pi = 1.667\text{ k}\Omega$ ,  $\alpha = 0.99$ , and  $r_e = 16.67\ \Omega$ .
2. For the common-emitter amplifier of Figure (a):

- (a) Replace the BJT with the  $\pi$  model. Label the controlled source in the collector  $i'_c$ , the base current  $i'_c/\beta$ , and the emitter current  $i'_c/\alpha$ . Let the voltage across  $r_\pi$  be written  $v_\pi = i'_c/g_m$ . Write a loop equation around the base-emitter loop and solve for  $i'_c$ . Use the circuit to show that

$$\frac{i'_c}{v_{tb}} = \frac{1}{\frac{R_{tb} + r_x}{\beta} + \frac{1}{g_m} + \frac{R_{te}}{\alpha}} = 7.785\text{ mS}$$

$$\frac{v_o}{v_{tb}} = \frac{-R_{tc}}{\frac{R_{tb} + r_x}{\beta} + \frac{1}{g_m} + \frac{R_{te}}{\alpha}} = -77.85$$

Label the base current  $i_b$  and the emitter current  $(1 + \beta)i_b$ . Write the loop equation and show that

$$r_{in} = \frac{v_{tb}}{i_b} = R_{tb} + r_x + r_\pi + (1 + \beta)R_{te} = 12.72\text{ k}\Omega$$

Show that

$$r_{out} = R_{tc} = 10\text{ k}\Omega$$

- (b) Replace the BJT with the T model. Label the controlled source in the collector  $i'_c$ , the base current  $i'_c/\beta$ , and the emitter current  $i'_c/\alpha$ . Write a loop equation around the base-emitter loop and solve for  $i'_c$ . Use the circuit to show that

$$\frac{i'_c}{v_{tb}} = \frac{1}{\frac{R_{tb} + r_x}{\beta} + \frac{r_e + R_{te}}{\alpha}} = 7.785\text{ mS}$$

$$\frac{v_o}{v_{tb}} = \frac{-R_{tc}}{\frac{R_{tb} + r_x}{\beta} + \frac{r_e + R_{te}}{\alpha}} = -77.85$$

Label the base current  $i_b$  and the emitter current  $(1 + \beta) i_b$ . Write the loop equation and show that

$$r_{in} = \frac{v_{tb}}{i_b} = R_{tb} + r_x + (1 + \beta)(r_e + R_{te}) = 12.72 \text{ k}\Omega$$

Show that

$$r_{out} = R_{tc} = 10 \text{ k}\Omega$$

- (c) Show that the simplified T model and simplified  $\pi$  model give the same answers for  $v_o/v_{tb}$  and  $r_{out}$ .

3. For the common-collector amplifier of Figure (b):

- (a) Replace the BJT with the  $\pi$  model. Label the controlled source in the collector  $i'_c$ , the base current  $i'_e/(1 + \beta)$ , and the emitter current  $i'_e$ . Write a loop equation around the base-emitter loop and solve for  $i'_e$ . Use the circuit to show that

$$\frac{i'_e}{v_{tb}} = \frac{1}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + R_{te}} = 7.864 \text{ mS}$$

$$\frac{v_o}{v_{tb}} = \frac{R_{te}}{\frac{R_{tb} + r_x + r_\pi}{1 + \beta} + R_{te}} = 0.786$$

Label the base current  $i_b$  and the emitter current  $(1 + \beta) i_b$ . Write the loop equation and show that

$$r_{in} = \frac{v_{tb}}{i_b} = R_{tb} + r_x + r_\pi + (1 + \beta) R_{te} = 12.72 \text{ k}\Omega$$

The output resistance can be written  $r_{out} = R_{te} \parallel r_{ie}$ , where  $r_{ie}$  is the resistance seen looking up into the emitter. This can be solved for as the ratio of the open-circuit output voltage with  $R_{te} = \infty$  to the short-circuit output current with  $R_{te} = 0$ . Show that  $r_{ie}$  is given by

$$r_{ie} = \frac{v_{o(oc)}}{i_{o(sc)}} = \frac{v_o|_{R_{te}=\infty}}{\left. \frac{v_o}{R_{te}} \right|_{R_{te}=0}} = \frac{R_{tb} + r_x + r_\pi}{1 + \beta} = 27.17 \Omega$$

and that  $r_{out}$  is

$$r_{out} = R_{te} \parallel r_{ie} = 21.36 \Omega$$

- (b) Replace the BJT with the T model. Label the controlled source in the collector  $i'_c$ , the base current  $i'_e/(1 + \beta)$ , and the emitter current  $i'_e$ . Write a loop equation around the base-emitter loop and solve for  $i'_e$ . Use the circuit to show that

$$\frac{i'_e}{v_{tb}} = \frac{1}{\frac{R_{tb} + r_x}{1 + \beta} + r_e + R_{te}} = 7.864 \text{ mS}$$

$$\frac{v_o}{v_{tb}} = \frac{R_{te}}{\frac{R_{tb} + r_x}{1 + \beta} + r_e + R_{te}} = 0.786$$

Label the base current  $i_b$  and the emitter current  $(1 + \beta) i_b$ . Write the loop equation and show that

$$r_{in} = \frac{v_{tb}}{i_b} = R_{te} + r_x + (1 + \beta)(r_e + R_{te}) = 12.72 \text{ k}\Omega$$

The output resistance can be written  $r_{out} = R_{te} \parallel r_{ie}$ , where  $r_{ie}$  is the resistance seen looking up into the emitter. This can be solved for as the ratio of the open-circuit voltage with  $R_{te} = \infty$  to the short-circuit current with  $R_{te} = 0$ . Show that  $r_{ie}$  is given by

$$r_{ie} = \frac{v_{o(oc)}}{i_{o(sc)}} = \frac{v_o|_{R_{te}=\infty}}{\frac{v_o}{R_{te}}|_{R_{te}=0}} = \frac{R_{tb} + r_x}{1 + \beta} + r_e = 27.17 \Omega$$

and that  $r_{out}$  is

$$r_{out} = R_{te} \parallel r_{ie} = 21.36 \Omega$$

- (c) Show that the simplified T model gives the same answers for  $v_o/v_{tb}$  and  $r_{out}$ . Note that the simplified  $\pi$  model is not convenient because the  $v_o$  node does not appear in the circuit.

4. For the common-base amplifier of Figure (c):

- (a) Replace the BJT with the  $\pi$  model. Label the controlled source in the collector  $i'_c$ , the base current  $i'_b$ , and the emitter current  $i'_e = i'_c/\alpha$ . Let the voltage across  $r_\pi$  be written  $v_\pi = i'_c/g_m$ . Write a loop equation around the base-emitter loop and solve for  $i'_c$  to show that

$$\frac{i'_c}{v_{tb}} = \frac{-1}{\frac{R_{tb} + r_x + r_\pi}{\beta} + \frac{R_{te}}{\alpha}} = 7.785 \text{ mS}$$

$$\frac{v_o}{v_{te}} = \frac{R_{tc}}{\frac{R_{tb} + r_x + r_\pi}{\beta} + \frac{R_{te}}{\alpha}} = 77.85$$

Label the base current  $i'_e/(1 + \beta)$  and the emitter current  $i'_e$ . Write the loop equation and show that

$$r_{in} = \frac{v_{te}}{-i'_e} = \frac{R_{te} + r_x + r_\pi}{1 + \beta} + R_{te} = 127.2 \Omega$$

Show that

$$r_{out} = R_{tc} = 10 \text{ k}\Omega$$

- (b) Replace the BJT with the T model. Label the controlled source in the collector  $i'_c$ , the base current  $i'_c/\beta$ , and the emitter current  $i'_c/\alpha$ . Write a loop equation around the base-emitter loop and solve for  $i'_e$ . Use the circuit to show that

$$\frac{i'_c}{v_{te}} = \frac{-1}{\frac{R_{tb} + r_x}{\beta} + \frac{r_e + R_{te}}{\alpha}} = 7.785 \text{ mS}$$

$$\frac{v_o}{v_{te}} = \frac{R_{tc}}{\frac{R_{tb} + r_x}{\beta} + \frac{r_e + R_{te}}{\alpha}} = 77.85$$

Label the base current  $i'_e/(1 + \beta)$  and the emitter current  $i'_e$ . Write the loop equation and show that

$$r_{in} = \frac{v_{te}}{-i'_e} = \frac{R_{te} + r_x}{1 + \beta} + r_e + R_{te} = 127.2 \Omega$$

Show that

$$r_{out} = R_{tc} = 10 \text{ k}\Omega$$

(c) Show that the simplified T model and the simplified  $\pi$  model give the same answers.