

Common-Emitter Amplifier Frequency Response Example

$$R_P(x,y) := \frac{x \cdot y}{x + y} \quad \text{Function for calculating parallel resistors.}$$


$$R_1 := 100000 \quad R_2 := 120000 \quad R_C := 4300 \quad R_E := 5600 \quad R_S := 5000 \quad R_L := 10000$$

$$V_p := 15 \quad V_m := -15 \quad V_{BE} := 0.65 \quad V_T := 0.025 \quad \beta := 99 \quad \alpha := 0.99$$


$$r_x := 20 \quad r_0 := 50000 \quad R_3 := 100$$

$v_s := 1$ With $v_s = 1$, the voltage gain is equal to v_o .
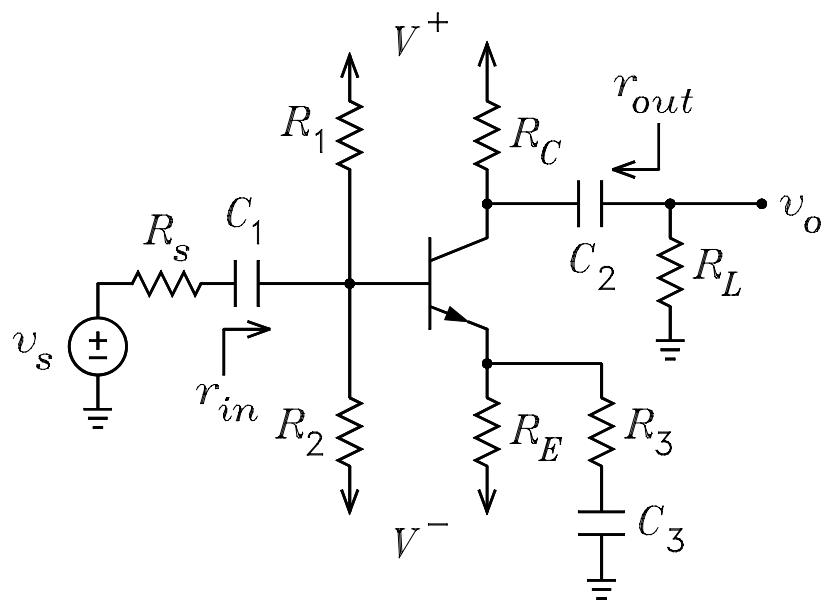
$$c_\mu := 15 \cdot 10^{-12} \quad c_\pi := 75 \cdot 10^{-12} \quad C_1 := 0.2 \cdot 10^{-6} \quad C_2 := 5 \cdot 10^{-6} \quad C_3 := 100 \cdot 10^{-6}$$



DC Bias Solution

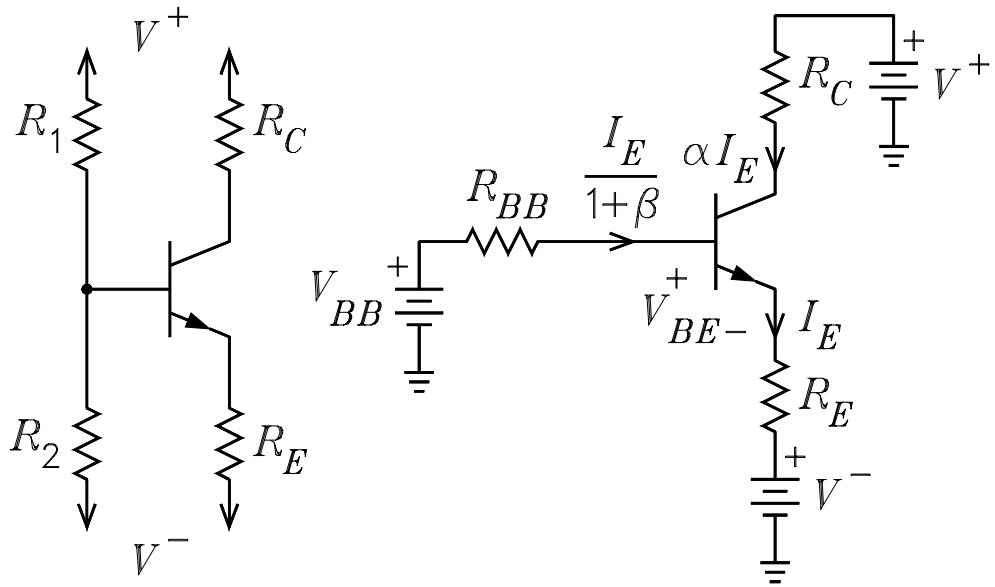



$$V_{BB} := \frac{V_p \cdot R_2 + V_m \cdot R_1}{R_1 + R_2} \quad V_{BB} = 1.3636 \quad R_{BB} := R_p(R_1, R_2) \quad R_{BB} = 5.4545 \cdot 10^4$$

$$I_E := \frac{V_{BB} - V_{BE} - V_m}{\frac{R_{BB}}{1+\beta} + R_E} \quad I_E = 2.557 \cdot 10^{-3} \quad V_C := V_p - \alpha \cdot I_E \cdot R_C \quad V_C = 4.1151$$

$$V_B := V_{BE} + I_E \cdot R_E + V_m \quad V_B = -0.0311 \quad V_C - V_B = 4.1461 \quad \text{Thus active mode.}$$

AC Solution

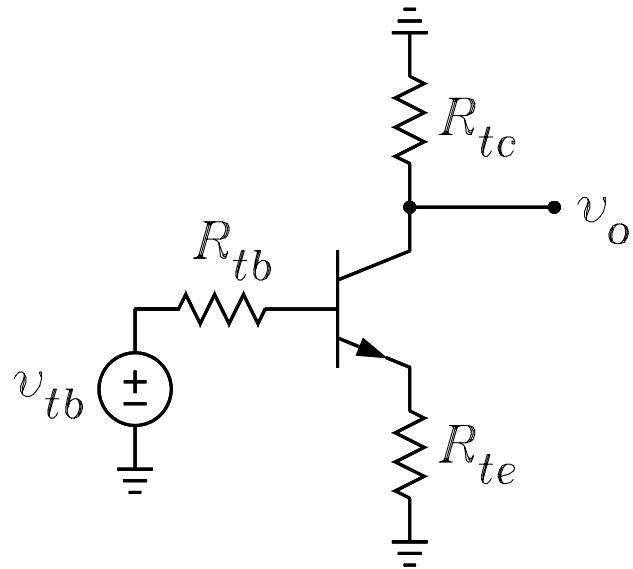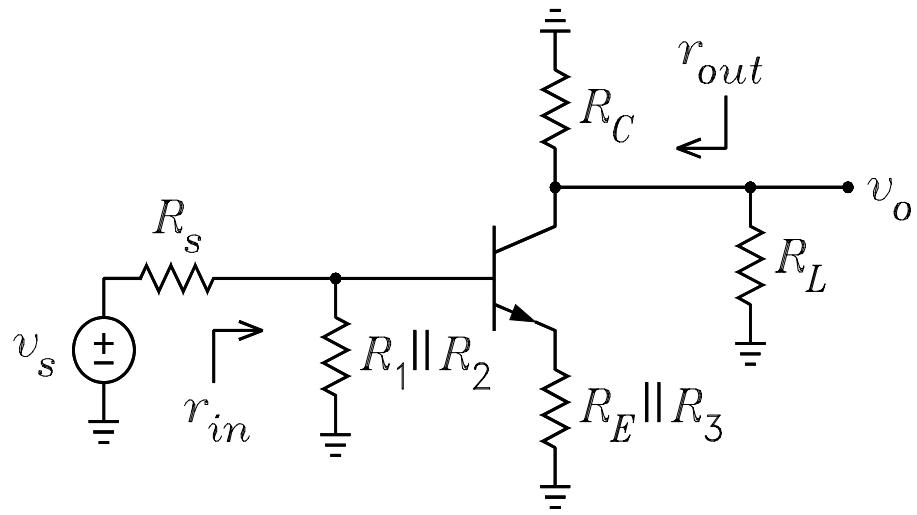
$$r_e := \frac{V_T}{I_E} \quad r_e = 9.7773 \quad g_m := \frac{\alpha \cdot I_E}{V_T} \quad g_m = 0.1013 \quad r_\pi := \frac{\beta \cdot V_T}{\alpha \cdot I_E} \quad r_\pi = 977.7264$$



$$v_{tb} := v_s \cdot \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \quad v_{tb} = 0.916 \quad R_{tb} := R_P(R_S, R_P(R_1, R_2)) \quad R_{tb} = 4.5802 \cdot 10^3$$

$$R_{te} := R_P(R_E, R_3) \quad R_{te} = 98.2456 \quad r'_e := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r'_e = 55.7788$$
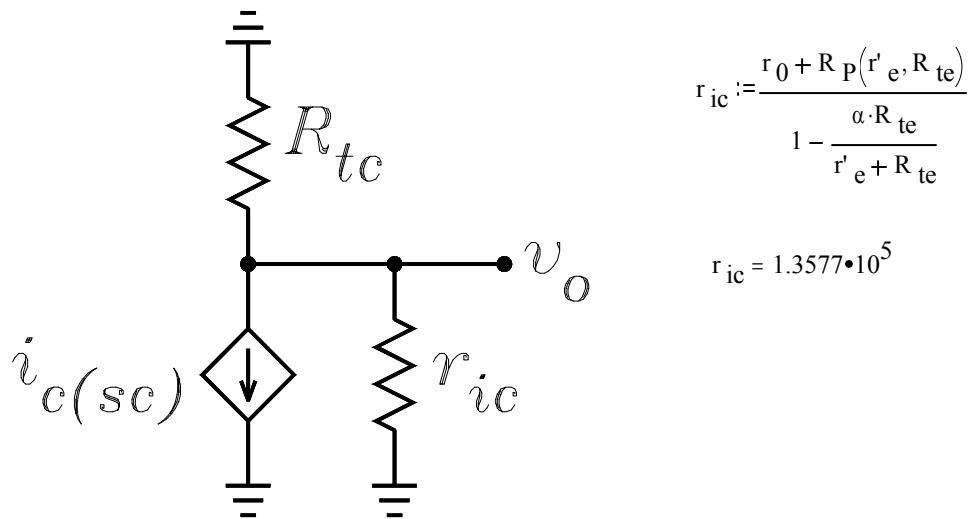
$$R_{tc} := R_P(R_C, R_L) \quad R_{tc} = 3.007 \cdot 10^3$$




$$r_{ic} := \frac{r_0 + R_p(r'_e, R_{te})}{1 - \frac{\alpha \cdot R_{te}}{r'_e + R_{te}}}$$

$$r_{ic} = 1.3577 \cdot 10^5$$

$$v_o := v_s \cdot \frac{\alpha}{\frac{R_{tb} + r_x}{1 + \beta} + r_e + R_{te}} \cdot R_p(R_C, R_p(r_{ic}, R_L)) \quad v_o = -18.9088$$

$$A_v := v_o \quad A_v = -18.9088 \quad \text{This is the midband voltage gain.}$$


Circuit for r_{out} :

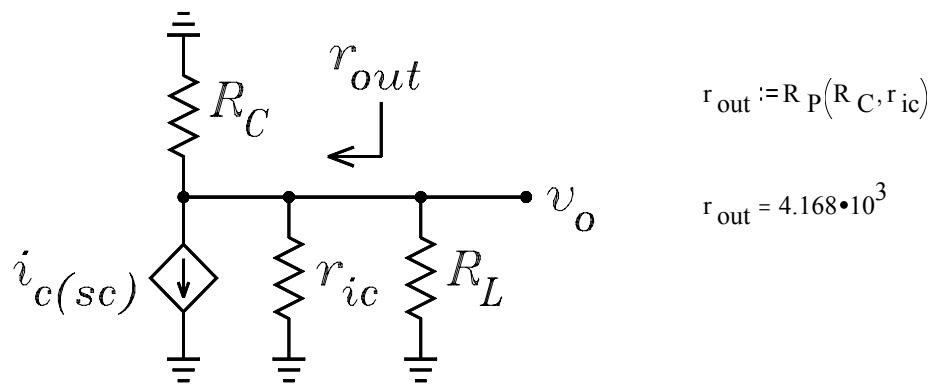

$$r_{out} := R_p(R_C, r_{ic})$$

$$r_{out} = 4.168 \cdot 10^3$$

Circuit for r_{in} .

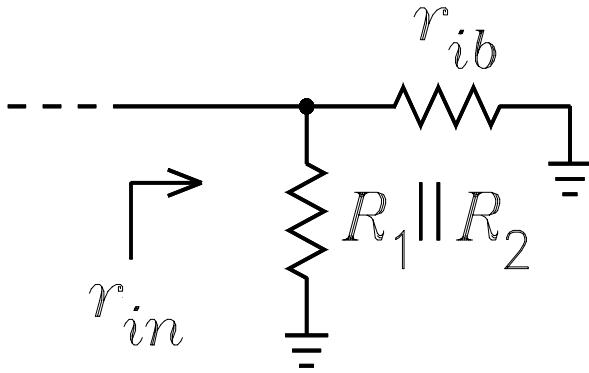

$$r_{ib} := r_x + r_\pi + (1 + \beta) \cdot R_{te}$$

$$r_{ib} = 1.0822 \cdot 10^4$$

$$r_{in} := R_P(r_{ib}, R_P(R_1, R_2))$$

$$r_{in} = 9.0305 \cdot 10^3$$

Time constant for C_1

$$\tau_1 := (R_S + r_{in}) \cdot C_1 \quad \tau_1 = 2.8061 \cdot 10^{-3} \quad f_1 := \frac{1}{2 \cdot \pi \cdot \tau_1} \quad f_1 = 56.7173$$

Time constant for C_2

$$\tau_2 := (r_{out} + R_L) \cdot C_2 \quad \tau_2 = 0.0708 \quad f_2 := \frac{1}{2 \cdot \pi \cdot \tau_2} \quad f_2 = 2.2467$$

Time constants for C_3 (To simplify the calculation, neglect the effect of r_0).

$$\tau_{3p} := (R_P(R_E, r'_e) + R_3) \cdot C_3 \quad \tau_{3p} = 0.0155 \quad f_{3p} := \frac{1}{2 \cdot \pi \cdot \tau_{3p}} \quad f_{3p} = 10.2529$$

$$\tau_{3Z} := (R_E + R_3) \cdot C_3 \quad \tau_{3Z} = 0.57 \quad f_{3Z} := \frac{1}{2 \cdot \pi \cdot \tau_{3Z}} \quad f_{3Z} = 0.2792$$

Approximate lower cutoff frequency

$$f_L := \sqrt{f_1^2 + f_2^2 + f_{3p}^2 - 2 \cdot f_{3Z}^2} \quad f_L = 57.679$$

Calculation of $K = v_o/v_b$ for the Miller Theorem.

$$v_b := 1 \quad \text{Thus } K = v_o$$

$$K := -\frac{\alpha}{r_e + R_{te}} \cdot R_P(R_C, R_P(r_{ic}, R_L)) \quad K = -26.9612$$

Time constants for c_μ

$$c_{\mu b} := (1 - K) \cdot c_\mu \quad c_{\mu b} = 4.1942 \cdot 10^{-10}$$

$$\tau_{\mu b} := R_P(R_{tb} + r_x, r_{ib} - r_x) \cdot c_{\mu b} \quad \tau_{\mu b} = 1.3531 \cdot 10^{-6}$$

$$c_{\mu c} := c_\mu \quad c_{\mu c} = 1.5 \cdot 10^{-11} \quad \tau_{\mu c} := (R_P(r_{out}, R_L)) \cdot c_{\mu c} \quad \tau_{\mu c} = 4.4128 \cdot 10^{-8}$$

$$\tau_\mu := \tau_{\mu b} + \tau_{\mu c} \quad \tau_\mu = 1.3973 \cdot 10^{-6} \quad f_\mu := \frac{1}{2 \cdot \pi \cdot \tau_\mu} \quad f_\mu = 1.139 \cdot 10^5$$

Time constants for c_π . (To simplify the calculation, neglect the effect of r_0).

$$\tau_\pi := \frac{R_{tb} + r_x + R_{te}}{R_{tb} + r_x + r_\pi + (1 + \beta) \cdot R_{te}} \cdot r_\pi \cdot c_\pi \quad \tau_\pi = 2.2369 \cdot 10^{-8}$$

$$f_\pi := \frac{1}{2 \cdot \pi \cdot \tau_\pi} \quad f_\pi = 7.1151 \cdot 10^6$$

Approximate upper cutoff frequency

$$f_H := \sqrt{\left(\frac{1}{f_\mu^2} + \frac{1}{f_\pi^2} \right)^{-1}} \quad f_H = 1.1389 \cdot 10^5$$