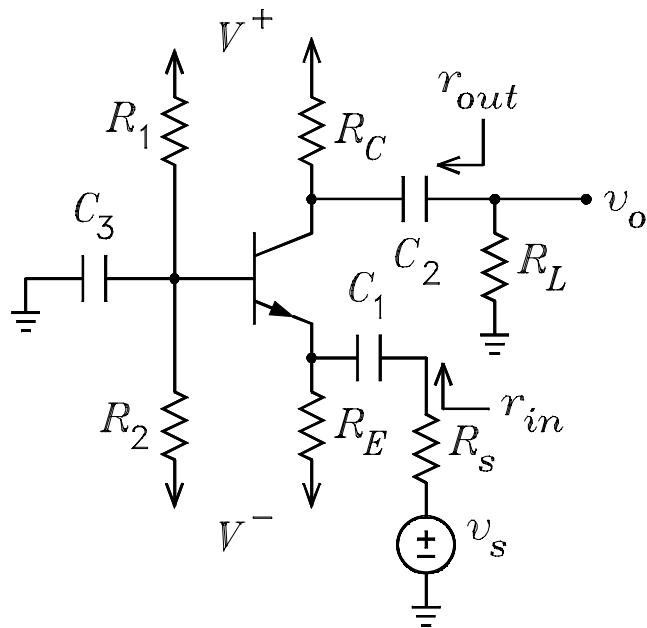


## Common-Base Amplifier Example - Summer 2000

$$R_P(x,y) := \frac{x \cdot y}{x + y} \quad \text{Function for calculating parallel resistors.}$$

$$\begin{aligned} R_1 &:= 100000 & R_2 &:= 120000 & R_C &:= 4300 & R_E &:= 5600 & R_S &:= 100 & R_L &:= 10000 \\ V_p &:= 15 & V_m &:= -15 & V_{BE} &:= 0.65 & V_T &:= 0.025 & \beta &:= 99 & \alpha &:= 0.99 \\ r_x &:= 20 & r_0 &:= 50000 \end{aligned}$$

$v_s := 1$       With  $v_s = 0$ , the voltage gain is equal to  $v_o$ .



### DC Bias Solution

$$V_{BB} := \frac{V_p \cdot R_2 + V_m \cdot R_1}{R_1 + R_2} \quad V_{BB} = 1.364$$

$$R_{BB} := R_P(R_1, R_2) \quad R_{BB} = 5.455 \cdot 10^4$$

$$I_E := \frac{V_{BB} - V_{BE} - V_m}{\frac{R_{BB}}{1 + \beta} + R_E} \quad I_E = 2.557 \cdot 10^{-3}$$

$$V_C := V_p - \alpha \cdot I_E \cdot R_C \quad V_C = 4.115$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 9.777$$

AC Solution

$$v_{te} := v_s \cdot \frac{R_E}{R_S + R_E} \quad v_{te} = 0.982$$

$$R_{te} := R_P(R_E, R_S) \quad R_{te} = 98.246$$

$$R_{tb} := 0 \quad R_{tb} = 0$$

$$r_{ie} := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r_{ie} = 9.977$$

$$R_{tc} := R_P(R_C, R_L) \quad R_{tc} = 3.007 \cdot 10^3$$

$$r_{ic} := \frac{r_0 + R_P(r_{ie}, R_{te})}{1 - \frac{\alpha \cdot R_{te}}{r_{ie} + R_{te}}} \quad r_{ic} = 4.938 \cdot 10^5$$

$$i_{csc} := \frac{-v_{te}}{R_{te} + R_P(r_{ie}, r_0)} \cdot \frac{\alpha \cdot r_0 + r_{ie}}{r_0 + r_{ie}} \quad i_{csc} = -8.987 \cdot 10^{-3}$$

$$v_o := -i_{csc} \cdot R_P(R_C, R_P(r_{ic}, R_L)) \quad v_o = 26.862 \quad \text{This is the voltage gain.}$$

$$r_{out} := R_P(R_C, r_{ic}) \quad r_{out} = 4.263 \cdot 10^3$$

$$r_{ieo} := r_{ie} \cdot \frac{r_0 + R_{tc}}{\frac{R_{tc}}{1 + \beta} + r_0 + r_{ie}} \quad r_{ieo} = 10.569$$

$$r_{in} := R_P(r_{ieo}, R_E) \quad r_{in} = 10.549$$

The following solution is based on the  $r_{ic}$  approximations.

$$i_{csc} := -v_{te} \cdot \frac{\alpha}{r_{ie} + R_{te}} \quad i_{csc} = -8.987 \cdot 10^{-3}$$

$$v_c := -i_{csc} \cdot R_P(R_C, R_P(r_{ic}, R_L)) \quad v_c = 26.861 \quad \text{This is the voltage gain. It is 0.004% lower than the exact solution.}$$

$$r_{out} := R_P(r_{ic}, R_C) \quad r_{out} = 4.263 \cdot 10^3$$

$$r_{in} := R_P(r_{ie}, R_E) \quad r_{in} = 9.96$$