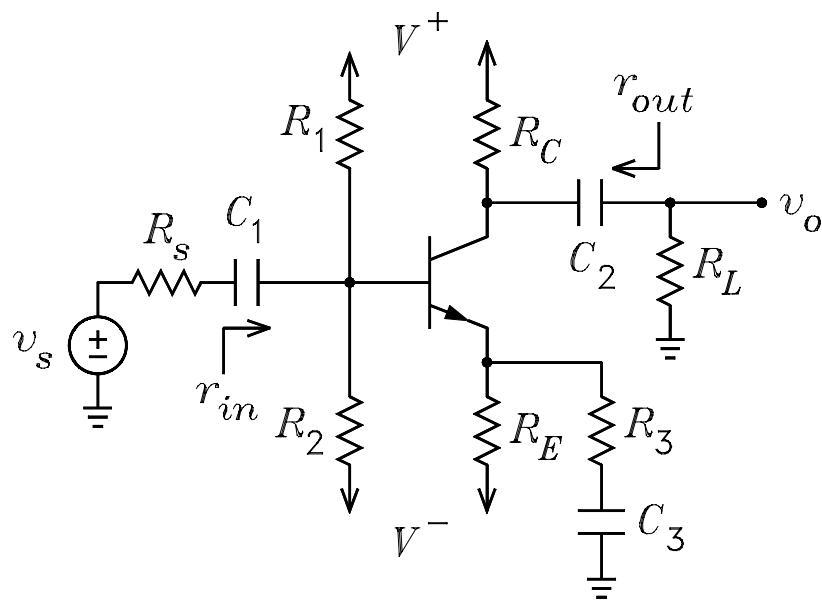


Common-Emitter Amplifier Example - Summer 2000

$$R_P(x,y) := \frac{x \cdot y}{x + y} \quad \text{Function for calculating parallel resistors.}$$

$$\begin{aligned} R_1 &:= 100000 & R_2 &:= 120000 & R_C &:= 4300 & R_E &:= 5600 & R_S &:= 5000 & R_L &:= 10000 \\ V_p &:= 15 & V_m &:= -15 & V_{BE} &:= 0.65 & V_T &:= 0.025 & \beta &:= 99 & \alpha &:= 0.99 \\ r_x &:= 20 & r_0 &:= 50000 & R_3 &:= 100 \end{aligned}$$

$v_s := 1$ With $v_s = 0$, the voltage gain is equal to v_o .



DC Bias Solution

$$V_{BB} := \frac{V_p \cdot R_2 + V_m \cdot R_1}{R_1 + R_2} \quad V_{BB} = 1.3636$$

$$R_{BB} := R_P(R_1, R_2) \quad R_{BB} = 5.4545 \cdot 10^4$$

$$I_E := \frac{V_{BB} - V_{BE} - V_m}{\frac{R_{BB}}{1 + \beta} + R_E} \quad I_E = 2.557 \cdot 10^{-3}$$

$$V_C := V_p - \alpha \cdot I_E \cdot R_C \quad V_C = 4.1151$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 9.7773$$

AC Solution

$$v_{tb} := v_s \cdot \frac{R_P(R_1, R_2)}{R_S + R_P(R_1, R_2)} \quad v_{tb} = 0.916$$

$$R_{tb} := R_P(R_S, R_P(R_1, R_2)) \quad R_{tb} = 4.5802 \cdot 10^3$$

$$R_{te} := R_P(R_E, R_3) \quad R_{te} = 98.2456$$

$$r_{ie} := \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad r_{ie} = 55.7788$$

$$R_{tc} := R_P(R_C, R_L) \quad R_{tc} = 3.007 \cdot 10^3$$

$$r_{ic} := \frac{r_0 + R_P(r_{ie}, R_{te})}{1 - \frac{\alpha \cdot R_{te}}{r_{ie} + R_{te}}} \quad r_{ic} = 1.3577 \cdot 10^5$$

$$i_{csc} := \frac{v_{tb}}{r_{ie} + R_P(R_{te}, r_0)} \cdot \left(\alpha - \frac{R_{te}}{R_{te} + r_0} \right) \quad i_{csc} = 5.8835 \cdot 10^{-3}$$

$$v_o := -i_{csc} \cdot R_P(R_C, R_P(r_{ic}, R_L)) \quad v_o = -17.3084 \quad \text{This is the voltage gain.}$$

$$r_{out} := R_P(R_C, r_{ic}) \quad r_{out} = 4.168 \cdot 10^3$$

$$r_{ib} := r_x + (1 + \beta) \cdot (r_e + R_p(R_{te}, r_0 + R_{tc})) - \frac{\beta \cdot R_{te} \cdot R_{tc}}{R_{tc} + r_0 + R_{te}}$$

$$r_{ib} = 1.0253 \cdot 10^4$$

$$r_{in} := R_p(r_{ib}, R_p(R_1, R_2)) \quad r_{in} = 8.6309 \cdot 10^3$$

The following solution is based on the r_0 approximations.

$$i_{csc} := v_{tb} \cdot \frac{\alpha}{r_{ie} + R_{te}} \quad i_{csc} = 5.8878 \cdot 10^{-3}$$

$$v_c := -i_{csc} \cdot R_p(R_C, R_p(r_{ic}, R_L)) \quad v_c = -17.3211 \quad \text{This is the voltage gain. It is 0.075% lower than the exact solution.}$$

$$r_{out} := R_p(r_{ic}, R_C) \quad r_{out} = 4.168 \cdot 10^3$$

$$r_{ib} := r_x + (1 + \beta) \cdot (r_e + R_{te}) \quad r_{ib} = 1.0822 \cdot 10^4$$

$$r_{in} := R_p(r_{ib}, R_p(R_1, R_2)) \quad r_{in} = 9.0305 \cdot 10^3$$