

Simplified T Model

Figure 1 shows the T model with a Thévenin source in series with the base. We wish to solve for an equivalent circuit in which the source i'_c connects from the collector node to ground rather than from the collector node to the B' node. The first step is to replace the source i'_c with two identical series sources with the common node grounded. The circuit is shown in Fig. 2(a).

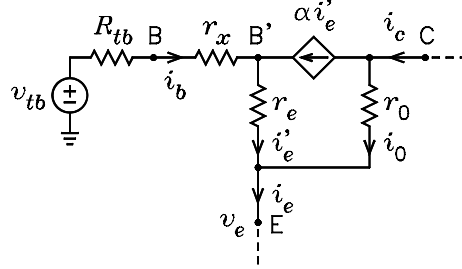


Figure 1: T model with Thévenin source connected to the base.

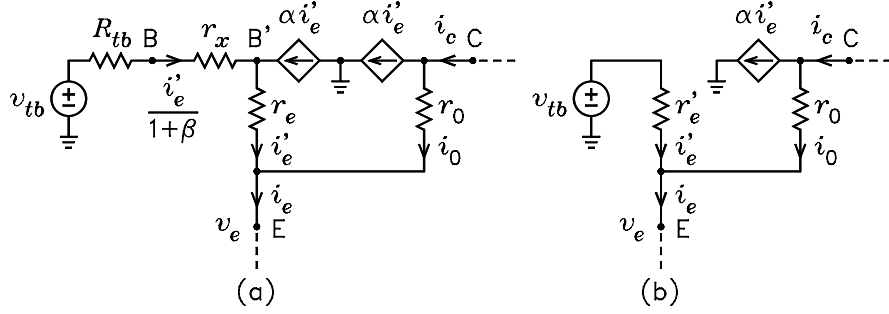


Figure 2: (a) Circuit with the i'_c source replaced by identical series sources. (b) Simplified T model.

For the circuit in Fig. 2(a), we can write

$$v_e = v_{tb} - \frac{i'_e}{1 + \beta} (R_{tb} + r_x) - i'_e r_e = v_{tb} - i'_e \left(\frac{R_{tb} + r_x}{1 + \beta} + r_e \right) \quad (1)$$

Let us define the resistance r'_e by

$$r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e = \frac{R_{tb} + r_x + r_e}{1 + \beta} \quad (2)$$

With this definition, v_e is given by

$$v_e = v_{tb} - i'_e r'_e \quad (3)$$

The circuit which models this equation is shown in Fig. 2(b). This will be called the simplified T model. It predicts the same emitter and collector currents as the circuit in Fig. 1. Note that the resistors R_{tb} and r_x do not appear in this circuit. They are part of the resistor r'_e .