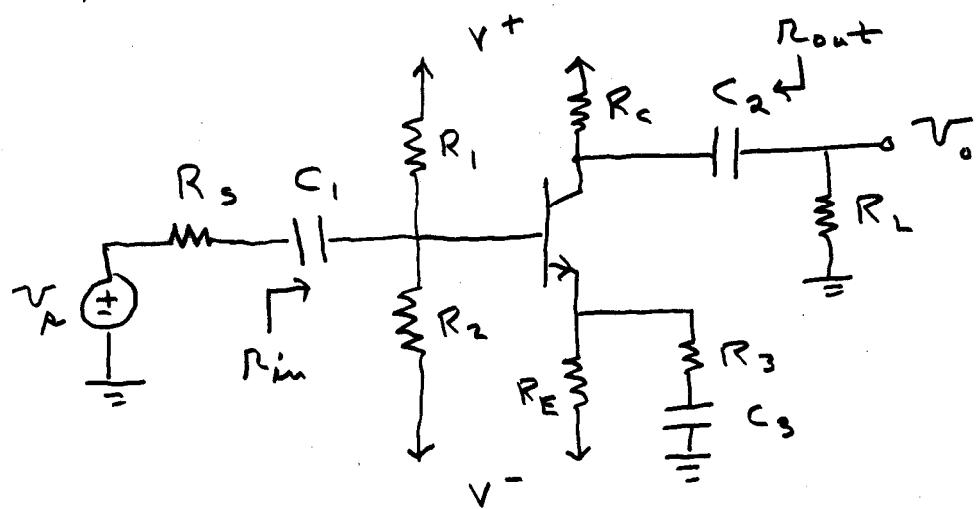


1-05/29/03


The Common Emitter (CE) Amplifier

For the CE amplifier, the signal is applied to the base and the output is taken from the collector. A typical capacitively coupled CE amplifier is shown.



The dc bias currents and voltages are solved for assuming the capacitors are open circuits. For the ac small-signal solution, set $v^+ = v^- = 0$ and assume the capacitors are ac short circuits. The circuit reduces to

2-05/29/03

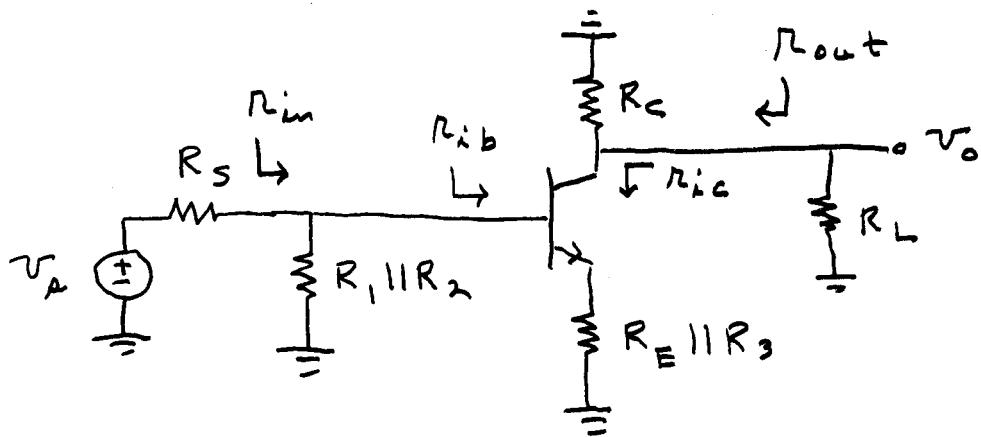

The input and output resistances are given by

$$R_{in} = R_1 \parallel R_2 \parallel R_{ib}$$

$$R_{out} = R_C \parallel R_{ic}$$

where

$$R_{ib}' = R_x + R_\pi + R_{te} \frac{(1+\beta)R_o + R_{tc}}{R_o + R_{te} + R_{tc}}$$

$$R_{te} = R_E \parallel R_3 \quad R_{tc} = R_C \parallel R_L$$

$$R_{ic}' = \frac{R_o + R_e' \parallel R_{te}}{1 - \frac{\alpha R_{te}}{R_e' + R_{te}}}$$


$$R_e' = \frac{R_{tb} + R_x}{1 + \beta} + R_e \quad R_{tb} = R_s \parallel R_1 \parallel R_2$$

3-05/29/03

Looking out of the base, the Thévenin equivalent circuit has the values

$$v_{tb} = v_A \frac{R_1 || R_2}{R_s + R_1 || R_2} \quad R_{tb} = R_s || R_1 || R_2$$

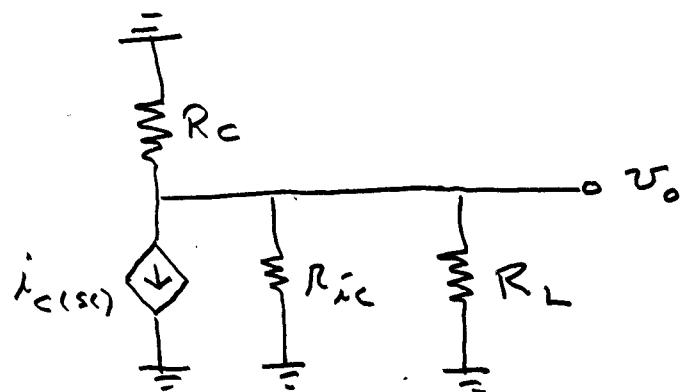To solve for v_o , we replace the BJT with the Norton collector circuit.



$i_{c(s)}$ is given by

$$i_{c(s)} = G_{mb} v_{tb}$$

where

$$G_{mb} = \frac{\alpha}{r'_e + R_{te} || R_o} \frac{R_o - R_{te}/\beta}{R_o + R_{te}}$$

4 - 05 | 29 / 03

The output voltage is given by

$$V_o = -i_{c(s)} R_{ic} \parallel R_c \parallel R_L$$

$$= -G_m b V_{tb} R_{ic} \parallel R_c \parallel R_L$$

$$= -G_m b V_A \frac{R_i \parallel R_2}{R_s + R_i \parallel R_2} R_{ic} \parallel R_c \parallel R_L$$

Thus the voltage gain is given by

$$A_v = \frac{V_o}{V_A}$$

$$= -\frac{R_i \parallel R_2}{R_s + R_i \parallel R_2} G_m b R_{ic} \parallel R_c \parallel R_L$$

The above solution is exact. Often, an approximate solution is made for rough calculations. Assume that $R_x = 0$ and $R_o = \infty$ for the approximations. In this case


$$R_{ib} = (1+\beta)(R_e + R_{te})$$

$$= R_\pi + (1+\beta) R_{te}$$

$$i_c = \alpha i_e = g_m V_{be} = g_m (V_b - V_e)$$

5 - 05/29/03

The signal equivalent circuit is

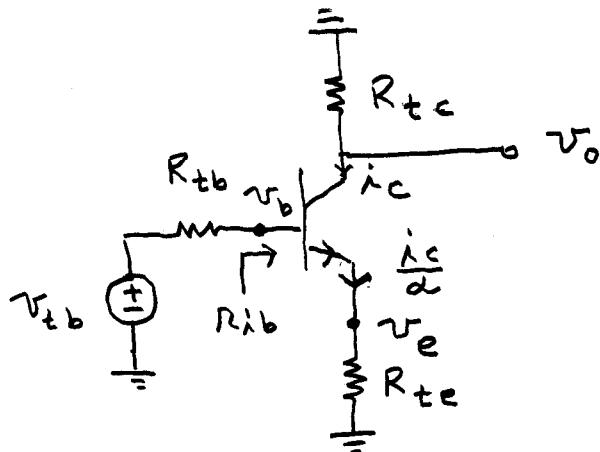

$$v_b = v_{tb} \frac{R_{ib}}{R_{tb} + R_{ib}} \quad v_e = \frac{i_c}{\alpha} R_{te}$$

$$i_c = g_m (v_b - v_e) = g_m \left(v_b - \frac{i_c}{\alpha} R_{te} \right)$$


$$\Rightarrow i_c = \frac{g_m v_b}{1 + \frac{g_m R_{te}}{\alpha}}$$

$$\begin{aligned} v_o &= -i_c R_{tc} = - \frac{g_m v_b}{1 + \frac{g_m R_{te}}{\alpha}} R_{tc} \\ &= -v_{tb} \frac{R_{ib}}{R_{tb} + R_{ib}} \frac{g_m R_{tc}}{1 + \frac{g_m R_{te}}{\alpha}} \\ &= -v_A \frac{R_1 || R_2}{R_s + R_1 || R_2} \frac{R_{ib}}{R_{tb} + R_{ib}} \frac{g_m R_{tc}}{1 + \frac{g_m R_{tc}}{\alpha}} \end{aligned}$$

$$\begin{aligned} \Rightarrow A_v &= \frac{v_o}{v_A} \\ &= - \frac{R_1 || R_2}{R_s + R_1 || R_2} \frac{R_{ib}}{R_{tb} + R_{ib}} \frac{g_m R_{tc}}{1 + \frac{g_m R_{tc}}{\alpha}} \end{aligned}$$

6 - 05 / 29 / 03

An Alternate Approximate Solution

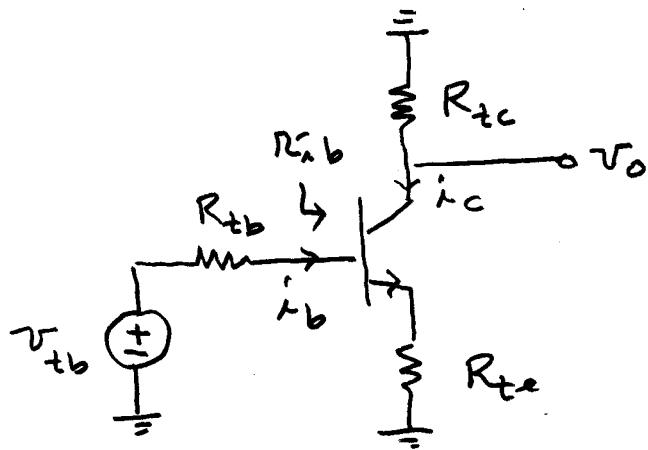

If $r_x = 0$ and $R_o = \infty$, R_{ib} is given by

$$R_{ib} = (1 + \beta) (r_e + R_{te}) = r_\pi + (1 + \beta) R_{te}$$

$$i_b = \frac{V_{tb}}{R_{tb} + R_{ib}}$$

$$i_c = \beta i_b$$

$$V_o = -i_c R_{tc} = -V_{tb} \frac{\beta R_{tc}}{R_{tb} + R_{ib}}$$

$$= -V_A \frac{R_1 || R_2}{R_s + R_1 || R_2} \frac{\beta R_{tc}}{R_{tb} + R_{ib}}$$

$$\Rightarrow A_v = \frac{V_o}{V_A} = - \frac{R_1 || R_2}{R_s + R_1 || R_2} \frac{\beta R_{tc}}{R_{tb} + R_{ib}}$$