
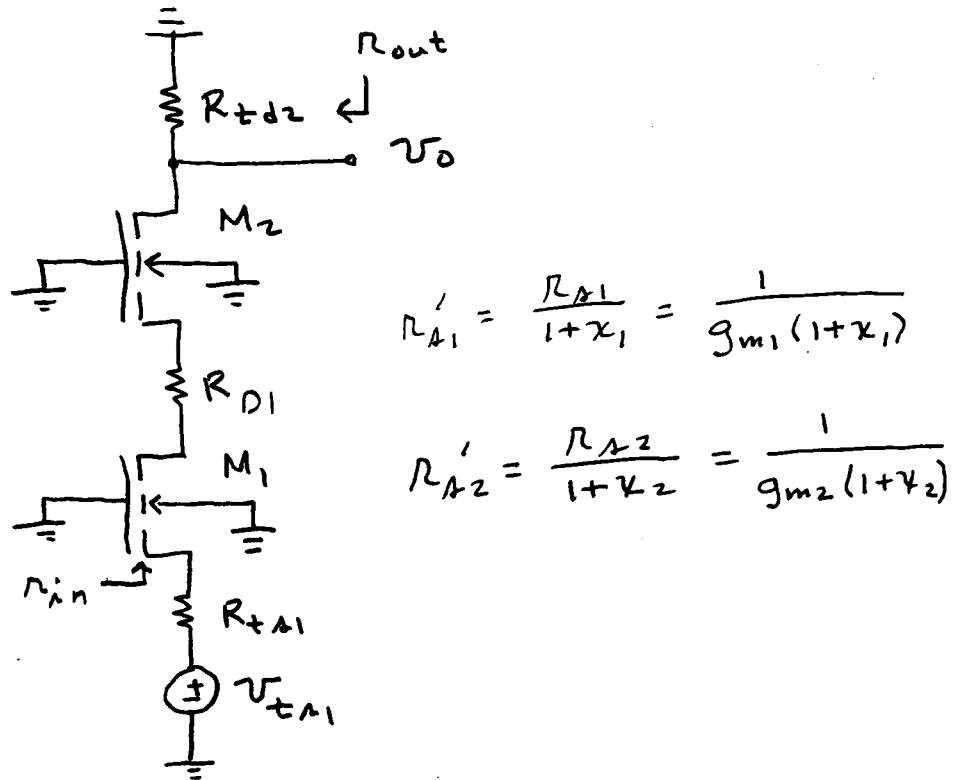


1-6/19/03

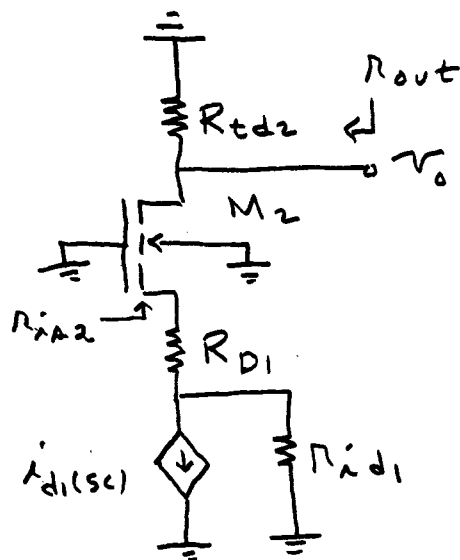A Two Stage CG Amplifier with Body Effect



Replace M_1 with its Norton Drain Circuit



2 - 6/19/03

where

$$i_{d1}(sc) = -G_{m1} v_{t11}$$

$$G_{m1} = \frac{1}{R_{t11} + R_{A1}' \parallel R_{o1}}$$


$$R_{A1}' = \frac{R_{A1}}{1 + \gamma_1} = \frac{1}{g_{m1}(1 + \gamma_1)}$$

$$R_{id1} = R_{o1} \left(1 + \frac{R_{t11}}{R_{A1}} \right) + R_{t11}$$

Make a Thévenin equivalent circuit looking out of the source of M_2 .


$$v_{t12} = -i_{d1}(sc) R_{id1}$$

$$R_{t12} = R_{D1} + R_{id1}$$

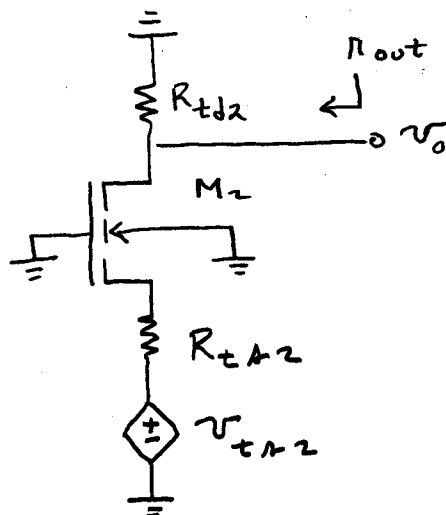

3-6/19/03

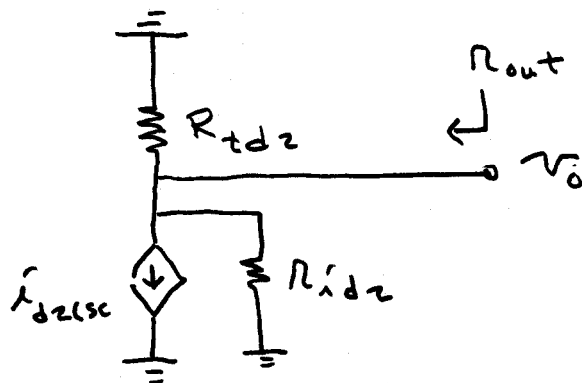Replace M_2 with its Norton drain circuit



$$v_o = -i_{d2(sc)} R_{id2} \parallel R_{td2}$$

$$= +G_{m2} v_{t2} R_{id2} \parallel R_{td2}$$

where

$$G_{m2} = \frac{1}{R_{t2} + R_{A2}' \parallel R_{o2}}$$

$$R_{id2} = R_{o2} \left(1 + \frac{R_{t2}}{R_{A2}'} \right) + R_{t2}$$

Combine results to obtain

$$v_o = +G_{m2} \left[-(-G_{m1} v_{t1}) R_{id1} \right] R_{id2} \parallel R_{td2}$$

Thus the voltage gain is

$$A_v = \frac{v_o}{v_{t1}} = G_{m1} R_{id1} G_{m2} R_{id2} \parallel R_{td2}$$

4 - 6/19/03

The output resistance is

$$R_{out} = R_{id2} \parallel R_{td2}$$

To solve for the input resistance, we must solve for R_{td1} . This is given by

$$R_{td1} = R_{o1} + R_{ia2}$$

where

$$R_{ia2} = R_{A2}' \frac{R_{o2} + R_{td2}}{R_{A2}' + R_{o2}}$$

The input resistance is given by

$$R_{in} = R_{ia1} = R_{A1}' \frac{R_{o1} + R_{td1}}{R_{A1}' + R_{o1}}$$