


ECE 3050 Analog Electronics Quiz 7

July 1, 2009

Professor Leach Last Name: _____ First Name: _____

Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials _____ For credit, you must give all equations that you use to calculate your answers. Credit will not be given for any answer without full supporting work.

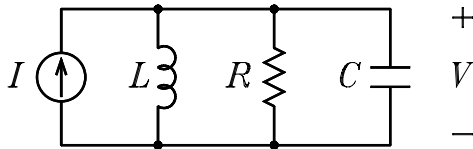
- 1 of 2. (a) Solve for the differential equation for the voltage V . Consider the current I to be an independent source.
 (b) Convert the differential equation into the transfer function $T(s) = V/I$.



$$i = \frac{1}{L} \int v dt + \frac{1}{R} v + C \frac{dv}{dt} \quad \frac{di}{dt} = \frac{1}{L} v + \frac{1}{R} \frac{dv}{dt} + C \frac{d^2 v}{dt^2}$$

$$sI = \frac{1}{L} V + \frac{1}{R} sV + Cs^2 V \quad Z = \frac{V}{I} = \frac{s}{\frac{1}{L} + \frac{s}{R} + Cs^2} = R \frac{\frac{L}{R} s}{LCs^2 + \frac{L}{R} s + 1}$$

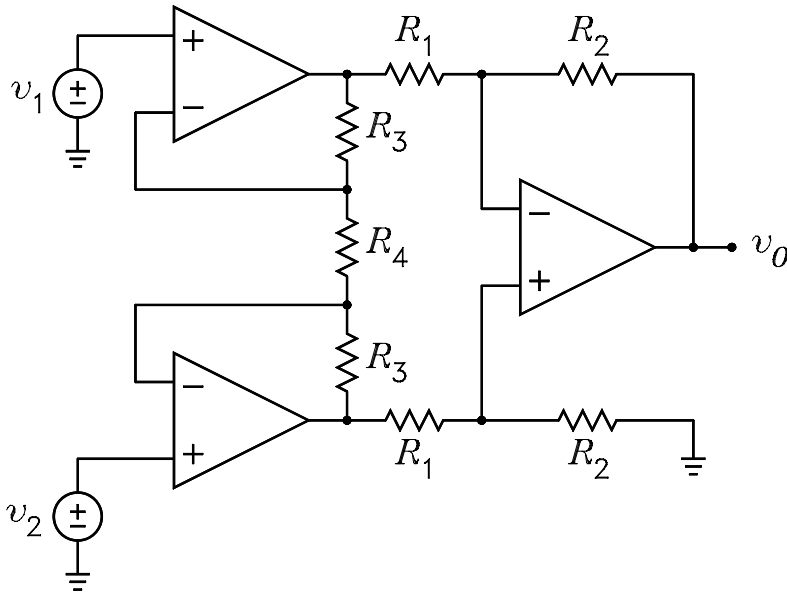- 2 of 2. For $R_1 = 10 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_3 = 2 \text{ k}\Omega$, and $R_4 = 100 \Omega$, $v_1 = 0.03 \text{ V}$, and $v_2 = -0.02 \text{ V}$, solve for and label the voltage at each node in the circuit. (There are 7 node voltages to solve for.)



$$v_{N1} = v_1 = 0.03 \text{ V} \quad v_{N2} = v_2 = -0.02 \text{ V}$$

$$v_{O1} = \left(1 + \frac{R_3}{R_4}\right) v_1 - \frac{R_3}{R_4} v_2 = 21 \times 0.03 - 20 \times (-0.02) = 1.03 \text{ V}$$

$$v_{O2} = \left(1 + \frac{R_3}{R_4}\right) v_2 - \frac{R_3}{R_4} v_1 = 21 \times (-0.02) - 20 \times 0.03 = -1.02 \text{ V}$$

$$v_O = \frac{R_2}{R_1} (v_{O1} - v_{O2}) = 2 \times (1.03 + 1.02) = 4.1 \text{ V}$$