

ECE 3050 Analog Electronics Quiz 2


June 2, 2010

Professor Leach Last Name: _____ First Name: _____

Instructions. Print and sign your name in the spaces above. Place a box around answers when appropriate.

Honor Code Statement: *I have neither given nor received help on this quiz.* Initials _____

- 1 of 2. Given: $R_C = 12\text{ k}\Omega$, $R_B = 82\text{ k}\Omega$, $R_E = 1.5\text{ k}\Omega$, $V^+ = 15\text{ V}$, $\beta = 99$, $V_{BE} = 0.65\text{ V}$, and $I_C = \beta I_B = \alpha I_E$
- Write the equations for V_{BB} and R_{BB} . Why is R_B not a part of the equation for V_{BB} ?
 - Write the equations for V_{CC} and R_{CC} .
 - Draw the bias equivalent circuit and write the loop equation for I_C .
 - Use the equation found above to solve numerically for I_C .

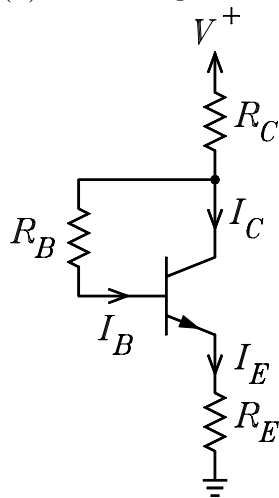

$$V_{BB} = V^+ - I_C R_C \quad R_{BB} = R_B + R_C$$


R_{BB} is not part of V_{BB} because you set $I_B = 0$ to solve for V_{BB} .

$$V_{CC} = V^+ - I_B R_C \quad R_{CC} = R_C$$

$$V_{BB} - V_{EE} = I_B R_{BB} + V_{BE} + I_E R_{EE} \implies V^+ - I_C R_C = \frac{I_C}{\beta} (R_B + R_C) + V_{BE} + \frac{I_C}{\alpha} R_E$$

$$I_C = \frac{V^+ - V_{BE}}{R_C + \frac{R_B + R_C}{\beta} + \frac{R_E}{\alpha}} = 1\text{ mA}$$

- 2 of 2. (a) The hybrid- π model of the BJT is shown with a Thévenin equivalent source connected to the base. Write the equation for the emitter voltage v_e as a function of v_{tb} , i_b , and any appropriate resistors.
- (b) If i_0 is neglected and $i'_c = g_m v_\pi = \beta i_b = \alpha i'_e$, solve the equation obtained above for v_e as a function of v_{tb} , i_e , and any appropriate resistors.
- (c) Use the equation obtained above to obtain and draw the Thévenin equivalent circuit seen looking into the emitter.

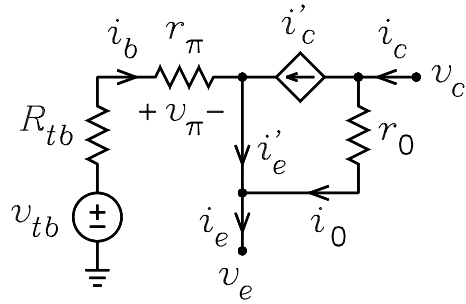

$$\begin{aligned}
 v_e &= v_{tb} - i_b (R_{tb} + r_\pi) = v_{tb} - \frac{i'_e}{1 + \beta} (R_{tb} + r_\pi) \\
 &= v_{tb} - (i_e - i_0) \frac{R_{tb} + r_\pi}{1 + \beta} \simeq v_{tb} - i_e \frac{R_{tb} + r_\pi}{1 + \beta}
 \end{aligned}$$

The circuit is a voltage source v_{tb} in series with a resistor $(R_{tb} + r_\pi) / (1 + \beta)$.